


MAKING A KILO-VOLTMETER

Practical Television 13

JUNE 1957

AND TELEVISION TIMES

EDITOR: F.J. CAMM

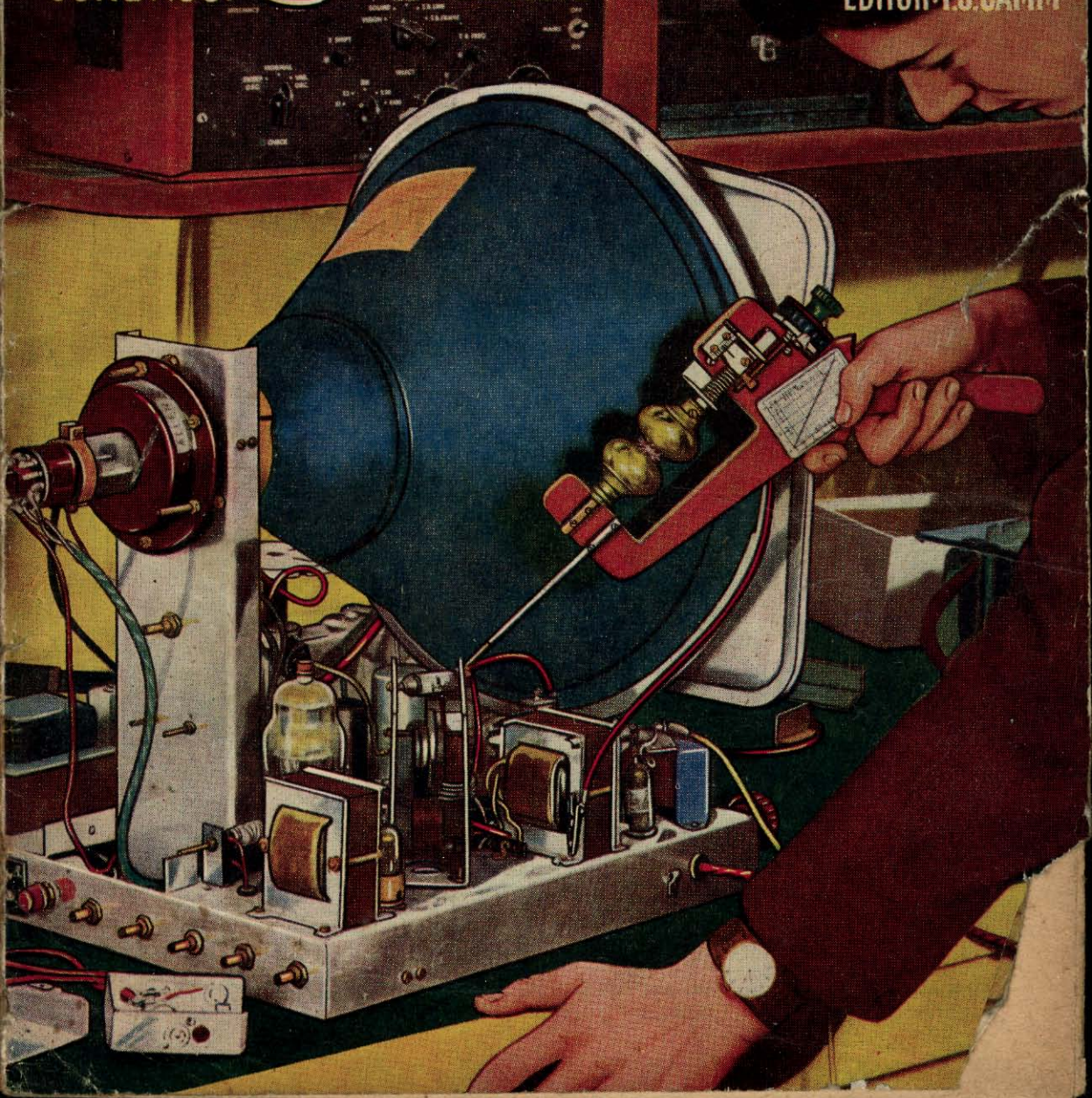

TELEVISION TUBES

MULLARD	...	12in. £6.10.0	14in. £7.0.0	17in. £8.10.0
COSSOR	...	12in. £6.10.0	14in. £6.10.0	17in. £8.10.0
EMITRON	...	12in. £6.10.0	14in. £7.0.0	17in. £8.10.0

MULLARD. 12in. now 6 weeks delivery. All other types ex-stock.

MONTHLY CLEARANCE REDUCTIONS

MAZDA	...	14in. £5.10.0	15in. £6.10.0	17in. £7.0.0
MULLARD	...	16in. Metal Cone £5.10.0	17in. Metal Cone £6.10.0	
CATHODEON	...	14in. £6.0.0		17in. £7.0.0

All Tubes plus 12/6 carriage and insurance.

SIX MONTHS' GUARANTEE

Terms to the Trade.

RE-VIEW (LONDON) LTD.

81, HIGH STREET . . . MERTON S.W.19

Telephone : CHERRYWOOD 3255

PREMIER RADIO COMPANY

OPEN TILL
6 P.M. SATURDAYS

(Regd.) B. H. MORRIS & CO. (RADIO) LTD.
(Dep. P.T.) 207, EDGWARE ROAD, LONDON, W.2

Telephone :
AMBASSADOR 4033
PADDDINGTON 3271

SAFETY FIRST!

Build these PREMIER TELEVISORS

*which give complete safety
to the constructor!*


These Televisors use a double wound mains transformer which gives you complete safety from contact with the mains supply when handling the chassis or controls.

★ **BBC & ITA** (WITH NEW TURRET TUNER)

DESIGN No. 1 **£33.7.11** PLUS COST OF C.R.T.

★ **BBC** (ALL CHANNELS)

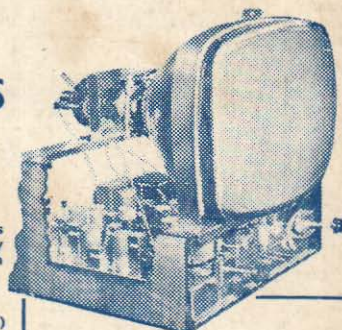DESIGN No. 2 **£27.9.4** PLUS COST OF C.R.T.



WHY buy surplus or reconditioned tubes when these Fully Guaranteed Wide Angle Tubes are available? The latest type 17in. Rectangular Tube MW43/64 by Telefunken at £17 (inc. tax) post and packing 21/- extra. Also 14in. Rectangular Tube Type 14 LP4, £13.17.6 (inc. tax), Pkg. & carr. 15/- extra.


CONSOLE CABINETS with full length doors for 14in., 15in. and 17in. tubes. PRICE £14.14.0. H.P. Terms: Deposit £6 and 9 monthly payments of 18/6. CONSOLE CABINETS, half door, still available at £12.12.0. H.P. Terms: Deposit £6.6.0 and 8 monthly payments of 18/3.

On above cabinets add 21/- for pkg. and carr.

MAY BE EASILY BUILT IN 5 SEPARATE UNITS
FULL CONSTRUCTION DETAILS AVAILABLE. INSTRUCTION BOOK 3/6 POST FREE INCLUDES BOTH DESIGNS.
SEND 2d. STAMP FOR OUR 1957 CATALOGUE



Practical Television

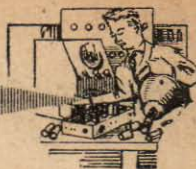

& TELEVISION TIMES

Editor : F. J. CAMM

Vol. 7 No. 83

EVERY MONTH

JUNE, 1957

TELEVISIONS

COLOUR TV IN AMERICA

AN extraordinary situation has developed in America as a result of the too-early publicity relating to colour television. The American public was led to believe that it was just round the corner. As a result, the sales of black and white receivers dropped considerably and several of the large companies were therefore forced to cut their prices below cost in order to clear their stocks. Some of the large firms, such as Columbia and Raytheon, decided to cease manufacture of television receivers, and they disposed of their stocks at low prices. Other manufacturers were forced to follow suit. At the same time, R.C.A. was indulging in an intensive campaign of propaganda on colour television, and its associated network, N.B.C., was putting out three hours of colour programmes a day. As a result, the American public presumed that colour television was near and they declined to buy black and white receivers.

As all manufacturers had cut the prices of black and white receivers, a price level was established for that type which was not really representative of the true value, and so there is a great disparity between the market price of a black and white receiver and a colour receiver, the former costing about 160 dollars and the latter 500 dollars. The American public is therefore not prepared to pay what it wrongly considers to be too high a price for colour TV.

The inevitable result is that there is now only one manufacturer in the market, R.C.A., which manufactured only 102,000 colour sets last year; yet three years ago, Sarnoff publicly stated that he had budgeted for an annual production during last year of over 6 million colour TV receivers! It is not surprising, therefore, that the American television industry is in a very bad way. Those who have tried to receive the colour television programmes on black and white receivers, especially those a long way from the transmitter, complain of the poor quality and that the pictures are full of dots and distortion. Equally, reception of black and white transmissions on a colour set is inferior. It is well-known that colour television receivers are troublesome and require a great deal of servicing, and the service engineers do not exist in sufficient numbers. This country can take a lesson from America in this respect and manufacturers should cease to talk airily about colour television being round the corner, if they do not wish to duplicate the American experience.

Although colour television is inevitable it will be some years before it has been brought to the stage where it possesses entertainment value, and the technique at present will need considerable improvement—possibly an entirely new system—

F. J. C.

Editorial and Advertisement Offices :
PRACTICAL TELEVISION
George Newnes, Ltd., Tower House,
Southampton Street, Strand, W.C.2.
Phone : Temple Bar 4363.
Telegrams : Newnes, Rand, London.
Registered at the G.P.O. for trans-
mission by Canadian Magazine Post.

SUBSCRIPTION RATES

including postage for one year

Inland - - 17s. 6d. per annum
Abroad - - 16s. 6d. per annum
Canada - - 16s. per annum

CONTENTS :

	Page
Editorial	503
Beginner's Guide to TV	504
An Automatic TV Clock	507
Servicing the Etronic ECV1523 and ECV1527	509
A Band III Aerial for the Loft	512
A C.R.T. Quality Tester	515
Starting a Service Dept.	517
A Projection TV Improve- ment	521
Making a Kilo-voltmeter	524
Oscillator Radiation	526
Telenews	531
Underneath the Dipole	535
Correspondence	539
Your Problems Solved	543


The Editor will be pleased to consider articles of a practical nature suitable for publication in "Practical Television." Such articles should be written on one side of the paper only, and should contain the name and address of the sender. Whilst the Editor does not hold himself responsible for manuscripts, every effort will be made to return them if a stamped and addressed envelope is enclosed. All correspondence intended for the Editor should be addressed to : The Editor, "Practical Television," George Newnes, Ltd., Tower House, Southampton Street, Strand, W.C.2.

Owing to the rapid progress in the design of radio apparatus and to our efforts to keep our readers in touch with the latest developments, we give no warranty that apparatus described in our columns is not the subject of letters patent.

Copyright in all drawings, photographs and articles published in "Practical Television" is specifically reserved throughout the countries signatory to the Berne Convention and the U.S.A. Reproductions or imitations of any of these are therefore expressly forbidden.

Our next issue, dated July, will be published on June 21st.

A Beginner's Guide to Television

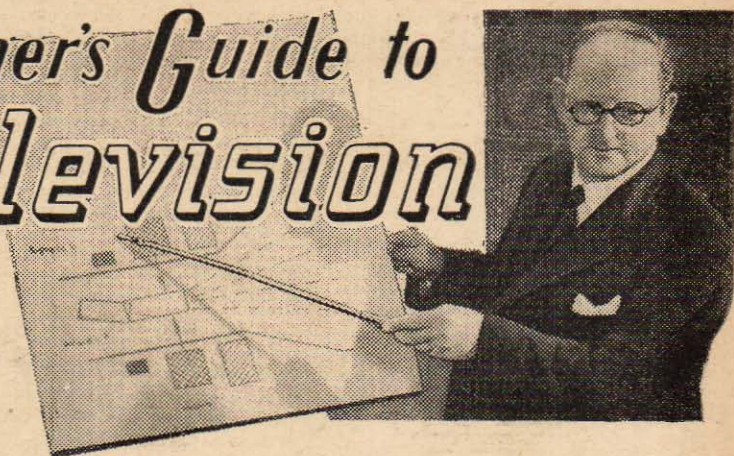

TECHNICAL TERMS (contd.)

By F. J. Camm

Image Drift

A TERM referring to the drifting movement of the received image on a television screen which sometimes occurs in consequence of slight lack of synchronisation.

Incident Ray

Name applied to any ray of light which falls upon an object or medium.

Indirectly Heated Cathode

A cathode heated by an electrically separate element known as the heater.

Intensity Modulation

The usual method of modulating the output current of a television transmitter by means of variations in the intensity of the light reaching the photo-electric cell of the transmitter.

Intercalation

Synonymous term for interlacing, as related to television scanning.

Interlaced Scanning

A system of exploration of the scene or image in which complete scanning is accomplished in two or more operations, the strips of scanning field successively traversed in the course of one operation not being contiguous. During subsequent operations the lines previously omitted are scanned according to some set rule or order.

Ion

An atom which has been stripped of one or more of its electrons. See Ionisation.

Ion Burn

The dark patch which forms on the face of a tube due to its bombardment with the heavy ions of the electron beam. Avoided by using an aluminised screen or an ion trap.

Ion Trap (Beam Bender)

A small magnet placed at the rear of the neck of a specially made tube to prevent ion burn. The gun

is not straight in this type of tube, but is offset so that the beam would normally fall outside the face of the tube. The magnet deflects only the lighter part of the beam and brings it, when properly adjusted, on the face in the normal manner, but the heavier ions carry on the original path and thus do not strike the screen.

Ionisation

In television terminology this expression refers to the production of "ions" within an electric discharge tube such as, for instance, a neon tube.

The neon tube contains a small proportion of neon gas. An electrical discharge passed through the tube strips away some of the outer electrons from each atom of neon gas. Owing to the loss of negatively charged electrons, each atom of neon gas shows a positive charge and it is called an "ion," the electron-stripping process to which it has been subjected being termed "ionisation."

Ions are electrically conductive. Hence, when they are present in comparatively small numbers within a gas discharge tube, they allow the current to pass and they give off a characteristic glow. The glow of electrically excited neon ions is, as is well known, a pinkish-orange shade.

Isochronism

The operating condition which obtains when the reconstruction of the image and the scanning of the object occur at the same time.

Light-sensitive Cell

A general term applying to any electrical device which, on illumination, undergoes a modification in its electrical properties. All photocells are included under this general definition.

Magnetic Focusing

Term referring to a method of focusing the beam of rays in a cathode-ray tube by placing an electromagnetic coil in their path.

Lissajou's Figures

Any closed figures traversed by a point moving with the resultant of two periodic oscillatory motions at right-angles. Originally applied to certain experi-

ments in connection with pendulums and sound, but now used for a class of records of this nature by such instruments as the cathode-ray oscillograph.

Low Definition

A system of television in which the number of scanning lines into which the complete picture is divided is less than 100. Low definition systems are now obsolete.

Mirror Drum

An obsolete scanning device employed in some early television systems. Essentially, it consisted of a drum-shaped wheel having fixed upon its periphery or outer edge a number of mirrors, each

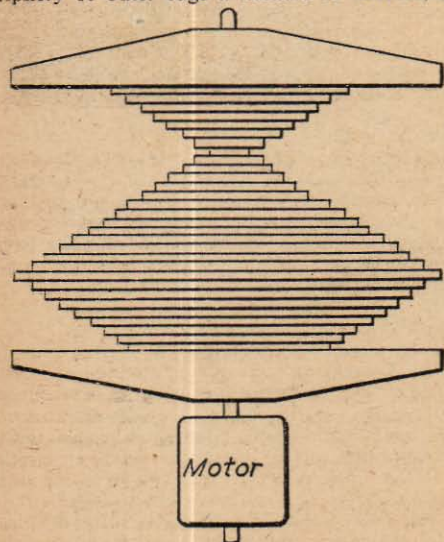


Diagram of a mirror screw.

mirror being tilted at a slightly different angle from that of the preceding mirror. A beam of light is suitably focused upon the edge of the mirror drum, which is rapidly rotated, thus causing a light spot to be flashed in successive lines over the image or object to be televised.

In a similar way, also, the mirror drum is made to assemble the televised picture at the receiving end.

The main advantage of the mirror drum is that it allows a more intense spot of light to be focused upon the object.

Mirror Screw

Another obsolete scanning device comprising a number of mirrors arranged on a frame in the form of a screw spiral. Unlike the mirror drum (which see) the mirrors are not separately tilted in relation to one another, the directing of the light spot on the screen or on the object to be televised being effected by the suitable and exact positioning of the mirrors on the spiral.

The mirror screw does not reflect the light as does the mirror drum. It has, however, the advantage of greater compactness.

Multiple Scanning

Expression referring to television systems in which two scanning devices, as, for example, two mirror

drums, reflect the televised picture on to a screen, the object of these methods being to increase the intensity of the illumination on the screen.

Negative Image

An image resembling that shown by a photographic negative, i.e., one in which the light parts of the original picture are dark and the dark portions of the original are light. It is the opposite of a positive image.

Some television receivers will give rise to negative images on their screens when a fault or maladjustment is present in the electrical circuit of the receiver.

Neon Timebase

Name given to a timebase circuit in which a neon lamp provides the means of providing a periodic voltage across one pair of deflector plates in a cathode-ray tube.

Nipkow Disc

Name sometimes given to the scanning disc employed in many television systems. It was originally the invention of the Polish scientist, Paul Nipkow, in 1884. Nipkow employed it in the crude shadowgraph transmitters with which he experimented at the end of the last century.

Objective


A frequently used term which denotes the image-forming or projecting lens of an optical instrument, as, for instance, the projection lens of a television or film/television apparatus.

Orthicon

The special camera used for television. The American name for the Emitron camera.

Oscillatory Scanning

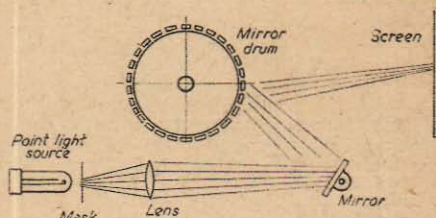Name given to scanning methods by means of which the light spot oscillates or travels forwards and backwards over the image to be televised. After each complete oscillation the light spot shifts laterally,



Details of the mirror drum projector.

thus enabling the new area of the picture to be scanned. Oscillatory scanning possesses many practical disadvantages.

Oscillogram

Name given to the wave-like pattern, representing the graphical form of an alternating current, which is traced out by the light spot on the fluorescent screen of a cathode-ray oscillograph tube.

Oscillograph

See cathode-ray tube.

Out of Frame

The state of a televised image when, as seen on the screen of the receiver, it is divided horizontally or vertically, the two portions of the image appearing in opposite positions. The image is correctly "framed" by the manipulation of a small control which influences the synchronising gear of the receiver.

Parabolic Reflector

Name given to a light reflector, usually of highly polished metal, which, being shaped to a parabolic curve (a parabola is the section of a cone cut parallel to one of its sloping sides) causes a beam of parallel rays to be reflected from an illuminating source placed in the focus of the reflector.

Parabolic reflectors are frequently used for obtaining strong beams of parallel light rays in optical experiments connected with illuminating and light-projecting matters.

Parallel Rays

Light rays which travel parallel to one another, as, for instance, the light rays reflected from a parabolic reflector. Light rays coming from a very distant object, such as the sun, are always parallel from a practical standpoint, although, in strictest truth, they are very slightly divergent.

Persistence of Vision

When light rays impinge upon the retina of the eye the impression which they make does not cease immediately the light rays stop. On the contrary, it persists for an appreciable time afterwards, this effect being known as "persistence of vision," or "visual persistence."

It is upon this "lag of the retina," as persistence of vision is sometimes called, that we are able to build up a reproduction of motion on the television or cinema screen, in both instances a series of successive pictures (each differing slightly from the preceding one) being formed or thrown on a screen so rapidly that the eye is not able to get rid of the impression made by the one picture or image before the next one arrives.

Phase Shift

A condition in television reception in which, owing to stray circuit capacities in the receiver, the fluctuations in voltage do not keep in step with those originally transmitted, particularly at high and low frequencies. This results in some of the details of the televised picture being received at a later instant of time than the remainder of the picture, thereby setting up a displacement or distortion of the televised image.

Photo-electric Cell

A light-sensitive device which, by emitting a stream of electrons under the influence of light rays and in proportion to the amount of light falling upon it, enables light to be turned into electricity.

Photo-electric cells are of two kinds, viz., the Emission type and the Photronic or self-generating type.

Photo-electrons

Name sometimes applied to the stream of electrons which are liberated from certain bodies under the influence of light.

Photo-electric cells operate in virtue of the presence within them of a stream of photo-electrons whenever they are illuminated by light rays.

Picture Elements

Name given to the minute areas into which a picture, portrait, or scene which is to be televised is split up by one means or another. The picture elements are all of the same size, but they differ in brightness. The portion of the scene which determines or is determined by the instantaneous value of the signal current.

Picture Frequency

The number of complete images transmitted per second.

Polarisation

Applied to light rays the term denotes the cutting off of all the rays in a beam of light except those which vibrate in one plane. Light consisting of these one-plane vibrations is said to be "polarised" and, in such a condition, it possesses peculiar properties of its own. Light rays are usually polarised by passing them through certain crystals, such as Iceland Spar, which effect the process automatically.

Positive Image

The image as it is normally seen on a television screen. A photograph or any other type of illustration is a positive image, the lights and shades of it being a true or approximate reproduction of those of the original. A positive image is, as its name implies, the opposite to a negative image.

Primary Current

A term used in connection with gas-filled photo-electric cells to signify the actual minute current set up by the impact of light upon the sensitive cathode of the gas-filled cell.

Prism

A triangular-shaped piece of glass or other transparent material used in practical optical work for bending rays of light through a right-angle, and also in the spectroscope, for splitting up rays of light into their component colours.

Progressive Scanning

A system of exploration of the scene or image in which continuous strips of the scanning field are traversed in order.

Raster

The rectangular picture area built up by the scanning spot on the end of the cathode-ray tube.

Recurrent Vision

Name given to the phenomenon of an image recurring one or more times to the eye after the actual light rays from the object have been cut off.

Recurrent vision was first noted by Young in 1801, who observed that after an object had been intensely illuminated by an electric spark, the image recurred to the eye several times after the spark had passed, the image becoming fainter with each successive recurrence.

Reflection

The recoil of light rays from the surface on which they impinge.

(To be continued)

AN AUTOMATIC TV CLOCK

A MECHANICAL DEVICE

FOR SWITCHING ON OR OFF A TV OR RADIO SET

By Michael Dunn



It can so easily happen in a large and busy family that the beginning of a much-desired television (or radio) programme is missed, simply because nobody remembers to switch on at the right time; in fact, it is sometimes remembered only after the entire programme has ended. With the device to be described it is possible to set the timer at leisure, any convenient time prior to the programme, so that it will switch the set on automatically at the desired moment. It has proved its value over and over again.

Essentially the unit consists of an "alarm" clock which will switch on the set and an auxiliary circuit which will maintain it switched on indefinitely. Although the following details refer to the writer's own model, the principles involved can be subject to personal variation and improvement, both as regards the choice of components and the general layout. The entire unit was made from oddments already to hand and it is, therefore, not really possible to estimate the total cost. For instance, the telephone bell box was purchased on the surplus market for ninepence, is very nicely made in solid mahogany and makes the finished job look most professional—at any rate from the outside. The central feature is the electric alarm clock movement and it is around this that the circuit is designed. The telephone bell box was found ideal for the purpose and hangs on the wall beside the radio, serving also the additional function of telling the time. Being easily transportable it can also serve as an ordinary alarm clock, since the

bell was retained *in situ* and switched in parallel with the output. The bell can, therefore, serve the very useful purpose of calling the family from remote parts of the house or garden, at the same time as the set is switched on.

The original idea was simply to use the clock to switch on the television, but it was soon realised that a great improvement would be effected if the set could be kept on indefinitely and this is done by utilising the current drawn from the mains by the set itself to drop a few volts which will operate a relay.

The best way to describe both the layout and the function of the unit is to follow the circuit diagram (Fig. 1). It will be seen that it interrupts the mains supply to the set, but that for normal operation there is a by-pass switch which simply short-circuits the automatic timing switch circuit so that the TV can be turned on and off by its own switch in the usual manner. The clock, however, is permanently connected to the mains so that it keeps and tells the correct time. When wishing to make use of the automatic switching, the procedure and mode of operation are as follows:

1. With the by-pass switch closed, turn on the set in the normal way and tune to the desired station. The volume can then be adjusted to optimum level.

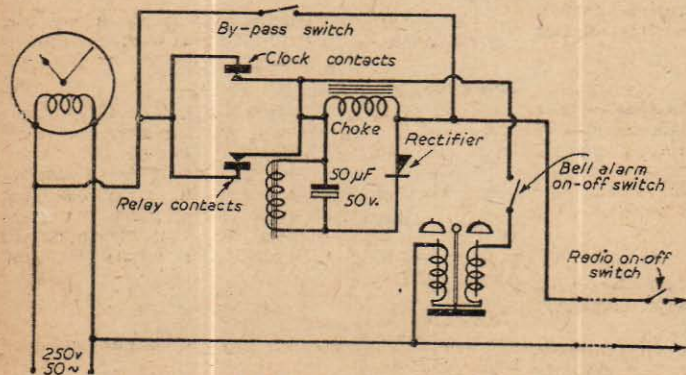


Fig. 1.—Theoretical circuit of the automatic clock switch.

LIST OF COMPONENTS

- (1) Electric alarm clock movement (or equivalent electrical timing device).
- (2) Dial, hands, bezel and glass for same (optional).
- (3) Suitable low impedance inductance (see text).
- (4) Metal rectifier: 12 volt 0.25 amp. or less (optionally F.W.).
- (5) Low voltage relay (less than 12 volts).
- (6) By-pass switch. S.P.S.T. toggle.
- (7) Electric bell (optional).
- (8) On/off switch for same. S.P.S.T. toggle.
- (9) Capacitor, 50 µF, 50 volts working (or less), electrolytic.
- (10) Container.

(Of course, if the station is not on the air at the time as, for instance, during some parts of the day, this will have to be done by eye and not by ear.)

2. Leave the set switched on, but open the by-pass switch which will effectively separate it from the mains.

3. Set the alarm clock indicator to the time of the desired programme.

At the appropriate moment the clock contacts will close and switch on the set. This will draw current through the inductance, across which will be dropped from six to 12 volts which, after rectification, operate the relay whose contacts are in parallel with those of the clock. Thus the set will remain switched on independent of the clock contacts, which will eventually open again and otherwise break the circuit. When the set is switched off (e.g., at the end of the programme) current will cease


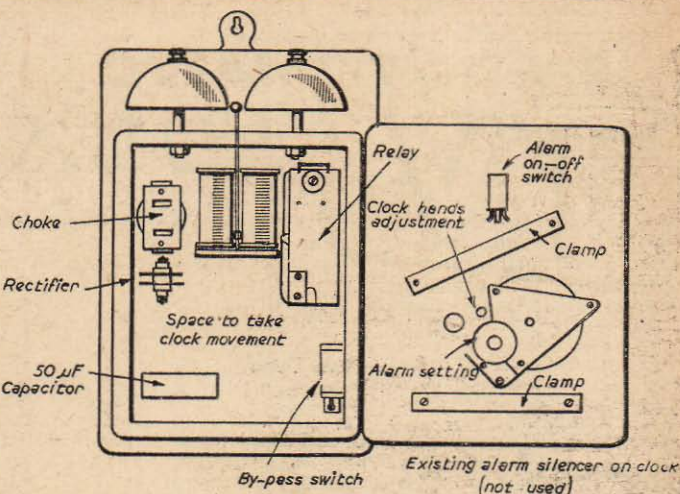


Fig. 3.—Details of the parts. The silencer is the large central circle.

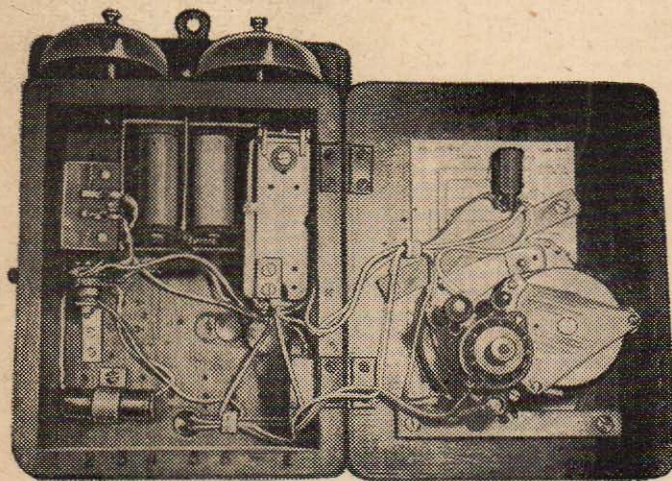

A view of the clock as shown in Fig. 3 above.

to flow through the inductance, the relay contacts will open and the cycle of events will return to its starting point. The set cannot, then, be switched on again until the by-pass switch is closed. Because the set is independent of the clock contacts the moment the relay has closed, the timing indicator may be re-set any time after that for a further programme if desired; or alternatively the by-pass switch may be closed for normal operation.

This timing unit can, of course, also be used to switch on any relatively low-powered apparatus at a predetermined time. If one considers the mode of working, it is manifest that the initial flow of current is made by the closing of the clock contacts—those of the relay closing a fraction of a second later when the current is already flowing. The current is broken solely by the on/off switch of the set (or other relevant apparatus) itself, so that neither the clock nor the relay contacts ever have to break the current. The

power limitations of the timer are, therefore, those of the capacity of the clock contacts to make the circuit and of both these and those of the relay to conduct it. So long as these are robust, it can serve many useful purposes as a delayed action switching device.

Components and Constructional Details

The clock movements used by the writer was an old one from a disused Smith's alarm clock. As it had no dial or hands these were provided from another broken and useless (mechanical) clock of suitable size. A circular hole of the right diameter was cut in the door of the box so that the glass and bezzel fitted friction tight. The dial and hands were fitted to the movement which was then clamped to the inside of the door so that it appeared quite central.

(Concluded on page 528)

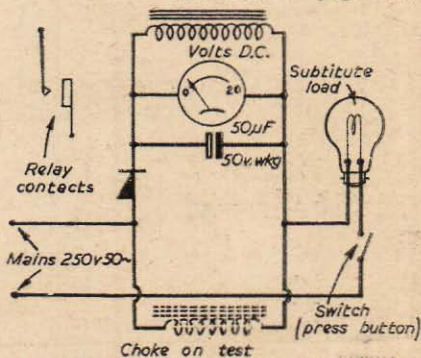


Fig. 4.—Experimental circuit for obtaining suitable value of inductance.

set-screws, through exact centre of each slot.

Next cut out the short wood block. The author used ordinary wood dowelling to fix after treating the block with glue.

The $\frac{1}{4}$ in. Perspex panel can then be cut out and drilled with the four holes, two being to attach the panel to the block, and two to fix the dipole back to the panel. Plywood could be used instead of Perspex without much loss, but the plastic will be found less likely to warp.

Cut the directors to the correct lengths from the $\frac{1}{4}$ in. duralumin tubing, and the reflector from the $\frac{1}{4}$ in. copper tubing. Cut off a sufficient length of copper tubing for the dipole, the details of which are shown in Fig. 1. This is quite a tricky business

worry too much if the tube is somewhat out of its true tubular section on the bends, and the author's does actually appear flatter at the bends than shown. Heat can be used, but care is required, as copper conducts heat very readily and unlike iron or steel the metal is softened if quenched in water. When exactly to shape, cut out and drill a piece of copper sheet for the flange, drill this with fixing holes, and sweat it in position at the top of the lower limb. A soldering iron is useless for this job, and it can

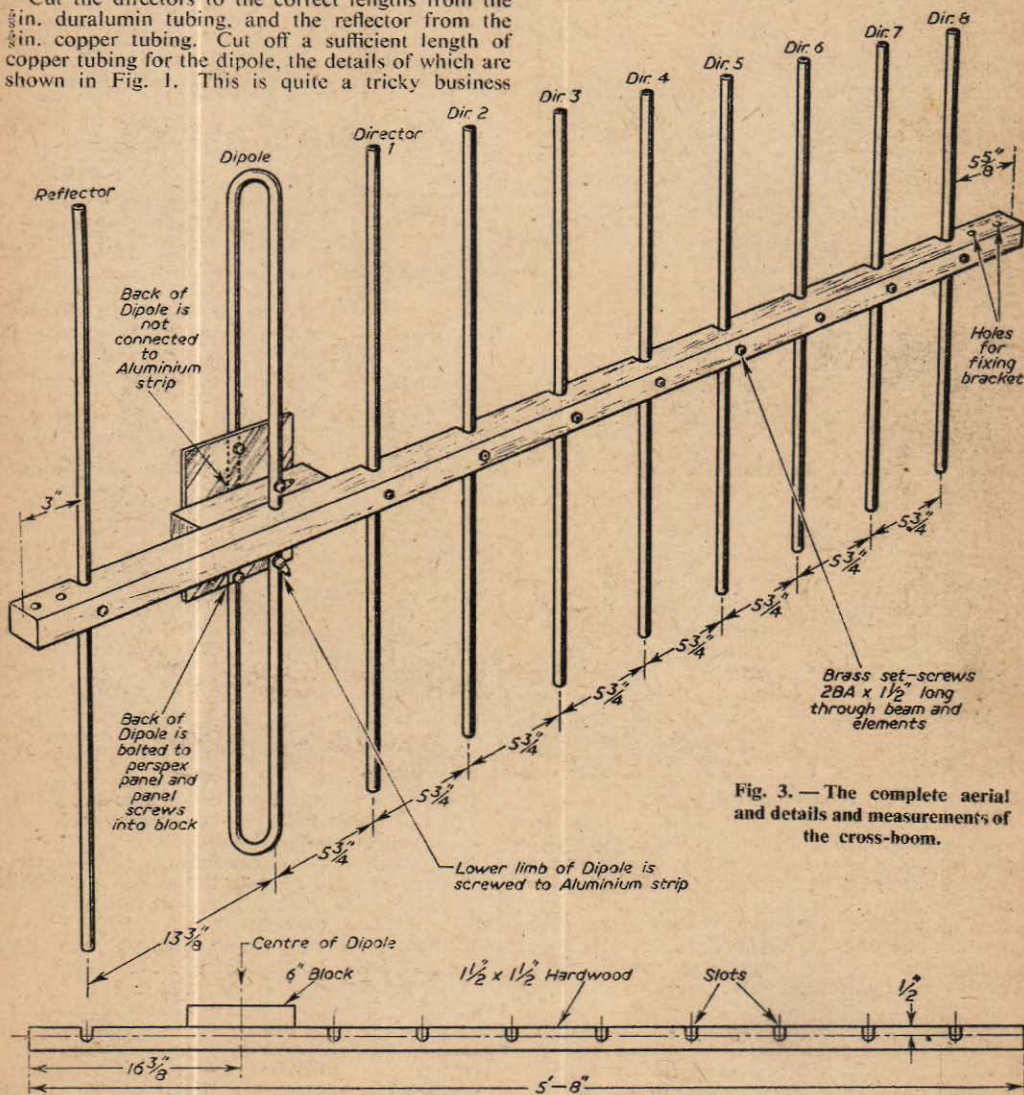


Fig. 3.—The complete aerial and details and measurements of the cross-boom.

especially the bending, and a full-size paper drawing should preferably be made, as shown in Fig. 1, but without dimensions. As the bending proceeds this will act as an accurate guide or template. A piece of string measured around the outside of the drawing will give the exact length of tubing required. Do not

only be done by heating the job over a gas flame, or by use of a blowlamp.

Drill each director at its exact centre, also the reflector. Aluminium foil was used by the author for the conductor, and this can be purchased in several yard lengths as cooking foil. Cut to the full

1½ in. width, and about 8 ft. long or more. Start from one end, and push into each slot, and fixing each director as you go along.

It is necessary to change from side to the underside of the beam for connecting to the lower limb of the dipole. Fig. 2 shows how this is done by four simple folds; no cutting is necessary. Some brass washers may be inserted under the cheese heads of the fixing set-screws, but if the hardwood is a good one they should not be necessary.

It will be noted that a sufficient length of beam has been allowed for, for fitting fixing brackets, although it is quite possible the aerial can be supported on suitable rafters if the direction of the aerial allows.

There are some readers who may prefer to make light trestles for each end. It is important, of course, to get the beam quite horizontal and the elements vertical.

The tubing lengths as used by the author are given below.

1 Dipole = 2 ft. 2½ in. As this is folded, over twice length should be taken to allow for bending radius.

Reflector = 2 ft. 4½ in. Director 5 = 1 ft. 11½ in.

Director 1 = 2 ft. 1½ in. Director 6 = 1 ft. 10½ in.

Director 2 = 2 ft. 1½ in. Director 7 = 1 ft. 10½ in.

Director 3 = 2 ft. 0½ in. Director 8 = 1 ft. 9½ in.

Director 4 = 2 ft. 0 in.

Spacing between Directors = 5½ in.

Spacing from Dipole to Reflector = 1 ft. 1½ in.

The aerial described was used in conjunction with a Marconi Model VT.53DA and their special converter type T2211, and it was found to tune in correctly to Channel 9 division of the converter's dial. Pick up was about equal to that of Channel 1, (also in loft) a slight adjustment of contrast control on unit only being necessary once to give an equal picture on both bands for switching purposes.

Additional Notes

The author would stress the point that this aerial was designed primarily for loft or indoor use, and it should not be erected outside where weather conditions would soon warp the wood beam.

When the beam has been slotted and drilled it should be given a coat of shellac varnish. This can be easily prepared by dissolving flake shellac in methylated spirit. This varnish dries quite quickly, and will help against any dampness warping the beam.

Stout brass screws should be used to fix the panel to the block, and make sure the panel, and dipole, are quite perpendicular. A piece of copper wire passed under each of the two screws and under the back tubing only of the dipole, is a small precaution against the possibility of ghost images caused by unconnected metal. This latter point brings up the question of loft junk. Have a look round, and remove any large metal objects lying around which might cause unwanted reflections. Old stair rods, if metal, are not helpful.

If one has a Channel 1 BBC aerial already working in the loft, some experiment will be necessary to find the best location for the new Band III aerial. The latter being more directional will, of course, be restricted to almost one definite angle.

The directors should, of course, be pointed towards the transmitter, with the reflector the farthest away.

Use good coaxial cable for this type of aerial. There is a special air spaced type, having approximately a ½ in. outside diameter. The conductor is stranded copper, and this is another point to guard

against in purchase. There are types with a solid single strand core conductor. Whilst satisfactory for the BBC band this type can cause losses on the higher frequency of Band III.

In purchasing copper tubing the inside diameter is usually referred to. It will be found that ½ in. tubing measures about ⅝ in. outside, ⅜ in. tubing equals about ½ in. outside and so on.

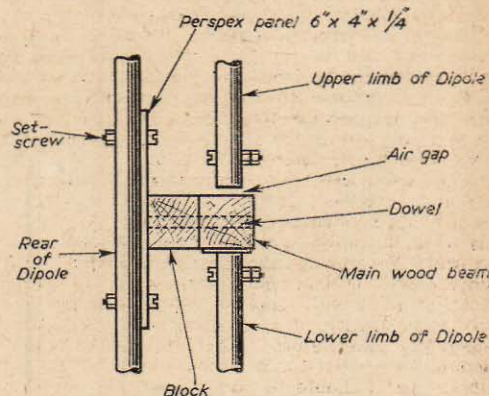


Fig. 4.—Details of the dipole gap.

If it is proposed to silver plate the copper tubing elements, dipole and reflector, the plating operation should be left until last, after all drilling, bending and sweating work is completed. The thin silver skin given by the simple plating powders will not take a lot of after friction, although, thin though it is, this type of plating does give a definite increase in efficiency, so desired in indoor aerials. After plating, remove excess chemical salts by a very light sponging with clean cold water. Do not scrub, of course, or light plating will be removed. There is little object in giving the tubes a heavier electro-plating, and that would, of course, be quite an expensive item. Keep coaxial lead clear from electric wiring cable.

Scottish Radio Show

VISITORS to the Scottish Radio Show, Kelvin Hall, Glasgow, May 22nd to June 1st, will be assured of seeing television pictures at their best. The Exhibition Technical Committee of the Radio Industry Council has made arrangements with the G.P.O. and the BBC for a vision circuit—a special land line—to be available between Kirk o' Shotts and the R.I.C. control room at Kelvin Hall, from which suitable programmes will be piped around the television receivers in the exhibition. There will also be a link between the BBC arena at Kelvin Hall and the R.I.C. control room to provide programmes at other times. And the BBC are planning an additional source of pictures—a dais for celebrity interviews equipped with TV camera.

For the alternative (Band III) television circuit, Scottish Television are to have two tele-cine equipments and two cameras providing popular TV programmes, including films—some of them current on commercial programmes in England—and live pictures from their celebrity dais.

The exhibition, of course, is too early for programmes from the I.T.A. transmitter at Black Hill.

A C.R.T. Quality Tester

ANOTHER VITAL ACCESSORY FOR THE SERVICE WORKSHOP

By J. Brown

CATHODE RAY TUBES and their condition always offer a query to both amateur and professional service engineers. We all know the 100 per cent. test is to replace the suspect with a "known to be good" tube. This means a large stock of C.R.T.s or the monotonous job of dismantling two sets to try the good tube from one. This is not possible to a busy firm or the Ham (who repairs the odd set), as there are at present no fewer than 40-50 tubes in use in various sets. The writer, however, decided to try and solve this "quality of C.R.T.s" problem; after many types of circuits, the circuit that developed is, as far as is known, completely original and most successful. Various modifications were made to the prototype and the final circuit is shown below. The circuit includes both quality test, also electrode shorts test, these are all carried out with the *Heater* at operating temperature. There is also included a method for reactivation or over-running the heater. At this stage, it should be pointed out that this has only been successful in one case out of 16 that were tried; however, this can be carried out at the last resort.

The Circuit

This is normal circuitry, using a small half-wave metal rectifier circuit to supply the small amount of D.C. voltage needed for the operations, there is perhaps unusual switching, also the transformer if built as the final instrument would have to be wound; the cost would be about 30s. Fig. 1 shows the original circuit. This used as the heater supply an Avo valve tester; any valve tester would suffice as the heater supply; this saves the cost of the transformer.

The Method of Operation

To set up to read quality, SIA-D is switched to the No. 1 position, heater voltage set to suit the tube under test, the tube is connected to the correct holder and the instrument switched on. As the heater warms up to the operating temperature, the meter needle moves to the position, giving the cathode current. Examples of readings are given as below.

A 14in. tube with poor emission and poor focus read 20 μ A.

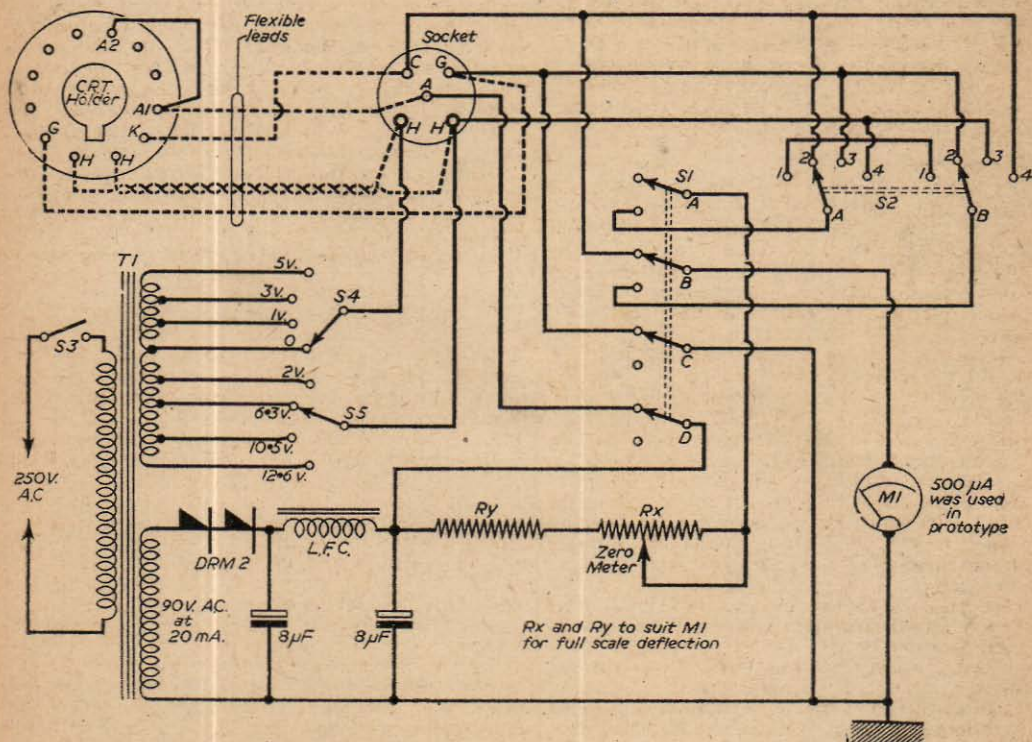


Fig. 1.—Theoretical circuit. S2 A and B are the shorts test switch. Position 1. Zero meter. Position 2. Cathode grid. Position 3. Grid/heater. Position 4. Heater cathode. Read on meter, if no reading, tube has no shorts. Shorts show up on meter as a deflection clockwise. S4 and S5 are set at 6.3 volts.

A 14in. tube brand new gave a reading of 150 μ A.
 A reactivated tube read 70 μ A after 33 mins. of reactivation (previous 25 μ A).
 A 17in. tube low in emission read 25 μ A.
 A 17in. new tube read 400 μ A.

To Reactivate

Set up as explained, with switch S5 set at the

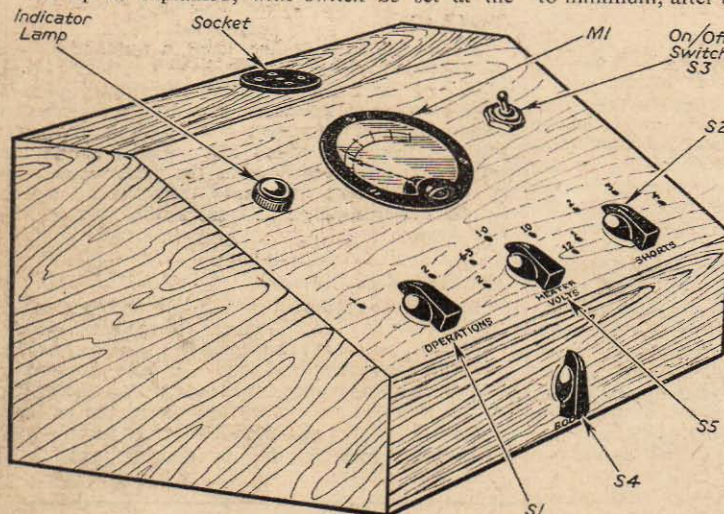


Fig. 2.—A suggested containing case for the tester. S4 should also have a scale.

correct voltage, take the quality reading. Switch S4 to 25 per cent. increase, e.g., if tube is 6.3 volts, switch S4 to increase the voltage to 1 volt boost, reactivate for a period and take the reading, if the reading has increased try in the set again. If still no good, increase the boost volts to 3 and reactivate again. This is the maximum of boost 50 per cent., this must never be exceeded at any time. The tube need not be removed from the set during this process. As explained there has been only one success this being a 12in. with poor brilliance. The tube was reactivated for 40 mins. at 2 volts plus 1 volt boost, and the reading increased from 20 μ A to 70 μ A and the tube gave another 10 months of useful life. The voltage for this test should be approximately 90 volts, at the choke. The meter used was a 500 μ A surplus movement, but a 1 mA

would be O.K., although the readings would be different and would have to be set up using tubes known to be O.K. These readings are tabulated in a little book for use when required.

To Set Up for Shorted Electrode Readings

Switch the instrument on with the zero pot, control to minimum, after the switch is in Position 1.

- Position 1. Zero meter
- Position 2. Cathode/ Grid short.
- Position 3. Heater/ Grid short.
- Position 4. Heater/Cathode short.

The meter is now zeroed up by adjusting the pot so the meter reads full scale. The voltage is not enough to damage the electrodes. Should at any time the meter read below half-scale the tube is doubtful, if it reads low (back to the settled position) there exists shorts. The switch S2 A and B can be switched to the three positions 1, 2, and 3. Any reading will give the state of shorts at the particular electrodes. Example: A 12in. tube read 90 μ A on the scale, there was very little

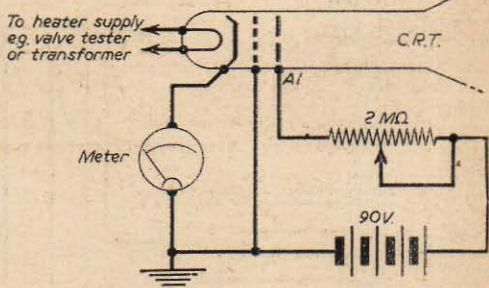


Fig. 3.—The meter may be used in the grid circuit to read grid current, but this was not successful, so the meter was placed in the cathode circuit.

COMPONENTS

Mains transformer Special Type. Wound by Majestic Winding Co.

1—DRM2 metal rectifier.

1—Receiver type smoothing choke.

2—8 μ F 250 volt working condensers.

RY and RX to suit meter used (RX was 100 K wirewound and RY was made a 1 Meg. variable also.)

S4 Single-pole 4-way.

S5 Single-pole 5-way.

S1A-D 4-pole 2-way.

S2A-B 4-way 2-pole.

500 μ A or 1 mA meter.

5-pin socket and plug (similar to the type used on batteries).

Tube holders.

Toggle switch for on/off switch.

Nuts, bolts, wire, etc.


Containing case

definition and was found to have a cathode heater short. The actual resistance with an ohmmeter 26 ohms from one side of heater to cathode and 11 ohms the other. Again emphasising these tests are carried out with the heater at the correct operating temperature as opposed to shorts trying to be found with an ohmmeter.

The 5-pin plug and socket is used, so that tubes of different bases may be tested by using extra leads and base to suit the tube. For example: Duodecal Base requires one lead, English Bases tubes use another lead, etc. This little instrument can prove its worth in a short while, as the tube quality can be tested without removing the tube from the set or carton. Whilst it is not claimed 100 per cent. infallible it gives a true report on the quality if used correctly and tabulated figures are available.

NEW! THE PRACTICAL WAY

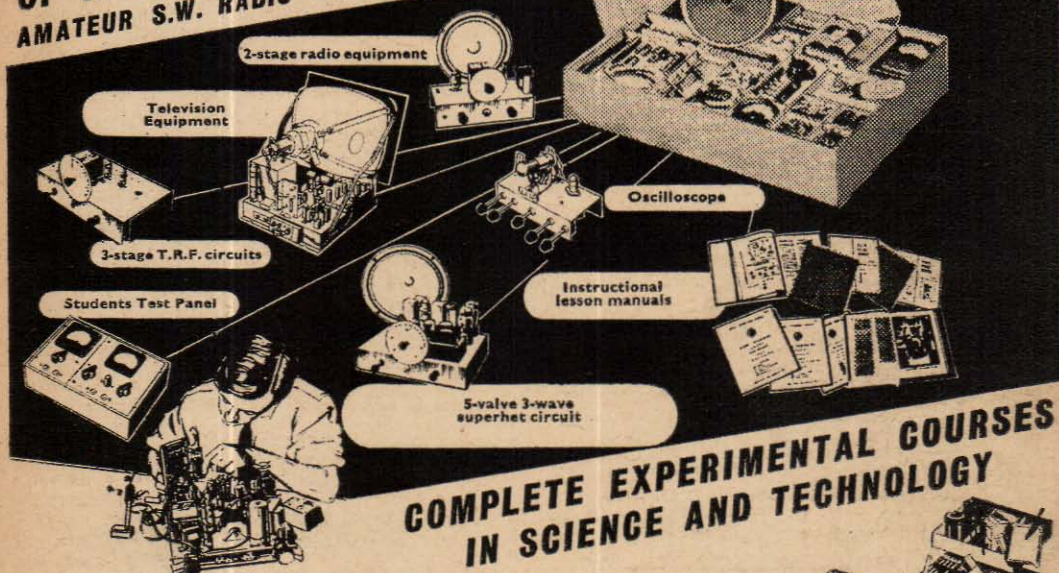of learning **RADIO • TELEVISION • ELECTRONICS**
AMATEUR S.W. RADIO • MECHANICS • PHOTOGRAPHY • CARPENTRY, Etc. Etc.



COMPLETE EXPERIMENTAL COURSES IN SCIENCE AND TECHNOLOGY

NEW... completely up-to-date methods of giving instruction in a wide range of technical subjects specially designed and arranged for self-study at home under the skilled guidance of our teaching staff.

NEW... experimental outfits and lesson manuals are despatched on enrolment and remain the student's property. A tutor is allotted to each student for personal and individual tuition throughout the course. In the case of radio and television, specially prepared components are supplied which teach the basic electronic circuits (amplifiers, oscillators, detectors, etc.) and lead, by easy stages, to the complete design and servicing of modern commercial radio and television receivers.

If you are studying for an examination, wanting a new hobby or interest, commencing a career in industry or running your own full-time or part-time business, these practical courses are ideal and may be yours for moderate cost. Send off the coupon to-day for a free Brochure and full details. There is no obligation whatsoever.

The only Home Study
College run by
a World-wide
industrial
organisation.

EMI INSTITUTES

EMI Factories at Hayes.

SUBJECTS INCLUDE—

**RADIO • SHORT WAVE RADIO
TELEVISION • MECHANICS • CHEMISTRY
PHOTOGRAPHY • ELECTRICITY • WOODWORK
ELECTRICAL WIRING • DRAUGHTSMANSHIP
ART, etc.**

**COURSES FROM
15/- PER MONTH**

E.M.I. INSTITUTES Dept. 138X, London, W 4

NAME _____ AGE _____
(if under 21)

ADDRESS _____

I am interested in the following subject(s) with/without equipment

JUNE/57 We shall not worry you with personal visits

BLOCK
CAPS
PLEASE

IC85

—Part of "His Master's Voice." Marconiophone, etc. etc.

OSMOR VARIABLE Band I ATTENUATOR

Balances reception of ITA and BBC in all areas and avoids constant adjustment of controls. The Osmor is the only variable attenuator that will reduce the signal exactly to the required level. Easily Fitted—just plug in. Reduction ratios variable 2-1 to 10-1. An Essential with all types of Band III Converters. 10/-, plus 9d. p. & p. From your Dealer—or direct.



BAND I FILTER

Rejects BBC from ITA aerial and improves picture. Suitable for all makes. Fitted in 2 minutes. 10/6, including instructions.

SWITCH-TUNED F.M.
Complete Kit for Switch-tuned F.M. Tuner with Automatic frequency control available.

ITA CONVERTERS

LONDON · LICHFIELD · MANCHESTER

A very efficient Band III Converter for all TV sets of any age (including TRF). Approximately one hour to build! Will convert any Band III Channel to any Band I Channel. Station switching. A.C. or A.C./D.C. Size 4 1/2 in. x 2 1/2 in. x 3 in. Circuits, Wiring Diagrams and full constructional information, ready to fit inside your TV cabinet.

Complete Kit **65/-** Completely wired **80/-**
Both plus 2/- post and packing.

FREE We keep right up to date in building the latest circuits published in "Practical Wireless," "Wireless World," and "Radio Constructor" and we stock the components specified. Send 10d. in stamps for circuits, fully descriptive literature together with coil and coilpack leaflets, component lists, chassis drawings and templates.

ITA Band III CONVERTER KIT


Complete with all components, including power unit, for construction of an efficient Band III converter. Nothing else to buy. Circuit, wiring diagram, chassis templates and complete instructions, **£6.19.0.**

Plus 2/6 p. & p.

OSMOR RADIO PRODUCTS LTD.

Dept. PT11.

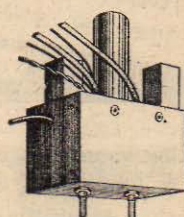418 Brighton Road, South Croydon
Surrey. Croydon 5148-9



BENTLEY ACOUSTIC CORPORATION LTD.

EXPRESS SERVICE!!!

C.O.D. ORDERS RECEIVED BY 3.30 P.M. EITHER BY LETTER, PHONE, OR WIRE, DESPATCHED SAME AFTERNOON

THE VALVE SPECIALISTS

38, CHALCOT RD., LONDON, N.W.1

PR11rose 9090

FOR ONLY 6d. EXTRA PER ORDER WE WILL INSURE YOUR VALVES AGAINST DAMAGE IN TRANSIT. ALL UNINSURED PARCELS AT CUSTOMERS' RISK.

024	6/-	6AC7	6/-	6F12	9/-	6V6G	7/-	12J5GT	4/-	4033L	12/6	CK325	6/6	EBF80	9/6	EL81	15/-	LN309	12/6	FY83	9/6	UL46	15/-	
1A3	3/-	6AG5	6/-	6F13	13/-	6V6GT	7/-	12J7GT	11/-	41MP	12/6	CV63	10/6	EBF89	9/6	EL84	10/6	LZ319	7/-	QP21	7/-	UU9	8/-	
1A5	6/-	6AG7	12/6	6F16	9/6	6X4	7/-	12K7GT	8/6	4MTEL	7/6	CV85	12/6	EC32	5/8	EL91	5/-	MM4	7/-	QP22B	12/6	UY41	8/6	
1A7	12/6	6A8	8/-	6F17	12/6	6X3GT	6/6	12K8GT	14/-	50C5	10/-	CV228	30/-	EC34	8/-	EM34	10/-	MHL4	7/6	QP25	6/6	V1507	5/-	
1C2	9/-	6AK5	5/-	6F32	10/6	6Z4/84	12/6	12Q7GT	8/6	50L6GT	8/6	D1	3/-	EC331	15/-	EM80	10/6	ML6	6/6	QS130/15	6/6	V1849A	5/-	
1H5	11/-	6AK8	7/6	6F33	12/6	6Z5	12/6	12S47	8/6	57	8/6	D42	10/6	EC332	10/6	EY51	10/6	MU14	8/6					
1L4	6/6	6AL5	6/6	6G6	6/6	630L2	15/-	12S47	7/6	58	8/6	D63	5/-	EC333	8/6	EY66	10/6	N77	5/-	R12	10/6	VMP46	15/-	
1LD3	5/-	6AM5	5/-	6H6G	2/6	7A7	12/6	12S47	7/6	61BT	12/6	D77	6/6	EC335	8/6	EZ35	6/6	N142	10/6	SD6	12/7	VP27	12/6	
1LN3	5/-	6AM9	9/-	6H6M	3/6	7B7	8/-	12S47	6/6	61SPT	15/-	DAC32	11/-	EC381	8/6	EZ40	8/-	N150	10/6	SP47	15/-	VP47	15/-	
1N5	11/-	6AQ5	7/6	6J5G	5/-	7C5	8/-	12S47	8/-	72	4/6	DAF91	7/6	EC382	7/6	EZ41	10/6	N154	9/-	SP41	3/8	VP130	7/-	
1K5	8/6	6AQ5	10/-	6J5GTG	6/6	7C6	8/-	12S47	6/6	77	8/-	DAF96	9/6	EC383	9/-	EZ80	8/6	N309	11/6	SP42	3/8	VP133	6/6	
1S5	7/6	6AT6	8/6	6J5GTM	6/6	7H7	8/-	12S47	3/6	78	8/6	DOC90	7/-	EC384	12/-	EZ81	10/6	N329	8/6	SP61	3/8	VP141	8/6	
1T4	7/6	6B4	6/-	6J6	6/6	7Q7	8/-	12S47	7/6	80	8/6	DP33	11/-	EC385	9/6	EZ82	8/6	N709	10/6	TH30C	25/-	VP133	12/6	
1U5	7/6	6B7	10/6	6J7G	6/-	7T7	8/6	12S47	6/6	82	8/6	DP91	7/-	EC391	5/6	GZ32	12/6	OC3	9/-	TP22	10/6	VT61A	5/-	
2A3	12/6	6B8G	4/-	6K7G	5/-	7Y4	8/-	12Y4	10/6	82A2	15/-	DP96	9/6	EC390	12/6	GZ34	14/-	OD3	8/-	U16	12/-	VT501	5/-	
2C26	4/-	6B8M	4/-	6K7GT	6/-	8A8	12/6	14R7	10/6	150B2	15/-	DEH3	8/6	EC392	12/6	H33	5/-	P61	3/8	U17	12/6	W76	8/-	
2D13C	7/6	6B8G	7/6	6K8G	8/-	8D3	9/-	14R7	14/-	210LF	10/6	DEH7	8/6	EC393	10/6	H33	12/6	PAD30	15/-	U25	13/6	X61	12/6	
2A2	4/6	6B8G	7/6	6L0D3	10/6	9D3	3/-	19H1	10/-	807	12/6	DR37	12/6	EC394	10/6	HL33C	7/6	PC384	12/6	U30	7/6	X66	11/6	
3A4	7/6	6B8G	8/6	6L0G	9/-	10C1	15/-	20D1	12/6	805A	10/6	DR39	10/6	EC395	10/6	HL33C	7/6	PC384	12/6	U30	7/6	X66	11/6	
2A5	7/6	6B8G	11/6	6L7M	12/6	10C2	13/-	20L1	13/6	885	10/6	DR39	10/6	EC396	10/6	HL33D	7/6	PCF80	7/6	U32	8/-	X76M	14/-	
3B7	8/6	6B8G	8/6	6L13	13/-	10F1	15/-	25L6GT	9/-	956	3/-	DK92	9/-	EP6	10/6	HL41	7/6	PCF80	7/6	U32	8/-	X76M	14/-	
3Q4	5/-	6BW7	10/-	6N7	8/-	10P9	11/6	25Z4G	9/-	1203	7/6	DK96	9/-	EP6	10/6	HL41	7/6	PCF80	7/6	U32	8/-	X76M	14/-	
3Q5GT	9/6	6BX6	10/-	6O7G	9/6	10LD3	8/6	25Z6GT	9/6	5763	12/6	DL2	15/-	EP37A	9/-									
384	7/6	6C4	7/6	6G7G	8/6	11E3	35/-	28D7	7/6	7475	7/6	DL92	7/6	EP40	12/6	HVR2A	6/6	PEN40D	10/6	U251	15/-	XYW10	6/6	
3V4	8/6	6C5	6/6	6S47	6/-	12A6	6/6	30	7/6	9002	5/6	DL94	8/6	EP41	10/6	HL33D	7/6	PCF82	11/6	U32	8/-	X76M	14/-	
5T4	8/6	6C6	6/6	6S47	6/6	12A7	8/-	30C1	12/6	9003	5/6	DL96	9/6	EP42	12/6	KT3	5/-	PEN46	6/6	U709	11/6	X86(1.5)	4/-	
5V4	10/6	6C8	8/-	6SH7	8/-	12A8	10/6	30F5	15/-	9006	6/6	DL180	10/6	EP50(A)	7/-	KT33C	10/6	PL51	13/6	U709	11/6	X86(1.5)	4/-	
5X4	10/6	6C9	12/6	6S47	8/-	12A9	10/6	30FL1	15/-	AC36P	6/6	DM70	10/6	EP50(B)	5/-	KT44	7/-	PL82	9/-					
5Y3	7/6	6C10	10/6	6S47	8/6	12A7	8/6	30L1	12/6	AC3H1	10/6	EL148	2/-	EP54	5/-	KT63	6/6	PL83	11/6	U709	11/6	X86(1.5)	4/-	
5Y4	10/6	6C10	7/6	6S47GT	8/-	12A7	7/6	30P12	13/6	DD1	15/-	EA50	2/-	EP73	10/6	KT63	6/6	PL83	11/6	U709	11/6	X86(1.5)	4/-	
5Z3	12/6	6D6	6/6	6S47GT	7/6	12A7	7/6	30P12	13/6	DD1	15/-	EA50	2/-	EP73	10/6	KT63	6/6	PL83	11/6	U709	11/6	X86(1.5)	4/-	
5Z4	3/6	6F1	15/-	6S87	7/6	12A6	6/6	30A/158M	14/60	10	7/6	AC/P4	8/-	EA76	9/6	EP80	8/6	PM12	6/6	U709	11/6	X86(1.5)	4/-	
6A3	10/6	6F6G	6/6	6U4GT	14/-	12B6	10/-	30-AF4	7/6	AC3H1	10/6	EL148	2/-	EP73	10/6	KT63	6/6	PL83	11/6	U709	11/6	X86(1.5)	4/-	
6A7	8/-	6F7	10/6	6U5G	7/6	12E1	30/-	35/12	6/6	ATP4	8/6	EA76	9/6	EP80	8/6	PM12	6/6	U709	11/6	U709	11/6	X86(1.5)	4/-	
6A8	10/6	6F8	10/6	6U7	8/6	12H6M	3/-	35A16T	9/-	B309	9/-	EB41	8/6	EP92	5/6									
								35Z3	10/6	B329	10/6	EB91	6/6	EL32	5/6									
								35Z4GT	8/-	BL63	7/6	EB93	7/6	EL41	10/6									
								35Z5GT	8/6	CK323	6/6	EB94	10/-	EL42	11/-									

Terms of business:—Cash with order or C.O.D. only. Orders below £3 or more sent post/packing free. Orders below £3 please add 6d. per valve. C.O.D. orders:—Minimum fee, including post and packing, 5/-; £3-£9.99 are for personal shoppers. Mon.-Fri. 9.30-5.30. Sat. 9.30-1 p.m.

We can supply any valve not listed. Phone or send 21d. stamp for quotation.

All valves new, boxed, tax paid, and subject to makers' guarantee. First grade goods only, no seconds or rejects. All orders received by first post despatched same day. S.A.E. for free complete list, with full terms of business.

A Projection TV Improvement

AVOIDING DISTORTION WHEN SCREEN AND OPTICAL UNIT ARE NOT PARALLEL

By A. M. St. Clair

PROJECTION television, once hailed as the answer to the simultaneous achievement of economy and big pictures, seems to be on the wane. Yet many serious writers are agreed that if colour is to achieve popularity it will be through a projection system. Certainly the cost of a 21in. colour tube must remain for many years a prohibitive factor. It therefore behoves the amateur, so often the prime mover, all too often later forgotten in new developments, to turn his attention to certain aspects of projection television.


The chief reason for the decline of projection systems is the rather unsatisfactory nature of a rear-projection picture. Even with the best screens, it is highly directional; even with the best optical arrangements, it is appreciably less brilliant than a directly-viewed picture on a good modern aluminised tube. The second objection means that really satisfactory daylight viewing is rarely achieved; the first sadly attenuates the advantages of any big picture set-up, in that it restricts the number of persons who can view simultaneously to those who may conveniently be seated more or less directly in front of the screen.

Neither of these disadvantages holds for front-projection systems. With a well-designed screen, less

mirror, must lie on the line perpendicular to the centre of the screen, thereby occupying so to speak the best seat in the house. It would be very pleasant if we could arrange things so that the front of the screen was unimpeded; so that viewers could move their heads, or walk about the room freely, without fear of interrupting the picture, or losing sight of it. Even perhaps if we could arrange a front-projection receiver with screen complete in a cabinet of reasonable size—a thing not possible in the ordinary way, precluded by the necessity of having some part of the optical system directly in front of the screen.


A Solution

All of these things can be achieved by a comparatively simple means. Look at Fig. 1. Here we have a projector—television or any other kind, the same laws of optics apply to magic lanterns—on the floor, throwing obliquely on to a vertical screen placed quite close to it. The outlines of a rectangular picture would be distorted into the shape shown in Fig. 2. This is a trapezium, and the effect is a form of trapezium distortion; to distinguish it from the electronic (C.R.T.) effect of that name, however, it is called "keystone effect." In ordinary cinema practice, and in very large-screen television, where both the screen and the projector are above the heads of the

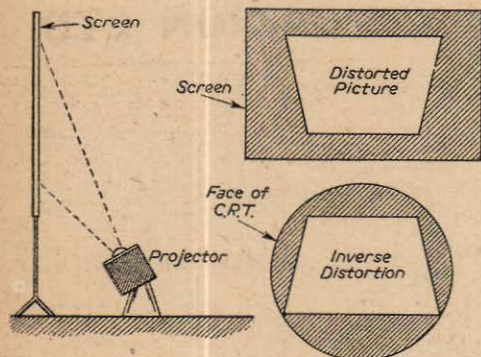

Figs. 1, 2 and 3.—A screen and projector at angle to each other and the resultant distorted picture.

light is lost by reflection than by transmission through a screen in the other method. Moreover, the picture is equally visible from all angles, and even the "hot-spot," so annoying to the best-placed viewers in a rear-projection set, is eliminated. Of course, these advantages are well-known to those whose business it is to provide really large-scale television for sizeable audiences; and I know of several amateurs who have established such apparatus. There are, however, two snags in front-projection for domestic use. In the first place, it means that a screen has to be set up, a separate article from the receiver, and correctly aligned each time that the set is brought into use. And it means that either the projector itself, or a

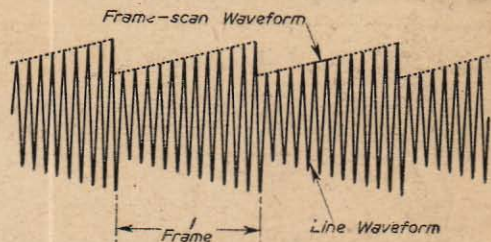

Number of lines greatly reduced to facilitate presentation.

Fig. 4.—Waveform of frame scan.

audience and the "throw" is a long one, it does not assume serious proportions, and is cured, or partially cured, by tilting the screen a little. Since, for our purposes, it would be desirable to have the projector very close to the plane of the screen, either above or below, and since in these conditions the tilt required would make the picture virtually invisible, we must seek other means of correction.

Consider what would happen if, instead of starting with a rectangular picture, we projected a *reverse* trapezium. It would show on the screen as a rectangle. So what we want on the end of our projection tube is a picture like Fig. 3.

Now think what this means in terms of the scanning waveforms, since it is these which determine the shape of the raster. It implies that each successive line must have a slightly greater amplitude than its

predecessor throughout the time of a frame scan. This gives us a form as in Fig. 4, from which we see that the output of the line timebase has been modulated by that of the frame timebase. How to achieve this?

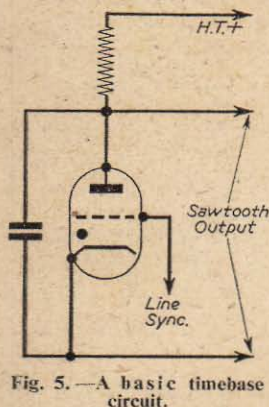


Fig. 5.—A basic timebase circuit.



Fig. 7.—Condenser waveform of Fig. 6.

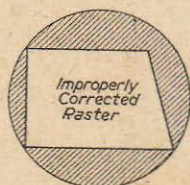


Fig. 8.—Raster shape produced by waveform of Fig. 7.

timebase really functions. In what follows, therefore, I shall use, for simplicity, the basic timebase of Fig. 5. It is not suggested that this timebase be actually used; it is serving as a symbol, for which the experimenter should substitute his own line timebase circuit.

The amplitude of scan developed depends on the rate of charge between successive sync. impulses. This in turn depends upon the applied voltage. Suppose we vary the applied voltage at frame frequency as in Fig. 6. Here, the condenser will charge up to a higher voltage each line, as in Fig. 7. But it will return to the same reference voltage each time, also as in Fig. 7. This would give the raster shape of Fig. 8. To avoid this, we must introduce some frame scan voltage between the condenser and the

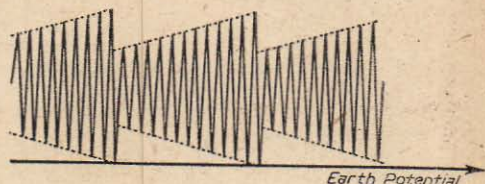


Fig. 9.—Waveform resulting from Fig. 10 circuit.

Circuits

Before we get down to circuitry, a brief word on timebases, as they are dealt with in this article. It will be noticed that in the above discussion no distinction has been drawn between current and voltage waveforms. Fundamentally, a timebase consists of a device for charging a condenser to a small fraction of the applied voltage, or of otherwise ensuring that its charging-rate is linear, and of discharging it very rapidly at the end of certain predetermined intervals. It produces a saw-tooth voltage. This voltage often undergoes modifications to enable a saw-tooth current to pass through a scanning-coil, but in the last analysis all timebases start off by producing a saw-tooth voltage. Inevitably, there are exceptions, or apparent exceptions. Timebases where the condenser is allowed to charge well beyond the point of linearity.

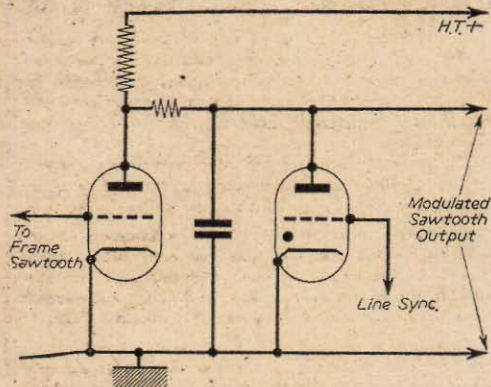


Fig. 6.—A frame timebase circuit.

Timebases where the compression of the circuitry is such that it obscures the fundamentals. But what is said here is true of all normal timebases, and its application in a particular instance requires merely that the experimenter should understand how his

earth line. This is done as in Fig. 9. The exact amount depends upon the ratio of the total H.T. at X to the normal amplitude of the condenser swing. If the condenser normally is allowed to charge to one-fifth of the H.T. voltage, for example, the signal at A should be one-fifth of that at B. The variation in the upwards excursions of the condenser voltage

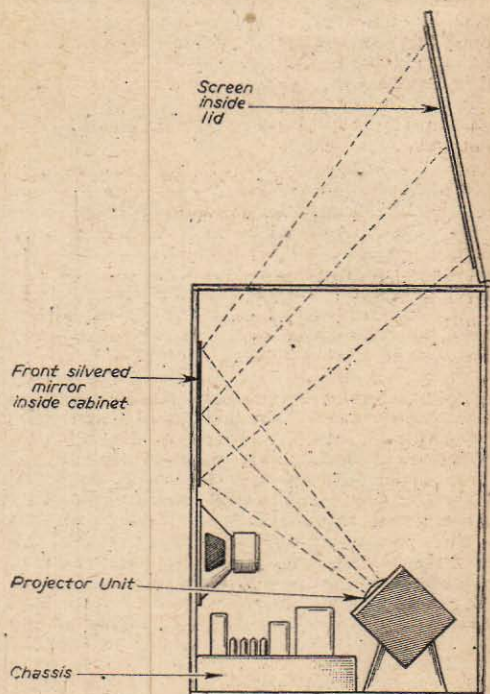


Fig. 11.—A layout to make use of the ideas expressed here.

will then be balanced by exactly opposite variations in the downwards excursions, giving the waveform of Fig. 10. The gain control in Fig. 10 enables us to adjust the slopes of the sides of the resultant raster, so that we can match it exactly to Fig. 3.

Now, we can project from an angle as steep, within reason, as we like. Within reason? Two things to note! The steeper the angle of projection, the greater the difficulty of obtaining satisfactory optical focus over the whole picture. And the shortened lines necessarily offer somewhat inferior definition to the

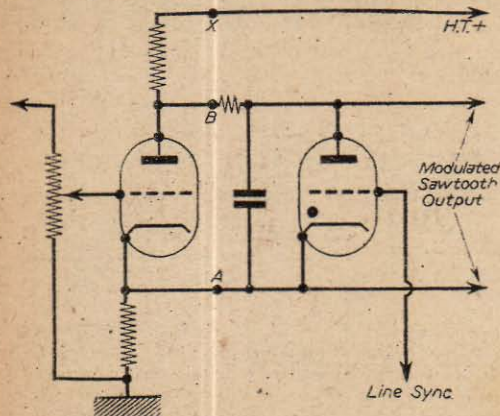


Fig. 10. — Gain control fitted to adjust slopes of sides.

full scan. A slightly tilted screen alleviates both effects simultaneously; under such conditions, an overall ratio of longest to shortest line of about 1.5:1 can be used. Even in a separate-screen set-up, this will enable the projector to be placed really close to the screen, and well below it, giving a lay-out vastly superior in convenience. It can also lead to the arrangement of Fig. 11.

This arrangement, which is given in rudimentary form, enables us to have front projection in a single-unit construction, with the screen on the inside of the lid of a radiogram-sized cabinet—a thing hitherto virtually impossible for front-projection systems. It has been tested by the author using the usual Mullard projection tube and Schmidt optical system, when the picture, of 36in. diagonal, gave really good daylight viewing; and also projecting a 21in. diagonal picture (equivalent to a 21in. tube in size), from a G.E.C. 9in. direct viewing tube, using as the optical system only an old, chipped two-part lens, diameter and focal length approximately 8in. and 20in., respectively. Its original purpose is unknown to me: it was housed in a brass tube which had the maker's name engraved in fine copperplate, followed by "Paris, 1893." It cost me 25s., and I feel that many similar "treasures" must remain to be found in local "junk shops." In this case, though the tube was given a 20 per cent. overvoltage (E.H.T.—heater volts were kept normal), viewing was satisfactory only in dim ambient lighting. It was, however, not notably inferior to many rear-projection systems of much greater complexity and cost.

Hints

A few practical points. It is difficult to modulate a line T.B. output stage. It is not impossible, but it

should be undertaken only by experimenters having an adequate knowledge of the power- and voltage-handling capacities of the preceding stage. It is better to modulate the line oscillator. In this case, it must be borne in mind that the compensating voltage developed at A, Fig. 10, must be used in such a fashion as to make the final raster symmetrical. This may mean removing true earth from the entire timebase, or using a voltage negative to earth to supply the modulator cathode, or applying the compensating voltage, perhaps suitably shaped by a network, between the bottom end of the line coil and earth. The appropriate method in each case will be dictated by the actual timebase circuitry. Any good home cine screen is suitable for these arrangements, but the best screen is a sheet of finely sand-blasted aluminium. If the folded optical system of Fig. 11, is attempted, a front-silvered mirror should be used. This, of course, is true of all mirrors used in any projection system, since rear-silvering gives "ghosts," and results in a loss of light. If it is felt that it is unsatisfactory to leave the contents of the cabinet in Fig. 11 open to the air when the lid is raised, a sheet of plate-glass may be used as a top-board. This will result in some slight loss of brilliance, and will have to be kept very clean; but it can give a good appearance, if the "works" beneath are suitably boxed, and if the controls are mounted through the glass in the corners, where they will not impede the light from the projector.

It is not claimed that the above notes exhaust the subject. Rather, they are intended as a guide to the experimenter. An idea is suggested, that of the trapezoidal raster, which can improve the performance of, and remove some of the snags from, front projection systems; and a method of realising it, found workable by the author, is outlined. It is not to be doubted that other, perhaps better or simpler, methods exist; and it is hoped that this article may assist others to their discovery.

PRACTICAL WIRELESS JUNE ISSUE NOW ON SALE

PRICE 1s. 3d.

An Electronic Timer and an Amateur Communications Receiver form the main constructional features of our companion paper **PRACTICAL WIRELESS** which is now on sale. The Timer will enable any switching operation to be carried out where a lapse of time has to be included, such as in photographic enlarging, opening or closing a door, etc. The Amateur Communications Receiver is an 8-valve plus rectifier set with multiple coil switching.

In addition to the above, the concluding article on a Hi-Fi Tape Recorder also appears, whilst there are two exhibition reviews also included in this issue. The first deals with the Radio Components Show, and the second with the Audio Fair.

Also appearing in the issue is the first article dealing with Starting a Service Department; and other articles deal with Short Wave Transposed Doublet Aerials; Transformers for Transistors; the R.1155 Communications Receiver; Transistor Circuit Applications; Using a "High Cycle" Transformer on 50 c/s Mains; and the usual features, whilst the Transmitting Article deals with Further Pointers on the VFO.

THIS instrument enables EHT voltages of up to 20 kV or more to be measured directly and quickly. It consists of a calibrated spark gap, which can be used for high-voltage measurement because the voltage required to spark across a gap of given length is virtually constant for the particular gap. (The required voltage is actually affected by changes in the atmospheric pressure and humidity, but for normal use these effects can be neglected.) In use, the gap is first opened up to its maximum value and the high voltage connected across it. The gap length is then slowly reduced until a spark occurs, at which point the length is read off and the value of the voltage determined from the instrument's calibration chart.

The use of a calibrated spark gap in this way is not new, of course, but this particular instrument is so designed that it can easily be made by the amateur using only simple hand tools and yet is still capable of good accuracy. It does not involve the use of a lathe or other precision work and the design can, without difficulty, be modified to use whatever materials happen to be in the scrap box.

As can be clearly seen from the illustrations, the spark gap itself consists of two brass door-knobs, mounted upon parts of their normal square-section operating spindle, but any similar spherical or nearly-spherical metal parts can be substituted, providing they are free from dents or projections near the middle. The diameter is not critical: in the unit being described, the knobs are 1 $\frac{1}{4}$ in. in diameter. The main framework of the voltmeter is made from $\frac{1}{4}$ in. thick "bakelite" sheet and its detailed design is a matter of taste. So long as a rigid mounting for the two halves of the gap is provided, the shape of the

Making a Kilo-Voltmeter

A CALIBRATED SPARK-GAP VOLTMETER
WHICH CAN BE MADE BY THE
AMATEUR

By A. C. Kay

or both ends of the bracket will help to correct the error. At one end of its travel, the moving knob (or "sphere," to give it the accepted term when talking of such spark gaps) is in contact with the fixed sphere, and less than $\frac{1}{16}$ in. of movement away from this position is needed.

We now come to the part of the instrument which controls the length of the gap. A short pillar is fixed to the moving spindle, projecting sideways from it for a distance of about $\frac{1}{4}$ in. This is drilled and tapped 6 B.A. in a direction parallel to the axis of the spindle, and one end of the operating rod is screwed through this hole. The rod can be a piece of 6 B.A. studding about 2 $\frac{1}{2}$ in. long or a suitably modified long 6 B.A. screw, and the back end of the rod passes through a hole in a substantial metal bracket fixed to the framework and so placed that the rod is parallel to the spindle. Lock-nuts are placed on the rod on the front side of the bracket, and it is a slight refinement in the design if the part of the rod passing through the hole can be left unthreaded. A compression spring slipped over the main spindle tends to open the gap and causes the lock-nuts on the

control rod to be kept in contact with the bracket: this completely eliminates back-lash when the voltmeter is in use and greatly contributes to its accuracy. The spring could be replaced by a rubber band stretched between the pillar on the spindle and the bracket supporting the operating rod, but the rubber would naturally not be so durable. A knob is later fixed to the back end of the operating rod, and turning this causes the gap to open or close; the knob, however, is not placed finally in position until the circular scale has been added.

The remainder of the instrument consists of the two scales, one linear (straight) and the other circular, which are so arranged that one complete rotation of the circular scale equals one division of the linear scale. They are thus similar in use to those on an ordinary micrometer. The linear scale is about $\frac{1}{4}$ in. long and is fixed to the framework so that it is parallel to the moving spindle and level with its upper surface. Each of its divisions is equal to the pitch of the 6 B.A. thread on the operating rod (i.e., the distance between successive threads). To mark it out, the simplest way

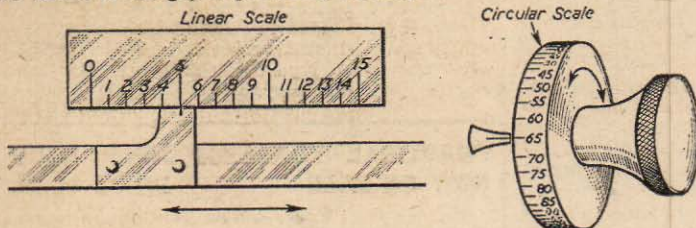



Fig. 1.—The two scales for calibration purposes.

remainder is not important, but the "pistol grip" handle shown has been found to be very convenient in use. The pistol grip can be made from a separate piece of the insulating material and bolted to the main body, if desired.

Construction

One of the door-knobs is rigidly fixed to the front of the main framework and electrically connected to the probe. The knob may most easily be fixed by means of a short length of its own spindle, although the version shown in the photograph uses a round-section rod for this purpose, since originally this rod was extended forwards to form the probe itself. The reason for subsequently providing a separate probe will be explained later.

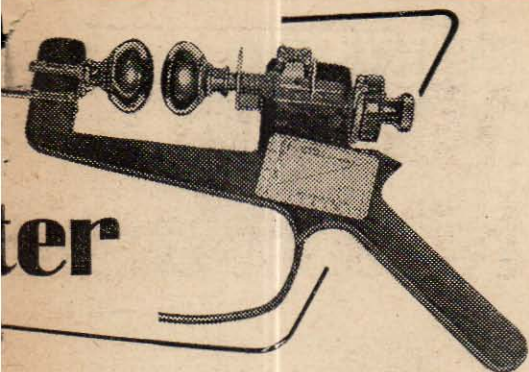The second door-knob is fixed to a longer piece of its own spindle, which slides in two square holes in a metal bracket fixed to the back of the framework. These holes should be carefully cut to have the least possible side play, but if they are accidentally made a little too large, judicious twisting or bending of one



is to press a 6 B.A. screw lengthways on to a piece of paper so that the threads make a series of marks on it; with a little care, the marks can then be used to mark out the actual scale. This can be made from a small piece of aluminium sheet, and if it is first rubbed lightly with a very fine emery cloth, it will be found that the scale can be drawn on it with Indian ink, using a mapping pen or similar fine nib. It is convenient to lengthen slightly and number the fifth and tenth divisions for ease of reading. A scale 15 divisions long should be ample.

its rim which are numbered 00, 05, 10, 15, 20 and so on up to 95, as indicated in Fig. 1. To set these out, draw a line about 3in. long on a piece of paper and then through the centre of this line draw a series of other lines like the spokes of a wheel, having angles of 18 deg. between them. A protractor will simplify this part of the job. Place the centre of the cap over the point where these lines intersect and mark the scale divisions on the rim immediately over each of the lines.

A small pointer is fixed to the bracket through which the operating rod passes and, as already described, the scale is placed on the rod adjacent to the pointer and fixed firmly to the rod by means of a nut on either side. It is important that the angular position of the circular scale should be such that, when the pointer of the linear scale is opposite one of the scale divisions, the pointer of the circular scale should be opposite the "00" mark.

Finally, the means for connecting the two sides of the spark gap to the high-voltage point are added. A flexible lead is attached, by means of a solder tag, to a convenient fixing screw of the metal bracket which supports the moving sphere, and the other end of the lead is equipped with a crocodile clip. This is always connected to the earthy side of the voltage being measured, a point which is important if the operator is to avoid the danger of contact with the "hot" side of the high voltage. A metal rod about

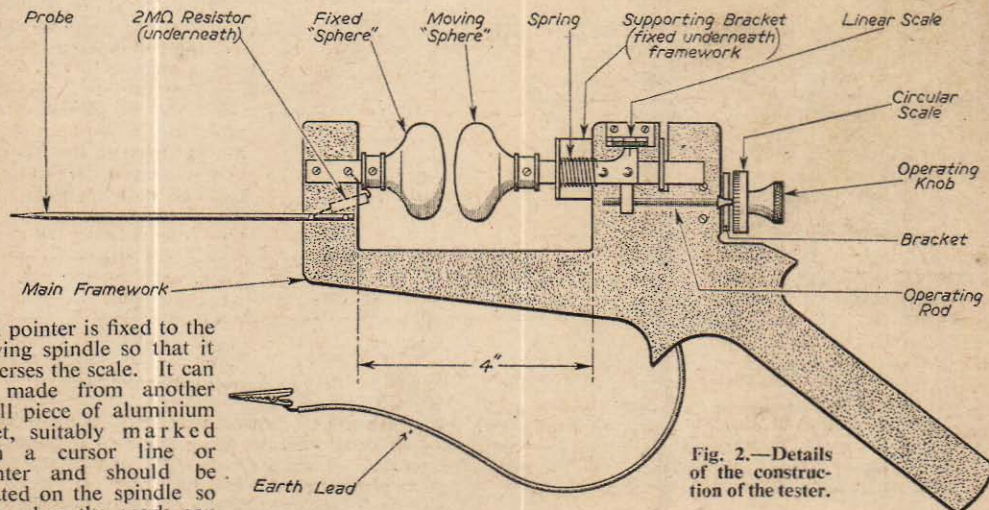


Fig. 2.—Details of the construction of the tester.

A pointer is fixed to the moving spindle so that it traverses the scale. It can be made from another small piece of aluminium sheet, suitably marked with a cursor line or pointer and should be located on the spindle so that, when the spark gap is closed, the pointer is at or near to the zero end of the scale. The exact position is unimportant, since the scale position is quite arbitrary.

The circular scale is made from the metal cap from a bottle of a well-known make of ink. Almost any circular piece of material, metal or otherwise, could be used, but the ink-bottle cap has been used because it has a fairly wide and reasonably flat rim and can be easily marked with the scale divisions by scratching away with a scribe the paint covering. A hole is drilled in the exact centre to enable the scale, when completed, to be placed on the control rod next to the operating knob and fixed very firmly in position by lock nuts.

The scale is marked with 20 equal divisions round

5in. long, with one end tapered to form a probe, is mounted at the front of the main framework close to the fixed sphere and connected to it via resistor of about 2 MΩ. The resistor is not essential and the probe may be connected directly to the fixed sphere, but its inclusion serves to limit the current surge when the gap sparks over. It has a negligible effect on the calibration of the instrument.

Reading the Scales

Reading the scales is very easy. Simply read the number on the linear scale against the nearest scale division on the left of the pointer. In the example shown in the illustration (Fig. 1) this is 4. Add to this

(Continued on page 540)

Oscillator Radiation

LIMITS OF RADIATION FROM TELEVISION AND V.H.F. SETS AND THE METHOD OF MEASUREMENT

IN 1954, B.R.E.M.A. announced limits which had been adopted by the Association for oscillator radiation from television and V.H.F. receivers, and details were given of the method of measurement. The limits were set out under three headings: (i) direct radiation measured at a distance of 10 m., (ii) aerial terminal voltage, and (iii) oscillator voltage appearing at the mains terminals.

Since then, considerable work has been carried out, both in this country and internationally, on the standardisation of a method of measurement having special regard to (a) simple site and apparatus requirements, (b) simplicity of measurement, and (c) repeatability of results, within reasonable limits, at different sites. As a result of this work, a method of measurement of the total free space radiation at 3 metres has been evolved by the International Electrotechnical Commission and it is anticipated that, with minor amendments, this will be universally adopted.

The method is sufficiently compact in its requirements to permit the apparatus to be set up on, for example, a flat roof. Its features have been extensively considered by the appropriate technical committees of B.R.E.M.A. with the result that recommendations were submitted that this method should now supersede the previous method of measurement at 10 metres; although the former aerial terminal voltage measurement is no longer laid down as part of the measurement, it should be noted as an additional measurement which is useful to designers, and details are given in Appendix "A".

At the same time, limits of radiation were reviewed and recommendations were made as under:

In the range over 30 Mc/s up to	41 Mc/s, not exceeding	200 μ V/m
" " " " "	41 " " "	68 " " "
" " " " "	68 " " "	100 " " "
" " " " "	100 " " "	174 " " "
" " " " "	174 " " "	216 " " "
" " " " "	216 " " "	250 " " "
" " " " "	250 " " "	1,000 " " "

* A television receiver tuned to Channel 6 and using the standard I.F. with oscillator high is not required to meet the "in-band" limit, but must not exceed 1 mV/m.

After making allowances for the differences in methods, the amount of "in-band" radiation in Band I is unchanged from the former limit, but the "out-of-band" limit up to 100 Mc/s has been slightly relaxed and new limits have been established for the range 100-250 Mc/s. The upper frequency limit for mains terminal voltage measurement has been fixed at 100 Mc/s and the limit remains 500 μ V into the

specified network, or 1.5 m μ W, when measured as set out in Appendix "B".

It is hoped that both these recommendations will be widely accepted. With the development of the V.H.F. bands for television and F.M. sound broadcasting, the whole question of mutual interference between receivers is attaining an increasing significance, and it is considered essential that these limits should be met.

It is anticipated that both the method and limits will be incorporated virtually unchanged in the revised British Standard 905 which, it is hoped, will be published later this year.

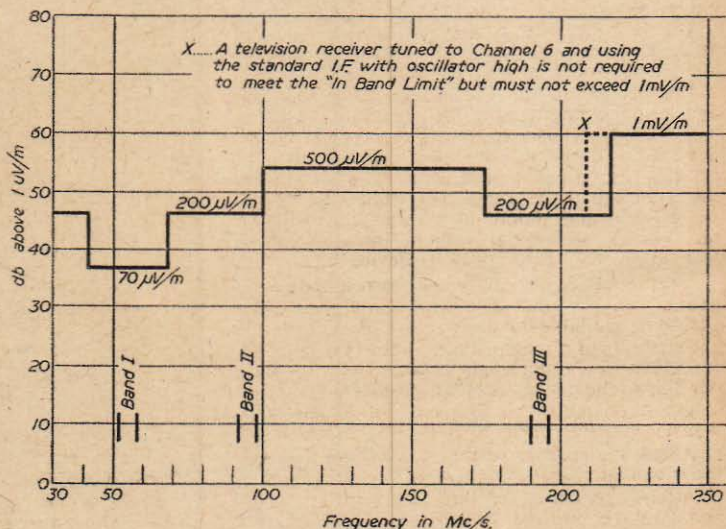


Fig. 1.—Limits for R.F. oscillator radiation.

This method of measurement and the same limits are also applicable to radiation at I.F. harmonic frequencies, which have been found to be troublesome in particular with some V.H.F./F.M. receivers.

Details of the procedure for measurement at 3 metres follow and have been prepared for convenience, prior to the publication of the official British Standard.

Site Requirement

The measuring site should be flat and free from reflecting objects. No extraneous metal objects having a dimension in excess of 15 cms. should be in the vicinity of the receiver under test or of the field strength meter aerial.

Setting-up and Measuring Procedure.

(1) Set up the apparatus as shown in Fig. 2, centrally on a wire mesh ground screen of dimensions 9 x 6 metres. All structures and supports should be

non-conducting material. The structure on which the receiver under test is mounted should be rotatable from a remote point through 360 deg. and the horizontal dipole should be parallel to the face of the receiver and rotatable through 180 deg. relative to it, so as to enable the phase relationship between chassis and aerial radiation to be reversed. This dipole should be 2.25 m. (88 in.) long for radiation measurements on television receivers, and 1.5 m. (59 in.) long for measurements on V.H.F./F.M. receivers, the diameter of the rod being $\frac{1}{2}$ in. in both cases.

The dipole for the field strength meter should be capable of being set either vertically or horizontally, and remotely raised or lowered so that its centre is between 1 and 4 metres from the ground plane. The length of the dipole should be adjustable to resonate at the frequency being measured or 80 Mc/s, whichever is the higher.

The measuring equipment and any unavoidable large extraneous objects should be disposed behind either the receiver or field strength meter aeriels.

The receiver should be so placed that its oscillator valve is immediately under the centre of its aerial and 1 m. above the ground plane.

The feeder to be connected between aerial and receiver should be of the type and characteristic impedance for which the receiver has been designed. If the receiver has been designed to operate with either a co-axial or balanced feeder, the latter should be used. The feeder should not be screened and should be directly connected to the receiver and aerial without inter-connection of a transformer, balun or other device.

Additional lengths of feeder corresponding to quarter wavelengths at 67, 100 and 200 Mc/s should be available for stage 5.

- (2) Set the field strength meter dipole in the horizontal position at the height shown in Fig. 3 corresponding to the receiver oscillator frequency, with its length resonant to this frequency or to 80 Mc/s, whichever is the higher.
- (3) Rotate the receiver to the position which gives the maximum reading on the field strength meter.
- (4) Adjust the height of the field strength meter aerial to the position which gives the maximum reading. Note this reading.

- (5) Insert the additional length of feeder (mentioned at the end of (1) above) nearest to the frequency in use in the position shown in Fig. 2, and repeat stages 3 and 4.
- (6) Rotate the receiver dipole through 180 deg.

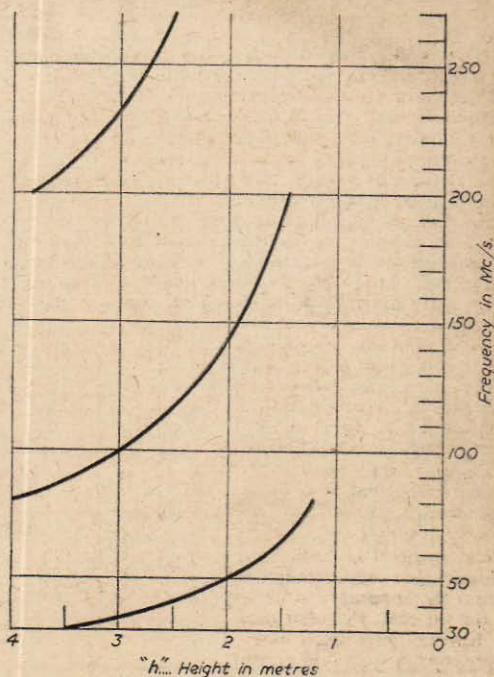


Fig. 3. — Field strength meter aerial height during receiver orientation.

- relative to the receiver and repeat stages 3, 4 and 5.
- (7) Change the field strength meter dipole to its vertical position and repeat stages 3, 4, 5 and 6.
- (8) If the receiver is fitted with an internal aerial, remove the main receiver dipole and repeat stages 3, 4 and 7 with the internal aerial connected. If

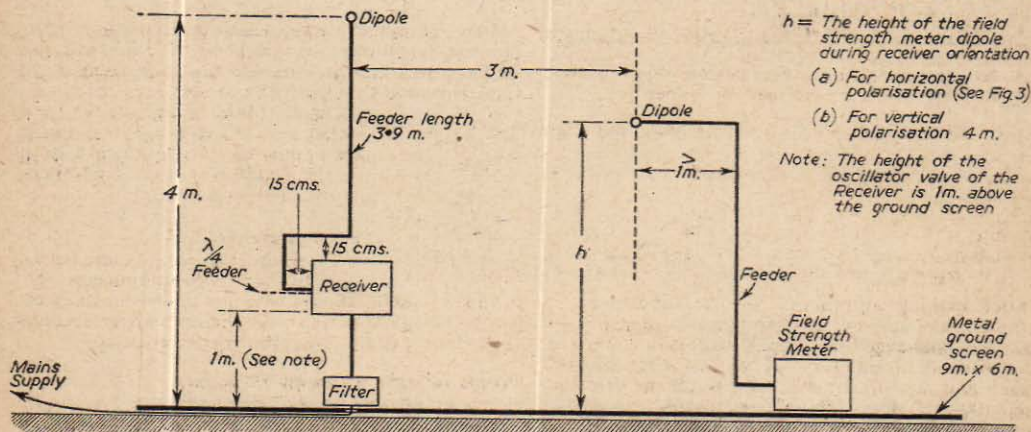


Fig. 2. — Measurement of R.F. oscillator radiation.

the internal aerial has reversible connections, these measurements should be carried out with the connections in both positions.

- (9) All the above measurements should be repeated on each channel in the case of television receivers, or at points near the bottom, middle and top of the tuning range of a V.H.F./F.M. receiver.
- (10) The highest reading obtained is the radiation figure for the receiver and should not exceed the value shown in Fig. 1.

Appendix "A"

Measurement of Aerial Terminal Voltage

Useful design information may be obtained in the laboratory by making a measurement of the symmetrical component of the aerial terminal voltage across a load equal to the nominal input impedance of the receiver.

The receiver under test is connected through a short length of feeder of the appropriate type to a well-screened measuring set that is used as a selective voltmeter. Where the input impedance of the measuring receiver differs from the required value, a matching pad must be inserted to terminate the feeder and provide the correct load. When a balanced system is measured using a measuring receiver having an unbalanced input or vice-versa, a balun must be used to suppress possible asymmetric currents on the feeder.

The measuring set is tuned to the frequency it is desired to measure and adjusted to give a suitable reference output. The receiver under test is then disconnected and replaced by a signal generator, which is adjusted to give a similar reading on the measuring set. The output of the signal generator will be equivalent to the aerial terminal voltage of the receiver under test.


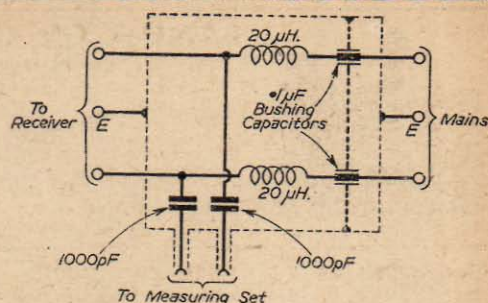


Fig. 4. — Isolating unit.

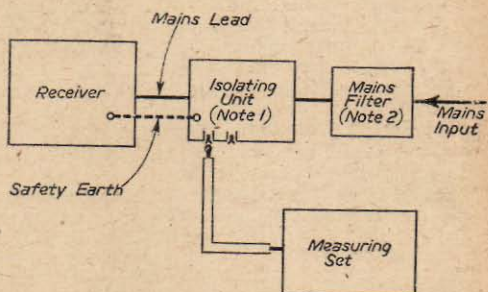

Note 1.—A measurement is made of the interference voltage existing between each Mains lead and earth.

Note 2.—A Mains filter is required when the ambient noise level is high.

Fig. 5. — Measurement of mains terminal interference voltage.

Frequency Range	Aerial Terminal Voltage	
	Across 75-ohm load	Across 300-ohm load
30–40 Mc/s	2,500 μ V	5,000 μ V
41–68 Mc/s	350 μ V	700 μ V
68–100 Mc/s	750 μ V	1,500 μ V
100–174 Mc/s	1,750 μ V	3,500 μ V
174–216 Mc/s	*1,000 μ V	*2,000 μ V
216–250 Mc/s	5,000 μ V	10,000 μ V

* A television receiver tuned to Channel 6 and using the standard I.F. with oscillator high is not required to meet the in-band limits, but it should not exceed the values for the frequency range 216–250 Mc/s.

It should be noted that the figures given in the table above will not be valid if the receiver under test is grossly mis-matched when connected to its nominal load impedance.

Appendix "B"

Mains-borne

Limit: 500 μ V or 1.5 mV/W

The measuring technique is that described in B.S.727 (Section 4). Essentially, this consists of measuring the terminal voltage across a standard network or isolating unit (Fig. 4). The primary object of the isolating unit is to ensure that the effective value of the measuring impedance is not materially affected by the impedance of the actual supply mains in use. See Fig. 5.

AN AUTOMATIC TV CLOCK

(Concluded from page 508)

The inductance is placed in series with the mains supply to the set and is such that it drops from 6 to 12 volts at the current drawn by the set. The exact figure is not unduly critical so long as it is within the working limits of the relay. A suitable component was arrived at by experiment. Initially, a resistor was tried, but apart from the disadvantage of it getting hot, it was found impossible, for some unapparent reason, to make the relay operate satisfactorily. Fig. 4 shows an experimental circuit made up of the actual components which will be used in the final unit, and this can be built up on the bench for testing out various trial values of inductance. It is worth while experimenting with some odd low impedance surplus chokes in the hopes of finding a suitable value. Otherwise about 100 turns of fairly thick wire can be wound on a small core (e.g., from an old output transformer) as a starting point. A 60 to 100-watt electric light bulb provides a suitable load.

As a relay coil takes a very small current, the rectifier can be rated at 0.25 amps or less and need not be a large item. The relay itself should be of the low voltage type as it is undesirable to drop too many volts in the supply to the set.

The bell which was *in situ* when the box was purchased is rated at about 75 volts A.C., the current being provided by a hand generator.

The 50 μ F capacitor was found to be essential to avoid the relay buzzing.

BAND 3 T/V CONVERTER—185 Mc/s-199 Mc/s

Suitable for London, Birmingham and Northern Transmissions

£2-5-0 post free.

A highly successful unit (W/World circuit), incorporating variable oscillator tuning, Midget BVA valves, etc. Chassis size 7 x 4 x 2 1/2 in. Thousands already in use. Suitable for most types of T/V sets. TRF or Superhet. Kit of parts 45/- . Blueprint 1/6, Power pack kit 30/- . Switch kit (Band 1—Band 3 Ac. switching)

6-6—all Post free. Wiring and aligning of above 20/- extra. Full range of Band 3 aerials in stock. Adaptors from 7.6 per set. Indoor or outdoor dipoles with 5 yds. cable 13.9. Band 1—Band 3 cross-over filter unit, 7.6. Variable attenuators 6 db—36 db, 6.9. BBC Break-through Filter, suitable for BBC pattern rejection, 8.6.

Volume Controls

Log. ratios, 10,000 ohms —2 Megohms. Long spindles. 1 year guarantee. Midget Ediswan type. No Sw. S.P. Sw. D.P. Sw. 3-4-4.9. Linear Ratio, 10,000 ohms—2 Megohms. Less switch, 4/- each. Coax plugs, 1.2. Coax sockets 1-. Couplers 1.3. Outlet boxes, 4/8. TWIN FEEDER, 80 ohms, 8d. yd.; 300 ohms, 8d. yd. TRIMMERS, Ceramic, 4 pf.—70 pf., 9d. 100 pf., 150 pf., 1.3; 250 pf., 1.6; 600 pf., 1.9. PHILIPS Beehive Type—2 to 8 pf. or 3 to 30 pf., 1.3 each. RESISTORS.—Pref. values 10 ohms to megohms.

80 ohm COAX

STANDARD 1/4 in. diam. Polythene insulated. GRADE "A" ONLY

8d. yd.

SPECIAL — Semi-air spaced polythene. 80 ohm. Coax 1/4 in. diam. Stranded core. Losses cut 50%.

9d. yd.

3w. LAB. COLVERN, etc. Standard Size Pots, 2 1/2 in. Spindles. High Grade. All Values, 100 ohms to 50 K, 5/6; 100 K, 6/6. W/W EXT. SPEAKER CONTROL 10d. 3/-.

CARBON

30% Type, 1 w., 3d.; 1 w., 5d.; 1 w., 8d.; 2 w., 9d.; 10% Type, 1 w., 9d.; 1 w., 1/-; 5% Hi-Stab. 1 w., 2/-.

WIRE WOUND

25 ohms—1.3; 10,000 1.6; 100 ohms 2-; 15,000 1.9; 25,000 2.3

WIRE-WOUND POTS

Pre-Set Min. T.V. Type. Knurled Slotted Knob. All values 25 ohms to 30 K, 3/- ea. 50 K, 4/-.

CONDENSERS

—Mica or S. Mica. All pref. values, 3 pf. to 650 pf., 6d. ea. Ceramic types, 2.2 pf.—5,000 pf. as available, 9d. each. Tubulars, 450 v., Hunts and T.C.C., .0005, .001, .005, .01 and 1, 350 v., 9d. .02, .05, 1, 500 v., Hunts, T.C.C., 1/- . 25 Hunts, 1.6. 5 Hunts, 1.9. 1, 1,500 v. T.C.C. (Simplex), 3/6. .001 6 kV. T.C.C., 5/6. .001 20 kV. T.C.C., 9/6.

SILVER MICA CONDENSERS

10% 5 pf. to 500 pf., 1/- . 600 pf. to 3,600 pf., 1.3. 1% 1.5 pf. to 500 pf., 1.8. 515 pf. to 3,600 pf., 2/-.

ALUMINUM CHASSIS


—18 s.w.g. Plain, undrilled, folded 4 sides and riveted corners lattice fixing holes. Strong and soundly constructed with 2 1/2 in. sides, 7 in. x 4 in., 4/6; 9 in. x 6 in., 5/9; 11 in. x 7 in., 6/9; 13 in. x 9 in., 8/6; 14 in. x 11 in., 10/6.

SOLO SOLDERING IRONS

(200-220 v. or 230-250 v.), 25 watt instrument type, 22/6; 65 watt Pencil Bit Type, 26/8; 65 watt Oval Bit Type, 25/- . Comprehensive stock of spares available.


RECORD PLAYER CABINET

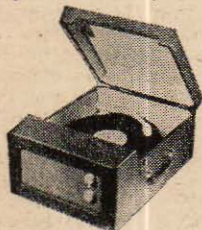Cabinet size, 18 1/2 x 13 1/2 x 11 in. 8 in., with uncut motor board 13 1/2 x 12 1/2 in., 23.3.0, carr. 3/6. 2 valve amplifier to fit above, ready wired and tested with 6 in. speaker, 28.12.6, carr. 2/6. Record changers available to suit this cabinet.



RECORD PLAYER CABINET

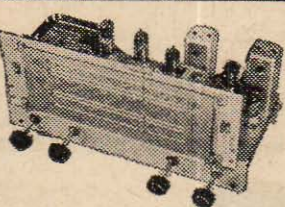Cabinet size, 18 1/2 x 13 1/2 x 11 in. 8 in., with uncut motor board 13 1/2 x 12 1/2 in., 23.3.0, carr. 3/6. 2 valve amplifier to fit above, ready wired and tested with 6 in. speaker, 28.12.6, carr. 2/6. Record changers available to suit this cabinet.



ALL WAVE RADIOGRAM CHASSIS

3 WAVEBANDS 5 VALVES S.W. 16 m.—30 m. LATEST MIDGET M.W. 200 m.—350 m. BVA L.W. 500 m.—2,600 m. SERIES

Brand new and guar. A.C. 200/250 v. 4 pos. W.C. sw. Short-Medium-Long-Gram. P.U. socket. High Q dust core coils. Latest circuit technique, delayed AVC and neg. feedback. O/P 4 watts. Chassis size, 13 1/2 x 3 1/2 x 2 1/2 in. Dist. 10 in. x 4 1/2 in. Hor. or vert. station names. Walnut or ivory knobs to choice. Aligned and calibrated ready for use. Sensitivity and Quality at Low Cost.

BARGAIN 9 1/2 Gns.

Double wound mains trans. PRICE Carr. and ins., 4/6. 8 or 10 in. speaker to match, 10/- and 25/- 7 Valve De Luxe, push-pull version, 7 watt output, £12.10.0. Carr. & ins. 5/-.

RECORD PLAYER BARGAINS

Latest Model UAS BSR Monarch 4-speed auto-changer £3.15.0, carr. 4/6. B.S.R. Three-speed Single Player, Model T.U.S. 84.12.6, carr. 3/- . Cut mounting board 5/-, carr. 1/- . Garrard and Collaro 4-speed Changers from 9/- gns. (as available).

NEW BOXED VALVES

NEW BOXED	ALL GUARANTEED
1R5, 1L17, 6 DAF96	9/- ECL50
185, 184 7/6 DFP96	9/- ECL50
384, 3V4 8/6 DK96	9/- EFL41
524 9/6 DL96	9/- EFL80
6AT6 8/6 33L6	10/- EFL80
6X7 6/6 2ABCO5	9/6 EFL80
6K8 6/6 EB31	6/6 EFL80
6Q7 6/6 EB41	10/- EFL80
6N87 8/6 EBC33	8/6 EY31
6V6 7/6 EBC34	12/6 EY31
6X4 7/6 ECP80	12/6 EY31
6X5 7/6 ECP82	12/6 EY31
7C5 9/- ECH42	10/6 PCC84
7Y4 8/6 ECH51	10/6 PCC80

SPECIAL PRICE PER SET

1R5, 174, 185, 184 or 384, or 3V4 ... 27/6 DK96, DAF96, DAF96, DL96 ... 35/- 6K8, 6K7, 6Q7, 6V6, 3Z4 or 6X5 ... 35/-

SPEAKER IRET.—Expanded Bronze anodised metal 8 in. x 8 in., 2/3; 12 in. x 8 in., 3/-; 12 in. x 12 in., 4/3; 12 in. x 16 in., 6/-; 24 in. x 12 in., 8/6, etc.

COPPER ENAMEL WIRE.—1 lb. 14 to 20 s.w.g., 2/-; 22 to 28 s.w.g., 3/-; 30 to 40 s.w.g., 3/3.

SWITCH CLEANER Fluid.—10 oz. tin, 3/3.

CHARGER TRANS. Prim.—0/200/250 v., sec., 6-9 v.—13 v. (for charging 6 v. and 12 v.), 1.3a., 13/6; 3a., 19/6; 4a., 22/6; 6a., 28/6.

FULL WAVE BRIDGE SELENIUM RECTIFIERS.—6 or 12 v. 11 amps., 8/9; 3 a., 15/6; 4 a., 28/6; 6 a., 24/6.

ELECTROLYTICS ALL TYPES NEW STOCK

Tubular Wire Ends	Can. Types, Clips, 3d. ea.
25/25 v. 50 12 v.	1/8 8/450 v.
50/50 v. 4500 v.	2/- 8/450 v. T.C.C. 2/6
100/25 v. 2450 v.	2/- 8/450 v. Hunts 5/-
8/450 v. B.E.C.	2/3 16/450 v. T.C.C. 4/6
8/500 v. Dub.	1/8 32/350 v.
8/500 v. Dub.	1/8 32/350 v. Hunts 4/6
8/500 v. Dub.	1/8 32/350 v. T.C.C. 4/6
16/450 v. B.E.C.	2/6 250/350 v. B.E.C. 8/6
16/500 v. Dub.	4/- 60/350 v. T.C.C. 6/6
16/450 v. T.C.C.	5/6 60/100/350 v. 11/6
32/350 v. Dub.	4/- 60/250/275 v. 12/6
32/500 v. Dub.	5/- 100/250/275 v. 12/6
50/450/550 v. B.E.C.	6/6 3,000 mid. 6 v. 2/6
32/250 v. B.E.C.	5/6 3,000 mid. 6 v. 2/6

SEMI-CONVERTERS. E.H.T. TYPE FLY-BACK VOLTAGES.—K3/25 2 kV., 5/-; K3/40 3.2 kV., 6/9; K3/45 3.6 kV., 7/3; K3/60 4 kV., 7/9; K3/100 5 kV., 12/6, etc.

MAINS TYPES.—RM1 125 v., 60 mA., 4/6; RM2 125 v., 100 mA., 4/9; RM3 125 v., 120 mA., 6/9; RM4 250 v., 250 mA., 10/-.

ENGRAVED CONTROL KNOBS for Lin. Spindle, 1 1/2 in. diam. Walnut or Ivory knobs to match above, 1/10. 10d. ea. 1 1/2 in. dia., 8d. ea. Superior Walnut or Ivory with gold ring, 1 1/2 in., 1/- ea. 1 in., 9d. ea. Pointer Knobs. Black with White Line, 9d. WEARITE "P" TYPE COILS. All ranges, 1 to 7, 2.6 ea. Osamor Q-series Coils. Sing. tuned. All ranges from 3.6. Full range popular Coil Packs.

I.F. TRANSFORMER—465 kc/s

Brand new ex-manufacturer's midget I.F.T. size 2 1/2 in. x 1 1/2 in. dist. core tuning. Latz wound coils, High Q. Bargain offer, 7/6 pair.

MAINS TRANSFORMERS

—Made in our own Workshops to Top Grade spec. Fully interleaved and impregnated. RADIO AND AMPLIFIER TYPE.—250 v., 60 mA. F.W. sec. 5 v. or 6.3 v. or 12 v. or 2.5 v. 2.5 a. set Htrs., 21/-, etc. C.R.T. HTR. ISOLATION TYPE.—Low leakage with or without 25% sec. boost voltage. Ratio 1:1 or 1.25:2.5, 10/6; 4 v., 10/6; 4 v., 10/6; 12.5:2.5, 10/6. Dittos with mains primaries 200/250 v., 12/6. Specials to order.

L.F. CHOKES.—10 H. 65 ma., 5/-; 15 H. 100 ma., 10/6; 10 H. 120 ma., 10/6; 20 H. 150 ma., 15/6; 30 H. 100 ma., 10/6; 40 H. 100 ma., 10/6.

ENGIN MULTICORE SOLDER CO 40 grade, 15g. 3d. per yd.; 16g., 4d. per yd.; 17b. 2.6.

LOUDSPEAKERS 8" x 8" OHM. 5in. R & A 16/6. 11in. Celest., 18/6; 7 x 4in. Goodman's Elliptical, 18/6; 8in. Elac., 20/-; 10in. R. and A., 25/-; 12in. Plessey 35/-; Goodman's Heavy Duty, Audion, 50, 15 ohms, 95/-; 2 1/2 in. Elac., 17/6.

SCOTCH BOY EMITAPE, etc., 1,200/20/-, 20/-, Long playing, 1,800/20/-, 20/-, 45/-, Paper tape, good quality 1,200/20/-, 20/-, 45/-, 8/6, 7/6, 4/3.

TWIN GANG TUNING CONDENSERS.—.0005 pf. Midget, 6/6; .0005 mfd. Standard size with feet, 8/6. BRIMISTONS.—CZ1 for 3a. heater chains, 3/3. CZ2 for 13a. or 2a., 2/6. CZ3 (Pilot Lamp), 1/6.

F.M. TUNER UNIT 87 mc/s—105 mc/s (by Jaxon).—As tested and approved by Radio Constructor. Complete Kit of parts to build this modern highly successful unit, drilled chassis and J.B. dial, coils and cans, 4 BVA miniature valves and all components, etc., for only £6.10.0 post free. SUPERIOR TYPE GLASS DIAL.—Calibrated in Mc/s and edge lit by 2 pilot lamps, 12/6 extra.

Illustrated handbook with full details, 2/- post free.

TRS RADIO COMPONENT SPECIALISTS (Est. 1946)

70 BRIGSTOCK ROAD, THORNTON HEATH, SURREY (THO 2188)



50 yards Thornton Heath Station. Listed above are only a few items from our very large stock. Hours: 9 a.m.—6 p.m., 1 p.m. Wed. Terms: C.F.H. or C.O.D. Kindly make cheques, P.O.s, etc., payable to T.R.S. Post Packing up to 1/6. Tel., 11b. 1/1, 51b. 1/6, 51b. 2/-, 151b. 3/5

Buses 130A, 133, 159, 166 & 190. Send 3d. stamp today for Complete Bargain List. OPEN ALL DAY SAT.

LASKY'S RADIO



SPECIAL OFFER OF BAND I-III TURRET TUNERS

Covering Channels 8-4 or I-9 with provision for 10 more coil sets. 2 valves: Mazda 30L1 cascade r.f. amp., Mazda 30C1 triode/pentode f.c. Complete with power supplies for 200-250 v. A.C. I.F. output 16-19 Mc/s., easily modified to other outputs. Full circuit diagram supplied.

LASKY'S PRICE

Complete with power supplies, valves and knob. **£5.17.6** Post 3/6


BRAND NEW AND PERFECT 16" METAL CONE C.R.T. AT ENORMOUS PRICE-SAVING

Brief specification: 6.3 v. heater, lon trap. 14 kV. E.H.T. wide angle 70 degrees, standard 38 mm. neck, duodecal base, magnetic focus and deflection. Length 17 11/16in. Gives large black and white picture 11 x 14in. Unused in original cartons. GUARANTEED BY US FOR 3 MONTHS. Full data, connections and suggested time bases supplied with every Tube.

LISTED AT £23.9.10. LASKY'S PRICE **£8.9.6**

Carr. & Insur. 22/6 extra.
Masks, Anti-Corona, Bases and Ion Traps available.

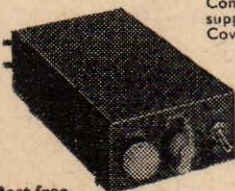SPECIAL OFFER OF "STIRLING" BAND III CONVERTERS



Post free.

Complete with own power supplies for 200-250 v. A.C. Covers all Channels Bands I and III and suitable for any TV set. Size: 7 x 3 1/2 x 2 in. approx. Metal case, brown crackle finish. Absolutely complete. Full instructions supplied.

LASKY'S PRICE

6 Gns.

LASKY'S (HARROW ROAD) LTD.

Open All Day Saturday. Early Closing, Thurs. Mail Orders to Harrow Rd.
42, TOTTENHAM COURT ROAD, W.1. 370, HARROW ROAD, WADINGTON, W.9.
Telephone: MUSUM 2803. LADBROKE 4075 and CUNNINGHAM 1979.

MAKER'S SURPLUS COMPONENT BARGAINS

WIDE ANGLE 38 mm.
Line E.H.T. trans., Ferroxcube core, 9-16 kV. 25/-
Scanning Coils, low imp. line and frame 25/-
Ferroxcube core Scanning Coils and Line Output Trans., 10-15 kV. EY51 winding Line Trans. Complete with circuit diagram, the pair 50/-
Frame Output Transformer Scanning Coils low imp. line and frame 17/6
Frame or line block osc. transformer 4/6
Focus Magnets, Ferroxcube P.M. Focus Magnets, Iron Cored 19/6
Duomag Focallisers 22/6
300 ma. Smoothing chokes Electromagnetic focus coil with combined scan coils 25/-

STANDARD 35 mm.

Line Output Transformers, No E.H.T. 12/6
Line Output Transformers, 6.9 kV. E.H.T. and 6.3 v. winding, Ferroxcube 19/6
Scanning coils. Low imp. line and frame 12/6
Ditto by Icarian 14/6
Frame or line blocking oscillator transformer 4/6
Frame output transformer 7/6
Focus Magnets: Without Vernier 12/6 With Vernier 17/6
Focus coils, Electromag 12/6
200 ma Smoothing Chokes 10/6

RADIO SUPPLY CO. (LEEDS) LTD.

Post Terms C.W.O. or C.O.D. NO C.O.D. under £1. Postage 1/9 extra under 22. 2/9 under 25. Open to callers 9 a.m. to 5.30 p.m. Sats. until 1 p.m. S.A.E. with enquiries, please. Full list 6d.; Trade list 5d.

R.S.C. TRANSFORMERS

Fully Guaranteed.

Interleaved and Impregnated.
Primaries 200-250 v. 50 c/s screened
TOP SHROUDED DROP THROUGH
250-0-250 v 70 ma. 6.3 v 2 a. 5 v 2 a. 16/9
350-0-350 v 80 ma. 6.3 v 2 a. 5 v 2 a. 18/9
250-0-250 v 100 ma. 6.3 v 4 a. 5 v 3 a. 23/9
350-0-350 v 100 ma. 6.3 v 4 a. 5 v 3 a. 23/9
350-0-350 v 150 ma. 6.3 v 4 a. 5 v 3 a. 29/9

FULLY SHROUDED UPRIGHT

250-0-250 v 60 ma. 6.3 v 2 a. 5 v 2 a. 17/9
Midjet type, 21-3-3in. 17/9
250-0-250 v 100 ma. 6.3 v 4 a. 5 v 3 a. 26/9
250-0-250 v 100 ma. 6.3 v 6 a. 5 v 3 a. 31/-
for R1335 Conversion 31/-
300-0-300 v 100 ma. 6.3 v 4 a. 5 v 3 a. 23/9
350-0-350 v 100 ma. 6.3 v 4 a. 5 v 3 a. 23/9
350-0-350 v 150 ma. 6.3 v 4 a. 5 v 3 a. 33/9
425-0-425 v 200 ma. 6.3 v 4 a. C.T. 6.3 v 4 a. C.T. 5 v 3 a. 49/9

FILAMENT TRANSFORMERS

All with 200-250 v 50 c/s Primaries: 6.3 v 1.5 a. 5/9; 6.3 v 2 a. 7/6; 0-4-6.3 v 2 a. 7/9; 12 v 1 a. 7/11; 6.3 v 3 a. 8/11; 6.3 v 6 a. 17/9.
CHARGER TRANSFORMERS
200-250 v 0-9-15 v 1 a. 11/9; 0-9-15 v 3 a. 16/9; 0-9-15 v 5 a. 19/9; 0-9-15 v 6 a. 22/9.

OUTPUT TRANSFORMERS

Standard Pentode 5,000 to 3 ohms 4/9
Small Pentode 5,000 to 3 ohms 2/9
E.H.T. TRANSFORMERS 200-250 v 250-250 v, 2,500 v 1 a. 2-0-2 v 1.1 a. 2-0-2 v 1.1 a. 36/6
for VCR97, VCR517 36/6

SMOOTHING CHOKES

250 ma 5 h 50 ohms 11/9
100 ma 10 h 250 ohms 8/9
30 ma 10 h 350 ohms 5/6
60 ma 10 h 400 ohms 4/11

SELENIUM METAL RECTIFIERS

E.C.C. 300 v 250 ma. 12/9; 130 v 40 ma. 3/9; 612 v 1 a P.W. 4/11; 240 v 50 ma. 4/11; 612 v 2 a P.W. 8/9; 612 v 4 a. 14/9; 250 v 50 ma. 7/9; 812 v 6 a P.W. 19/9; 612 v 10 a. 25/9.

BATTERY SET CONVERTER KIT

All parts for converting any normal type of Battery Receiver to A.C. mains 200-250 v 50 c/s. Supplies 120 v, 90 v or 60 v at 40 ma. Fully smoothed and fully smoothed L.T. of 2 at 0.4 a to 1 a. Price including circuit 49/9. Or ready for use, 9/9 extra.

ALL DRY RECEIVER BATTERY ELIMINATOR KIT

All parts for the construction of a unit (metal case 51-41-2in.) to supply Battery Portable receivers requiring 90 v and 1.5 v. Fully smoothed. From 200-250 v 50 c/s mains. Price, inc. point-to-point wiring diagrams, 39/9. Or assembled and tested at 46/9.

EX-GOVT. DOUBLE WOUND STEP UP STEP DOWN TRANSFORMER

10-0-100-200-230-240 v to 5-0-75-115-135 v or REVERSE. 80.100 watts. Only 11/9, plus 2/9 post.

EX-GOVT. CASE. Well ventilated black crackle finished, undrilled cover. Size 15 x 10 x 9 in. high. IDEAL FOR BATTERY CHARGER OR INSTRUMENT CASE, OR COVER COULD BE USED FOR AMPLIFIER. Only 9/9, plus 2/9 postage.

EX-GOVT. VALVES (NEW)

174	7/9	6K7G	3/9	6AT6	7/9
185	7/9	6X5GT	7/9	EB91	8/9
854	8/9	6L6G	11/9	EF89	8/8
6K8C	9/9	807	7/9	EF86	8/9
6S7GT	6/9	12A6	7/9	EL32	3/9
EF38	5/9	15D2	4/9	EL91	5/9
6V6GT	8/9	25Z4G	9/9	KT66	11/9
6U5G	6/9	35Z4	6/9	SP61	2/9
		MH4	4/9	MU14	8/9

EX-GOVT. UNIT RDL. Brand new, cartoned. Complete with 13 valves, including 5Z4G. Also mains trans. I.F. choke, rectifier, etc., etc. Only 29/6. Carr. 7/9.

Dept. N. 32, THE CALLS, LEEDS 2.

SMALL POTTED MAINS TRANSF. Removed from New ex-Govt. units. Primary 0-200-250 v Secs 250-0-250 v 60 ma. 6.3 v 2 a. 5 v 2 a. Size 3 1/2 x 4 1/2 x 3 in. **11/9**

CO-AXIAL CABLE 1in.

75 ohms 14/35 8d. yd.
Twinn-screened Feeder 11d. yd.

EX-GOVT. SMOOTHING CHOKES

100 ma 6-10 h 150 ohms 3/11
150 ma 6-10 h 150 ohms 6/9
150 ma 10 h 150 ohms 11/9
250 ma 5 h 50 ohms 12/9

E.H.T. SMOOTHERS

.02 mid. 5,000 v Cans (ex-Govt.), 2/11.

BATTERY CHARGER KITS

Consisting of attractive Blue Hammer Case, Transformer, F.W. Rectifier, Fuse, Fuseholder, Tag Strip Grommets and Circuits. For mains input 200-250 v 50 c/s, 6 v 2 a, 25/9; 6 v or 12 v 2 a, 31/6; 6 v or 12 v 4 a, 53/9. Any type assembled and tested for 6/9 extra.

R.S.C. 6 v or 12 v BATTERY CHARGER

For normal A.C. mains input 200-250 v 50 c/s. Selector panel for 6 v or 12 v charging. Variable charge rate of up to 4 AMPS. Fused, and with meter. Well ventilated case with attractive hammer finish. Guaranteed for 12 months. **75/-** Carr. 3/6.

TV CABINES

Handsome well-constructed with walnut veneer finish. Size 18in. high, 20in. wide, 13in. deep. Size of aperture 17in. 13ins. Fitted Doors. For 15in. or 17in. Tube. Limited number at only **79/6**

BATTERY CHARGERS

For mains 200-250 v 50 c/s. Output for charging 6 v or 12 v at 1 amp. In strong metal case. Only 25/9. Above can also be used for electric train power supply.



TELENEWS



Television Receiving Licences

DURING March the number of television licences increased by 103,022.

14,525,099 broadcast receiving licences, including 6,966,256 for television and 306,053 for sets fitted in cars, were current in Great Britain and Northern Ireland at the end of March, 1957.

It's an Ill Wind . . .

SHREWD advertisers are observing that one way of getting good value for money from I.T.V. is buying time opposite certain BBC programmes . . . "Twenty Questions," for example.

More than half of 240,000 London Area multichannel sets tuned to the "The Dave King Show" switched to I.T.V. at the approach of "Twenty Questions" on March 9th, Nielsen Audimeter recordings reveal, thus handing between 300,000 and 400,000 viewers to Val Parnell's "Saturday Spectacular." "Twenty Questions" subsequently averaged 230,000 viewers to "Saturday Spectacular's" 2,700,000.

New Fringevision Factory

THE accompanying illustration shows the commencement of building operations to treble the size of the present Fringevision factory so increasing the factory floor area from 5,000 to 15,000 sq. ft. All the construction work on the extension is being carried out by the firm's own staff and the technical department has assisted by supplying all the various plans and drawings, etc. These additions, it is hoped, will be completed by the end of August and so provide an even greater and more efficient service than in the past, which is anticipated will enable Messrs. Fringevision to despatch orders within twelve hours of their receipt.

Denmark Buys From Marconi Again

ANOTHER notable success has been gained for Britain in the export market. The Danish Posts and Telegraphs Department has ordered transmitting and aerial equipment to a value of £90,000 from Marconi's Wireless Telegraph Company Ltd. for three new television stations which are shortly to be built at Aalborg, Vestjylland and Naestved. The order, which includes monitoring and test equipment and flying spot slide scanning units, was obtained for Marconi's by their agent in Denmark, Sophus Berendsen Ltd.

Marconi equipment is already in use in three of the existing Danish television stations. These stations, fully equipped with Marconi transmitters, have come on the air in the last 22 months.

The three new stations will have identical transmitting equipment

consisting of a type BD.366, 4 kW Vision Transmitter and a type BD.317, 1 kW Sound Transmitter, feeding into a sixteen stack quadrant aerial. The vision transmitters will operate to European 625 line standards and will be amplitude modulated, while frequency modulation will be employed by the sound transmitters. To conform to international agreement the Aalborg station will operate at reduced power.

Both the 4 kW vision and 1 kW sound transmitters are of particular interest in that they are new designs representing a very important step forward in engineering practice.

TV for Wales and the West

PLANs for the building of studios and offices at Pontcanna Farm, Cardiff, for T.W.W. Ltd. (Television Wales and the West) have now been given approval at the monthly meeting of Cardiff City Council.

The model of the completed buildings, a view of which is shown



The scene on the site of the new Fringevision factory, with members of the staff at work.

on page 535, prepared by the architects Treadgold and Elsey, of Uxbridge, shows how the "new" has been blended with the "old." The proposed construction makes adequate allowance for any extensions which may be required in the future.

The 45-year-old Pontcanna farmhouse will be left intact and the new buildings will be "blistered" on to its side and back.

It is hoped that construction will start in May.

Lifetime Nuclear Battery Described

USE of nuclear energy for generating electrical current came under the spotlight recently

used experimentally at the Manvers Coal Preparation Plant at Wath-on-Deane, where it has been installed as an aid to plant control. This plant, which is the largest of its type in Britain, and one of the largest in Europe, processes the entire output of four collieries.

The installation, comprising a Marconi industrial vidicon camera, control unit and 14in. monitor is being used to view the coal input conveyor system at a cross-over point, where several conveyor belts converge. On the monitor, set up in the plant control room, the duty engineer is able to view belt working and loading conditions at this critical point. Any fouling of the belt

of last year, is now to become a permanent feature for excursion outings in the Scottish region of British Railways.

Television screens are positioned above the doors of eight second-class open coaches and are visible to all passengers. Each coach is also fitted with separate loudspeakers for recorded music, and points are provided for use with a roving microphone. The artistes will not only be televised but will also visit each coach and give a number over the microphone.

The diesel-electric unit which supplied the power for the broadcast is housed in a separate van.

New BBC TV and V.H.F. Station in West Wales

THE BBC's new television station at Blaen Plwy, near Aberystwyth, was brought into service on April 29th. On this date also the V.H.F. service from the same site which has been in partial operation on low power using a temporary mast and aerial, was brought into full power operation in conjunction with the new 500ft. mast which supports both the television and V.H.F. aerials. This will complete another stage in the BBC's plan to extend its television service and to improve the sound broadcasting service in Wales.

The television transmissions will be on Channel 3 (vision 56.75 Mc/s, sound 53.25 Mc/s), horizontally polarised, and with an effective radiated power of 1 kW. They will serve the coastal belt around Cardigan Bay including the Pwllheli and Portmadoc areas in the north and the Tregaron and Aberporth areas in the south.

The Blaen Plwy station will transmit all three sound programmes on V.H.F., the Welsh Home Service on 93.1 Mc/s, the Light Programme on 88.7 Mc/s, and the Third Programme on 90.9 Mc/s. Until now only the Welsh Home Service has been transmitted, under the temporary arrangement which was put into effect in October last year in order that improved reception of this programme could be made available to Welsh listeners as quickly as possible. The effective radiated power for each programme will now be 60 kW, and the area served by the V.H.F. transmissions will include the southern part of Caernarvonshire, western Merioneth, the whole of Cardiganshire, and parts of Carmarthenshire and Pembrokeshire.



A National Coal Board engineer watching the conveyor system on the new Marconi TV Monitor from the plant control room.

as 50,000 electronics engineers from all over the world met in the National Convention of the Institute of Radio Engineers at the Waldorf-Astoria Hotel and the New York Coliseum.

Engineers at the Air Force's Rome Air Development Centre, New York, discussed a practical source of electrical energy that uses the heat from decay of radioactive isotopes to drive a semi-conductor "thermopile"—a transistor-like device which produces electrical energy when heated. The thermoelectric generator was described as a rugged and stable "sealed-in lifetime power source" which can last "up to 30 years."

Coal Board and Industrial TV

THE first industrial television equipment to be purchased by the National Coal Board is being

or failure of the drive system is thus immediately observed. An obstruction or conveyor drive failure of only a few minutes' duration can cause tons of coal to pile up and spill over.

By presenting to the plant control engineer a constant picture of what is happening on the coal input conveyor, the effect of obstruction and drive failures can be minimised. This facility can be of considerable assistance in the efficient working of the complex system in a plant such as this, where obstructions and breakdowns can have very serious effects if not quickly observed by the control staff.

Television Train for Excursion Outings

THE Scottish Region's closed-circuit TV show train, which made experimental excursions to Oban and Blackpool in the autumn

NEWNES GREAT NEW REFERENCE WORK

AN ESSENTIAL "PIECE OF EQUIPMENT" FOR EVERY

Radio & Television Engineer

BROADCASTING • COMMUNICATIONS • NAVIGATION • SERVICING, Etc.
45 SECTIONS CRAMMED WITH FACTS, FIGURES AND DATA

This new work provides in compact form all the information required by ENGINEERS, TECHNICIANS, RADIO AMATEURS. To those engaged in design, maintenance, technical sales, operation and servicing of modern radio and TV transmitting and receiving equipment it is invaluable.

This is the work you have always needed for your technical library—supplying in an instant the practical data and theory, the formulae, calculations and information you need, and which is often not obtainable without recourse to numerous references. For the technician and executive-to-be it is indispensable.

This is a Newnes publication and worthy of your immediate attention. Claim your copy for Free Examination to-day.

WRITTEN BY 36 SPECIALISTS

Formulae & Calculations. Electron Optics. Materials. Studios & Equipment—*planning, lighting, camera tubes, etc.* Broadcasting Transmitters & Power Plant. Communication Transmitters—*design, components, marine, ground-to-air, mobile, call signs, etc.* Amateur Radio Equipment—*licences, frequencies, H-F transmitter and receiver design, etc.* R.F. Transmission Lines. Waveguides. Broadcasting Receivers—*design, developments, V.H.F., etc.* TV Receiver Design—*frequency conversion, channel selection, colour TV, etc.* Commercial H.F. Links. Broad-Band Radio Systems. Navigation & Radar. Aero Equipment. Industrial TV. Aerials—*fundamentals, vertical rod-inverted L-loop-aerials, V.H.F.—band III—car aerials, fringe equipment, etc.* Transistors. Crystal Diodes. Resistors. Capacitors. Inductors & Transformers. Microphones. Loudspeakers. Interference—*causes, etc.* Recording. Gramophone Mechanisms. Batteries & Conversion Equipment—*dry, storage, charging, vibrators, etc.* Measuring & Test Equipment. Radio & TV Installation & Servicing—*equipment, alignment, precautions, fault-finding, etc.* Projection TV—*tubes, adjustment, theatre, etc.* Quartz Oscillators & Frequency Allocations. Units & Symbols, etc., etc.

PROVE ITS VALUE—

FREE FOR 7 DAYS

It is impossible to list above more than a small fraction of the contents of this important new work—so we provide you with the opportunity to examine it freely in your own home, and without obligation. POST THE COUPON NOW . . . it is greatly to your advantage to see this invaluable reference work.

To: George Newnes, Ltd., 66-69, Great Queen Street, London, W.C.99.
 Please send me Newnes RADIO AND TELEVISION ENGINEERS' REFERENCE BOOK without obligation to purchase. I will either return the work within eight days or I will send the first payment of 7s. 6d. eight days after delivery, and 10s. monthly thereafter until the sum of £3 17s. 6d. has been paid. Cash price within eight days is £3 12s.

Name

Address


Occupation

Your Signature

(Or your parent's signature if under 21) RTRB.35

Place X where it applies.

HouseOWNER	☐
Householder	☐
Living with parents	☐
Lodging address	☐

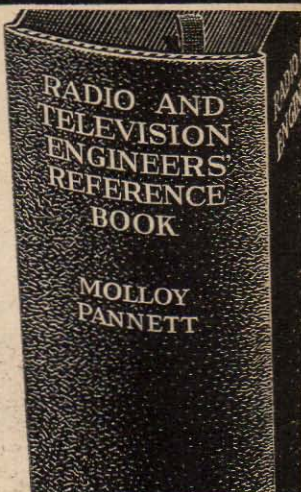

STUDY IT—TEST IT
IN YOUR OWN HOME
WITHOUT COST OR
OBLIGATION

1,600

pages of information and data to meet your everyday needs.

45

main sections, written and compiled by leading authorities.

1,860

diagrams, tables, standard formulae, calculations, measurements.

2,500

cross-referenced index entries enabling wanted information to be found in an instant.

POST TO-DAY

T.V. UNITS

THE I.F. UNIT

This unit employs 3 miniature valves, the first two of which are common to sound and vision. After separation, sound and vision are amplified separately at 34.38 and 37.5 mc/s respectively. Vision is then detected and passed to two stages of Video amplification, and sound is detected and further amplified by output valve type EL84 to give just over one watt of high fidelity sound. The circuit employs a variable peak white clipper to reduce vision interference and the second section of the audio detector is used to limit sound interference. The unit which can be driven by any standard 34/37 mc/s current or other tuner is beautifully made and contained on a chassis size approx. 8in. x 4 1/2in. x 2in.

The unit with valves made up, aligned and ready to work is available price £9.12.6.



THE POWER UNIT

Intended for A.C./D.C. working with 3 amp. valves, this unit contains all the necessary power components. Rectification is by metal rectifier, smoothing is by a 3 Henry choke, and large electrolytic condensers ensure freedom from hum and a clean picture. The ballast resistor has ample

tappings to compensate for H.T. voltage as well as heater current and a thermistor protects the circuit against initial current surges, fuses are fitted in the mains input lead. There is a front control comprising a double pole on/off switch. This is attached to the sound volume control which, although not part of the power unit, is included for the sake of convenience and symmetry. The size of the unit is 15 1/2in. x 3in. x 2in. It is all wired up and ready to work, price £3.5.0.

THE TIME BASE CHASSIS

This uses 6 valves and includes the sync separator, the focus magnet, scanning coils and ion trap. The line time base is of the self-oscillating type employing an auto wound O.P.T. and efficiency diode to provide boost voltage for the line fly back E.H.T. transformer which gives about 12.5 kV, the frame time base is multi vibrator type, using an ECL80.

The whole unit measures 15 1/2in. x 6 1/2in. x 2 1/2in., and the metal work includes tube support for chassis mounting a 1 1/2in. tube, but up to 2 1/2in. tube can be scanned but will require separate mounting. Price for the unit with valves ready made up and tested is £12.15.0.

NOTE


These three units, although quite separate and usable separately, may also be joined together and then comprise a complete T.V. less only tuner unit and speaker (available if required). Demonstrations at all branches.

TURRET TUNER

Brand new stock, not surplus, with coils for Band I and III supplied complete with valves PC84 and PCF80—L.F. Output 33.38 Mc/s with instructions and circuit diagram 99/6. With knobs 3/6 extra; post and insurance 2/6.

T.V. SET FREE

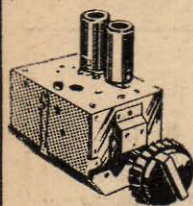Everyone who buys a copy of our new publication "The Easier to Build 13 Channel T.V." stands a fair chance of winning the set. The price of the publication is only 3/6, fully illustrated.



ELECTRONIC PRECISION EQUIPMENT, LTD.

Post orders should be addressed to

E.P.E., LTD., Dept. 5, Sutton Road, Eastbourne.

Personal shoppers to one of these addresses, please.

266, London Road, Croydon. Phone: CRO 6558

42-46, Windmill Hill, Reddip, Middx. Phone: RUISLIP 5790

152-3, Fleet Street, E.C.4. Phone: FLEET 2833

29 Stroud Green Rd., Finsbury Park, N.4. Phone: ARCHWAY 1049

249, Kilburn High Road, Kilburn. Phone: MAIDA VALE 4921

MAKE YOUR OWN BAND III CONVERTOR

Teletron Band III Coil Set

Supplied with circuit diagram 15/-
Plus packing and postage 1/6

Small Mains Transformer for Converter

Pri.: 200/250 volt. Sec.:
200 volt 25 m/a. 6.3
volt. 1 mains 15/9
Plus packing and postage 1/6

Walsey Crossover Unit

This unit is for matching two separate aerials into 70/80 coaxial cable 11/6
Plus packing and postage 1/6

Spencer-West Type 54 Pat-

terned Removal Unit 25/-
Plus packing and postage 1/6

Brayhead Turret Convertors

(State channels required)
Post free £7/7/-

BRING YOUR TECHNICAL LIBRARY

UP TO DATE (All prices shown, P. & P. free)

Television Faults

by N. Stevens, with circuit diagrams for Baird, Everyman, English Electric, Marconi, Murphy, Philips and Ultra 5/6

Television Servicing for Beginners

Book 1, by L. G. Furley, A.M./Brit./I.R.E. 5/6

Television Circuit Refinements

by C. H. Banthorpe 5/6

Television Test Equipment

by E. N. Bradley 5/6

40 Circuits using Germanium Diodes 3/6

Television Timebase Circuits

by C. H. Banthorpe 5/6

Television Circuits and Service Data No. 1

by C. H. Banthorpe covering over 25 models including: Alba, Ambassador, Bush, Ferranti, G.E.C., K.B., Masteradio, Murphy, Philco, Philips, Pilot, Pye, Raymond, Ultra, Vidor, White-

Ibbotson 10/-

The complete set including DTV Replacements Handbook 38/-



REPLACEMENTS

134/136 LEWISHAM WAY, NEW

CROSS, S.E.14. TIDeway 3696/2330

Telegrams: FLIBAK, London, S.E.14

VALVES • SAME DAY SERVICE

All Guaranteed New and Boxed

1.4v. midget, 1R5, 1S5, 1T4, 1U5, 884, DAF91, DP91, DK91, DL92, DL94: any 4 for 27/6.

1A7GT	12/6	6K8G	7/9	80	8/6	ECH81	8/-	PCF82	11/6
1C5GT	15/6	6K8GT	9/6	B36	19/6	ECL80	9/-	PEN46	6/6
1H5GT	11/-	6L18	13/6	CL33	16/6	EF37A	9/-	PL36	18/6
1N5GT	11/-	6TGT	9/6	D15	3/-	EF39	6/-	PL33	22/6
1R5	8/6	6SN7GT	9/6	D77	6/6	EF40	12/6	PL81	11/9
1S5	7/6	6U4GT	12/6	D77	6/6	EF41	9/6	PL82	9/-
1T4	7/3	6V8G	7/-	DAC32	11/-	EF42	12/-	PL83	10/6
3A5	7/-	6V8GT	7/6	DAF96	8/6	EF50	6/6	PY80	9/-
3C4	9/-	6X4	7/-	DC90	7/-	EF80	8/6	PY81	8/-
3Q5GT	9/6	6X5GT	6/6	DF33	11/-	EF83	7/6	PY82	7/-
384	7/6	7B7	8/-	DF96	8/6	EF85	12/6	PY83	9/6
3V4	8/6	7C5	8/-	DH76	8/6	EF89	10/-	PZ30	18/-
5U4G	8/-	7C6	8/-	DH77	8/6	EF91	6/-	SP41	3/6
5Y3GT	7/6	7H7	8/-	DK32	12/6	EF92	5/6	SP61	3/6
5Z4G	9/-	7S7	9/-	DK2	9/-	EL38	22/6	U25	12/6
6AB8	7/6	7Y4	8/-	DK96	8/6	EL41	10/-	U50	7/6
6AK5	4/6	10C2	13/6	DL33	13/6	EL42	11/-	U78	8/-
6AL5	6/6	10P1	15/6	DL35	15/6	EL84	9/6	U78	7/-
6AM5	5/-	12AB8	10/6	DL86	8/6	EM34	10/-	U804	8/6
6AM6	6/-	12AT7	8/-	DM70	8/6	EM80	10/6	UABCO	11/6
6AQ5	7/6	12AU7	7/6	EABC80	7/6	EY51	10/6		
6AT8	8/6	12AX7	9/-	EAF42	10/6	EY86	9/6	UAF42	10/6
6BA6	7/6	12J7GT	11/6	EB91	8/6	EZ40	8/-	UBC41	8/6
6B6	7/6	12K7GT	8/6	EBC39	7/6	EZ80	8/6	UP80	9/6
6B6B	7/6	12N3GT	14/-	EB041	10/-	EZ81	10/-	UCH42	10/6
6B6B	7/6	12Q7GT	8/6	EF83	9/6	FW4.500	9/6	UF41	9/-
6B6B	7/6	12Z3	7/6	EF89	8/6	GZ32	12/6	UL41	10/-
6E1	17/6	1487	14/-	ECC81	8/6	GZ3C	10/-	UL84	11/6
6F8G	8/6	25L2GT	9/-	ECC82	7/6	KT44	6/6	UY21	15/6
6F12	6/-	25Z4G	9/6	ECC83	9/-	KT83	7/6	UY41	8/6
6F13	13/-	25Z6GT	9/6	ECC84	10/6	KT83	7/6	UY41	8/6
6F15	14/9	35A5	11/-	ECC85	9/6	KT86	6/6	UY85	10/6
6J6	5/6	35L6GT	9/6	ECC89	5/6	MU14	8/6	W78	8/6
6J7G	7/6	35Z3	10/6	ECC93	12/6	N77	12/6	W77	5/6
6K7G	4/6	35Z4GT	8/-	ECCF82	11/-	P81	3/6	X78	12/6
6K7G	4/6	35Z5GT	9/-	ECCF84	8/-	P84	8/-	Y82	7/6
6K7GT	6/-	50L6GT	8/-	ECH42	10/-	PCF80	6/6	Z77	6/-

Postage 5d. per valve extra.

READERS RADIO

24, COLBERG PLACE, STAMFORD HILL, LONDON, N.16 STA. 4587



UNDERNEATH THE DIPOLE

TELEVISION PICK-UPS AND REFLECTIONS

By Iconos

IT is not often that I comment in these columns about the commercials. When I.T.A. commenced operations I watched the commercials with considerable interest, though—like most viewers—never admitting that they ever persuaded me to make a single purchase of an advertised product. Then the novelty began to fade. I was able to condition myself and ignore them altogether; alternatively, to make a cup of tea or a telephone call, or to put the dog out, while they were on.

THE STAR COMMERCIALS

THIS phase has now passed. Many commercials are now so well made and so amusing in content that they outshine the I.T.A. programmes that surround them. The cartoons are sometimes brilliant, the musical snippets are first class and the technical values are improving rapidly.

Some of the most popular musical advertising jingles have now become favourites with the children. I have heard of at least two babies whose crying bouts can be turned into contented chuckles when they recognise certain jolly little commercial melodies. This is surely advertising at its very best, indicative of the competition there is between the many small companies who make a living out of this new industry. The bold and blatant commercial no longer scores, it merely bores. The subtle and witty thumb-nail story, whether in cartoon or straight photography, which ends with a novel twist, does the trick. How disappointing it must be for an advertiser to find his latest TV commercial brain-child smothered on each side by some of the feeble programme matter that is appearing more and more on I.T.V. One might almost imagine that some of the brighter script writers are leaving the programme contractors and joining the commercial-making companies.


A CASK OF AMONTILLADO

I MUST admit that I have not seen very many A.B.C.-TV features networked through London in the evenings, and therefore may have been unlucky in the particular programmes I have seen. At any rate, I cannot remember anything outstanding since the "Jekyll and Hyde" series with Dennis Price. For me, A.B.C.-TV hit a new low, technically and artistically with *A Cask of Amontillado*, from a story by Edgar Allan Poe. With the colourful background of a masked carnival, this well-mounted playlet in macabre vein might have succeeded if the producer had restrained his tendency to self-conscious art-crafty production treatment. Titles were presented skewed, actors had their heads partly out of picture and many camera set-ups, intended to appear clever—merely looked like terrible camera handling. If this is a sample of the technical treatment of the remainder of the series under the title of *Armchair Theatre*, then either the producer should use more conventional camera angles or the A.B.C.-TV technicians take another course at their training school. The pro-

ducer, Dennis Vance, has given us many good TV plays in the past. I feel sure that he will give us good entertainment in *Armchair Theatre* when he restrains his actors from hamming and his technicians from being ham-handed.

TELEvised PLAYS

DO television excerpts of stage plays at theatres induce the viewer to buy a ticket to see the live show? Apparently they do—in certain cases. *Romanoff and Juliet* and *The Bride and the Bachelor* are two West End plays which seem to have scored on TV, to the benefit of their own box offices. Not all plays are so lucky, however. It is now essential for TV presentation to be carried out under invited audience conditions, so that the cameras and microphones can be manoeuvred to the best advantage. The actors can also play-down a little, not in the broad manner essential to put over lines to the back row of the gallery. This must not be construed as supporting the current tendency of British actors to slur their words, throw away lines and otherwise deliver dialogue in a

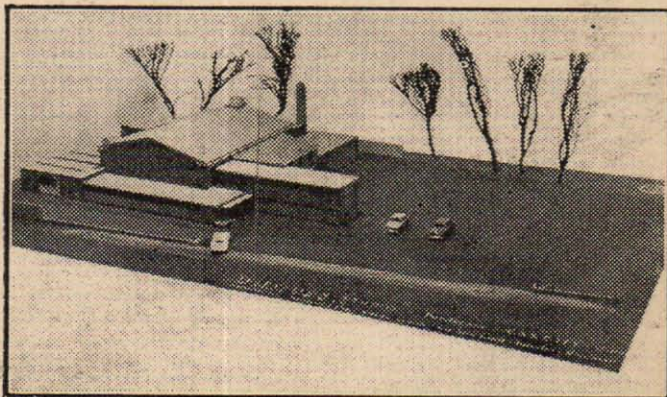

A model of the TV studio at Pontcanna, Cardiff, for the new transmitting Station for Wales and the West.

slovenly manner. Even dialect plays have to be presented in a modified form, if they are to be understood outside their own region. The BBC's recent presentation of Sean O'Casey's *Juno and the Paycock* was a model of how a dialect play should be produced. It was a long play—ninety minutes playing time—and I only viewed the last half-hour of it. However, I had seen it on the stage and on films, and heard it on the radio, so that I was able to pick it up with ease. I was sorry I had missed the beginning. The performances of Liam Redmond as the Captain and Noel Purcell as Joxer seemed to me to be perfect from every point of view, with excellent production work by Eric Crozier.

TV STUDIO EQUIPMENT

THE stage equipment to be found in most British television studios is largely made up of items specifically designed for feature films. Camera dollies, microphone booms, lights and their accessories, and many other items familiar in the film studios can be seen every day in use. Some of the equipment is almost brand new, delivered straight to the TV studio and not taken over from a film studio that has gone out of business. The requirements of the two media are on similar lines up to a point, and it was a natural expedient during the rapid expansion of TV studio facilities to make use of existing designs. In practice, television required lighter but stronger equipment, free from noises when being moved about during a scene or, in the case of lamps, when getting overheated through being left on for long periods. Equipment specially designed for television studios is now beginning to appear in Britain as well as in America. The demand for special tripod heads for mounting TV cameras is much larger than the demands of the film production industry in its boomiest days. Development contracts from the BBC are resulting in the appearance of beautifully made accessories, which are being turned out in batches of a hundred or so instead of the batches of ten which sufficed for the film studios. I am thinking in particular of a new Vinten camera head mounting, which admirably keeps the centre of gravity of a heavy TV camera at the same place, no matter how the camera is tilted or panned. The

price is modest, due to the large batches ordered.

CHROMIUM-PLATED GADGETS

THEN there are camera dollies of various types, which can "crab" about the stage in any direction without the use of metal or wood tracks. Knocking nails or screwing screws into the very level floors of TV studios is taboo, to enable these trackless dollies, cranes and velocitators to be used. Therefore, the scenery has different methods of bracing, which usually depends upon weights for holding it in position. There is now a new type of microphone boom, made by Scanners Ltd., which has some special advantages for television. In a model recently exhibited, however, the width between the wheels was too great to go through the average doorway in a set, a point which will shortly be remedied. Some of the equipment I have seen sparkles with smart-looking chromium plate, for which TV management seem to have a weakness. This is a mistake. A dull black finish is much more practical and avoids undesirable reflections of lights.

TELERECORDING PROGRESS

AS noted in this column a few months ago, the ITA programme contractors have been cautious in deciding to instal telerecording equipment for the British Standard 405 line, interlaced, picture. In addition to the Marconi equipment, recently announced, a new type of telerecording camera has been developed by High Definition Films in association with Pye. Both of these equipments give results far superior to the type of camera which photographs only half of the interlace, unavoidable owing to the slow mechanical pull-down of the film in the camera between photographing each frame. These new equipments, together with the elaborate flying-spot film scanners for reproducing film, made by Cintel and EMI, must be in the very front rank of television developments, and far ahead of the best in America.

NEW TV CAMERAS

THE latest type CPS Emitron cameras are coming into use at some of the BBC studios, signifying a victory for those BBC engineers who were unconvinced that the image orthicon camera was

the answer to all television camera problems. It is interesting to note that the horizontal angle of acceptance of a CPS Emitron camera lens of 75 mm. focal length is the same as a 50 mm. lens on an image orthicon or a 35 mm. lens on a standard cine camera. That angle is approximately 25 deg. Rarely do TV producers require wider acceptance angles than this. The feature film cameramen regularly use lenses of much shorter focal lengths, such as 18.5 mm. and 25 mm. These give interesting camera compositions, but tend to give peculiar distorting effects: thus, facial blemishes are exaggerated and the actors' noses seem to become more prominent in close-ups, while background perspective treatments are sometimes quite false. Nevertheless, carefully handled, these very wide gauge lenses have great dramatic value.

THE "CHELSEA REVUE"

FOR some months past Sidney Bernstein, of Granada, has been extending his entertainment commonwealth from films to television and from television to the music-hall. This is no backward step—it is the inevitable and natural link-up of an entertainment "combined operation." Granada-controlled music-halls now include the Metropolitan, Edgware Road, the Palaces at Chelsea and Walthamstow and the Empress at Brixton (which has now been turned into a cinema and renamed "The Granada"). The Walthamstow Palace is closed for the time being. The Metropolitan and the Chelsea Palace are gradually being modernised so far as the comfort of both audience and patrons are concerned, and bright new shows are being put on. The Chelsea Palace has already begun to play its part in connection with Granada TV, when an excerpt from a revue there was networked. This revue is being run on a resident season basis and is of a new style, about mid-way between the intimate and sophisticated West End revue on the one hand and the music-hall on the other. The first transmission on TV was excellent. Terry Scott was the star, and with him were Hugh Lloyd, Baker and Douglas, and Roma and Bob Dale.

OUR COMPANION JOURNAL
Practical Wireless

1/3 Every Month

SUMMER SALE

12 MONTHS' GUARANTEE.


14in. £5.10.0. 17in. £7.10.0.

We are now able to offer this wonderful guarantee. 6 months' full replacement and 6 months' progressive. Made possible only by improved high quality of our tubes. Carr., Ins., 15/6.

CONVERT YOUR 9in., 10in., 12in. to 14in., 15in. or 17in.

Our pamphlet is FREE and on many sets it costs only the tube to give you these giant pictures. SPECIAL OFFER 14in., 15in. and 16in. T.V. tubes £5. Perfect, see them working in our shops.

14in. T.V. CHASSIS, £13.19.6.

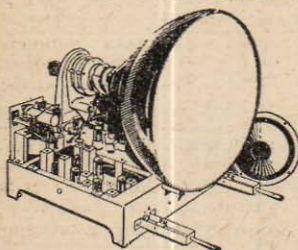

FAMOUS TURRET TUNER FITTED 50/- EXTRA.

Complete with tube and speaker. Modified ready working. Fully guaranteed for 3 months. These are demonstrated to personal callers. LESS valves. As above with 5 of the valves £15.19.6. Or with all the valves £19.19.6. Ins., Carr., incl. Tube 25/- 17in. TUBE RECTANGULAR on


adapted chassis. LESS valves £19.19.6. With 5 valves £21.19.6, or complete with all valves £25.19.6. Plus 25/- Ins., Carr. State BBC channel (and ITA if TURRET required).

MAINS TRANSFORMERS. 350-0-350 v., 3/9. 4 v.-4 v. heaters. 200-250 v. prim. Post & packing 2/3.
MAINS TRANSFORMERS. 350-0-350 v. 2/9. 12 v.-4 v. heaters. 200-250 v. prim. Postage 2/3.

O.P. TRANS. 1/3. 2-5 ohms. Standard size. Salvage guaranteed. P. & P. 1/- 20 for £1. P. & P. on 20 5/6.

T.V. CHASSIS 79/6

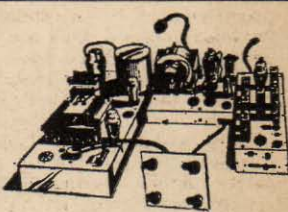Complete chassis by famous manfr. Easily converted to ITA. R.F. E.H.T. unit included. A.C. s'het 3 separate units (power, s'vision, t/base inter-connected). 8in. P.M. speaker and drawings FREE with each order. I.F.s 16.5-19.5 m/cs. Carr., Ins., 10/6.



SEND FOR FREE CATALOGUE of SUMMER SALE.

V.H.F. 1466 RECEIVER, 27/6.

With 6 valves, ex-W.D. new condition, dial drive tuning. Receives T.V. sound, police, fire and amateurs. 30.5 m/cs to 40 m/cs. I.F.s 7 m/cs. Post 2/6. Drawings and conversion data FREE with each set. (Similar to 1124 set but with slow-motion dial.) V.H.F. R.F. 24 UNIT. 7/9. Including valves, Chassis approx. 10in. x 8in. x 4in. Postage 2/6.
V.H.F. 1125 RECEIVER. 7/9. Including valves, Chassis approx. 12in. x 8in. x 3in. Drawings FREE with each order. Postage 1/9.

IDEAL RADIO OR R/GRAM CHASSIS, 39/9.

3 w/band and gram., s'het 5 valve international octal. Ideal table gram., but still giving high quality output. 4 knob control. 8in. P.M. speaker, 7/9 with order. Set of knobs 2/-. Chassis approx. 15in. x 6in. x 7 1/2in. LESS valves. Ins., Carr., 4/6.

RADIO-GRAM CHASSIS, 29/9.

Including 8in. speaker, dial and knobs. 5 valve s'het, 3 wave band. A.C. mains. Complete, tested, guaranteed. LESS valves. Post and packing 4/6.

SPEAKERS 8/9. 8in. P.M. Stocks cannot last. Have you had all you may require? Complete with O.P. trans., 10/-. All are guaranteed money back. P. & P. 1/9. Liverpool St. to Manor Park—10 mins.

DUKE & CO. (P.T.) 621/3, Romford Rd., Manor Park, London, E.12

GRA 6677-8-2791

Wanted QUALIFIED MEN & WOMEN

PERSONAL & INDIVIDUAL TRAINING IN—

Industry and Commerce offer their best posts to those with qualifications—appointments which bring personal satisfaction, good money, status and security. As part of a modern industrial organisation, we have skilled knowledge of what is required and the best means of training personnel for present day and future requirements. We specialise also in teaching for hobbies, new interests or part-time occupations in any of the subjects listed here. Write to us to-day for further information. There is no obligation of any kind.

Accountancy
Advertising
Aeronautical Eng.
A.R.B. Licences
Art
Automobile Eng.
Banking
Book-keeping
Building
Business
Management
Carpentry
Chemistry
City & Glds. Exams
Heat & Vent. Eng.
Also courses for GENERAL CERTIFICATE OF EDUCATION A.M.I.H., A.V.E., A.M.S.E., A.M.Brit. I.R.E., A.M.I.Mech.E., A.M.I.E.D., A.M.I.M.I., A.F.R.Ae.S., A.M.I.P.E., A.C.C.A., A.C.I.S., A.C.C.S., A.C.W.A., City & Guilds Examinations, R.T.E.B. Serv. Cert., R.S.A. Cert. etc.

Civil Service
Commercial Subjects
Commercial Art
Customs Officer
Draughtsmanship
Economics
Electrical Eng.
Electrical Installations
Electronics
Electronic
Draughtsmanship
Engineering
Export

High Speed
Oil Engines
Industrial Admin.
Jig & Tool Design
Journalism
Languages
Management
Maintenance Eng.
Mathematics
M.C.A. Licences
Mechanical Eng.
Metallurgy
Motor Eng.

Photography
P.M.G. Certs.
Police
Production Eng.
Prod. Planning
Radio Engineering
Radar
Radio Amateurs
(C & G) Licence
Radio & Television
Servicing
Refrigeration
Sales Management
Sanitary Engineering

Salesmanship
Secretaryship
Shorthand & Typing
Short Story Writing
Short Wave Radio
Sound Recording
Telecommunications
Television
Time & Motion Study
Tracing
Welding
Workshop Practice
Works Management

NEW! COURSES WITH PRACTICAL EQUIPMENT
in RADIO • TELEVISION • MECHANICS • CHEMISTRY
ELECTRICITY • DRAUGHTSMANSHIP • PHOTOGRAPHY ETC.

COURSES FROM 15/- PER MONTH

POST THIS TODAY

B E.M.I. INSTITUTES, Dept. 138K, London, W.4

I O NAME

C K ADDRESS

C I am interested in the following subjects with/without equipment

A P

S JUNE/57

(We shall not worry you with callers)

IC92

The only Home Study College
operated by a world-wide
manufacturing organisation

EMI

INSTITUTES

Associated with "H.M.V.", Marconiophone, etc., etc



FREE

TRANSISTORS

Junction Type P.N.P.

British Manufacture

Red Spot.	800 Kc/s. Audio Frequency	10-
Blue Spot.	1.6 Mc/s. Mixer and Pre-Changer	15-
White Spot.	2.5 Mc/s R.F. and I.F. Amp.	20-

All transistors are tested and Guaranteed.
N.B. Red Spot is similar to Mullard OC71.

PRE-SELECTED SEVEN TRANSISTOR PUSH-PULL PORTABLE SUPERHET

Just switch to your favourite Station. No tuning, no aerial or earth. Pre-select 3 stations. Complete with all components and seven Transistors. 7 x 4 Elliptical speaker. Teletron Superhet Coils and I.F.T.s. Powered by 71 v. dry battery which lasts for months. 150 Milliwatts output. All the above with Circuits, etc.

£9 17 6. Carriage paid.
Or with Matched Mullard OC72s (200 Milliwatts Output) and 7 x 4 Elliptical High Resistance Speaker 30" extra.
Suitable Plastic Cabinet, easy to assemble. 18 8.
Call and hear demonstration model working.

"EAVESDROPPER" THREE TRANSISTOR PERSONAL PORTABLE. No Aerial or Earth Required Pre-selected 2-station Receiver

We can supply all the components for building the above set as per "Radio Constructor" with Plastic Case, less Microphone for 77 6.
Complete with Acos mike 90-. Complete with min. Hearing Aid 92 6.

TRANSISTOR PUSH-PULL AUDIO AMPLIFIER (150 Milliwatts Output)

Build this Push-Pull Amplifier which is ideal for Crystal or Magnetic Pick-up Amplification, Baby Alarm, Microphone Amplifier, etc. Powered by 6 volt Dry Battery lasting for months. Complete Kit of Parts including 4 Transistors and all Components with Circuit (less Speaker), £4 10-.

SEND STAMPS FOR NEW 1957 28-PAGE CATALOGUE
OPEN MONDAY to SAT. 9-6. THURS. 1 o'clock.

HENRY'S RADIO LTD.

5, HARROW ROAD, EDGWARE ROAD, LONDON, W.2.

TEL.: PADDINGTON 1008-9, 0401

62A INDICATOR UNIT
Containing VCR97 with Mu-Metal Screen. 21 valves: 12-EP50, 4-SP61, 3-EA50, 2-EB34. Plus Pots, Switches, H.V. Cond., Resistors, Muirhead S.M. Dial, Double Deck Chassis and Crystal. BRAND NEW ORIGINAL CASES, 67 8. CARR. FREE.

RF24, 10-; RF25, 12 6;
RF26, 25-; BRAND NEW WITH VALVES. Carr. 2 6.

B.S.R. RECORD CHANGERS

Very latest type "Monarch." 3-speed with HGP57 crystal turn-over pick-up. Plays mixed records. Brand new and guaranteed. Listed at £16 10-
£7 19 6. carr. paid.
B.S.R. 4-SPEED
Plays mixed records.
£8 15-. P.P. 3 6.

TRANSMITTER RECEIVER

(Army Type "17" Mk. II)
This well-known R.T. Transmitter is offered complete with Valves, High Resistance Headphones, No. 3 Hand-Mike and Instruction Book all contained in wooden cabinet.

Frequency: 44.0 to 61.0 Mc/s.
Approximate Range: 3 to 8 miles.
Variable Tuning.
Power Requirements: Standard 120 v. H.T. and 2 v. L.T.

Ideal for Civil Defence and Inter-communications.
59 6 BRAND NEW.
Calibrated Wavemeter for same. 10-.

TRANSISTOR SIGNAL TRACER

Complete Kit with 2 Transistors. Components and Plastic Case. Phones with Circuit, 42 6.

INDICATOR UNIT TYPE 182A

Unit contains VCR517 Cathode Ray 6in. tube, complete with Mu-Metal screen, 3-EP50, 4-SP61 and 1 5U4G valves, 9 wirewound volume controls and quantity of resistors and condensers. Offered BRAND NEW (less relay) at 67 6. Plus 7 6 carr. "Radio-Constructor" scope circuit included.

TRANSISTOR SQUARE WAVE GENERATOR

Complete Kit with 2 Transistors. Components. Circuit and Plastic Case, 25-.

MINIATURE I.F. STRIP TYPE "373" 9-72 MEG.

Brand new miniature I.F. Strip size 10in. x 2 1/2in. x 3in. high. Valve line-up 2-EP50, 3-EP91 and EB91. With circuit.
Complete with valves 42 6.

F.M. CONVERTER UNIT 88 100 Mc/s.

Containing 6 valves—2 6BA6, EB91, VR137, 2-EP54. Two I.F. stages and separate local oscillator, graduated Vernier tuning. Just plug in to your radio and obtain good listening on F.M. Voltage required 250 v. 50MA. and 6.3 v. 2 amps. £7 19 6.

FIRST-CLASS TELEVISION and RADIO COURSES . .

GET A CERTIFICATE!

After brief, intensely interesting study—undertaken at home in your spare time—YOU can secure your professional qualification or learn Servicing and Theory. Let us show you how!

FREE GUIDE

The New Free Guide contains 132 pages of information of the greatest importance to those seeking such success compelling qualifications as A.M.Brit.I.R.E., City and Guilds Final Radio, P.M.G. Radio Amateurs' Exams, Gen. Cert. of Educ., London B.Sc. (Eng.), A.M.I.P.E.E., A.M.I.Mech.E., Draughtsmanship (all branches), etc., together with particulars of our remarkable Guarantee of

SUCCESS OR NO FEE

Write now for your copy of this invaluable publication. It may well prove to be the turning point in your career.

FOUNDED 1885—OVER

150,000 SUCCESSES

NATIONAL INSTITUTE OF ENGINEERING
(Dept. 462), 148, HOLBORN, LONDON, E.C.1.

ILLUSTRATED CATALOGUE No. 10

6d. post free (U.K. only)

56 pages, over 2,000 items, 135 photographic illustrations and technical data on brand new guaranteed components by leading manufacturers.

SOUTHERN RADIO & ELECTRICAL SUPPLIES

SORAD WORKS, REDLYNCH, SALISBURY, WILTS

Telephone: Downton 207

RADIO AND TELEVISION COMPONENTS

All parts in stock for:
Viewmaster, Soundmaster, Teleking, etc.

Easy Terms available.
21d. stamp (only) for Catalogue.

JAMES H. MARTIN & CO.
FINCHWATER, NEWBY BRIDGE,
ULVERSTON, LANC.

OSMOR CONVERTERS

ALL CHANNELS

Simple, efficient for all TV (including TRF). Guaranteed no break-through of Band I or re-radiation. Approx. 1 hr. to build. Will convert any Band III channel to any Band I channel. AC or AC/DC. Kit, £3.5.0. Ready wired, £4.0.0. Post free. Terms: C.W.O. Post orders only. THE ELECTRONIC SUPPLY CO., 29, Leigh Rd., Highbury, London, N.5

COVENTRY RADIO

Component Specialists
since 1925

We have now trebled the size of our premises in order to supply a larger range of Components, Amplifiers and Hi-Fi Equipment

Send your enquiries to:
189-191 Dunstable Road,
Luton, Beds.

New Telephone No.:
LUTON 7388-9

CORRESPONDENCE

The Editor does not necessarily agree with the opinions expressed by his correspondents. All letters must be accompanied by the name and address of the sender (not necessarily for publication).

BEGINNER'S GUIDE TO TV

SIR,—I feel that the title of the item "Duration of Vision" included in your current feature of "A Beginner's Guide to Television" is rather inapt. Duration of vision would more correctly be described as the length of time which the eye continues to "see" an image after the removal of that image. This property of the eye is of importance not only in the case of TV but also in the case of films where it is utilised to give a sensation of continuity.

As you so rightly state, it is extremely difficult to measure the minimum length of time in which the eye must be subjected to a stimulus for it to be "seen," and the situation is further complicated by the fact that the magnitude of the stimulus has also a bearing on what can or cannot be seen.—L. M. ARROW-SMITH (West Hartlepool).

SLOT AERIALS

SIR,—I was very interested to read your articles on "Slot Aerials," January and February, 1957, and also the letter on this subject from E. Lawton of Stoke.

As the materials were so cheap, although I am over 90 miles from the nearest I.T.A. transmitter I decided to make a Band III aerial. I had to hand a sheet of aluminium 36in. x 20in. and in this I cut a slot 27½in. x 5in. I used a 13½in. rod mounted on Perspex spacers in the slot as a matching device and mounted the whole on a wooden frame for outdoor use. I set the aerial up on my roof to face the Emley Moor transmitter, and I found that I could receive a powerful sound signal some 90 per cent. of transmission time, a picture which would not stay locked for 75 per cent., and a picture of entertainment value for about 50 per cent. of transmission time.

Spurred on by this I added a simple upright rod reflector to the slot about three weeks ago and I have found this to give some improvement. I also tried adding a director but this gave me a weaker signal I should imagine due to the aerial impedance not matching the feeder or set.

My biggest difficulty was in making a mounting for the aerial strong enough, as this design has a very high wind resistance.

I would have liked to try a Band I slot but my local transmitter is horizontally polarised and a slot would be rather cumbersome mounted vertically.

I hope this information may be of some interest to the writer of "Slot Aerials for Television."—J. W. DACHEY (Bircham Newton).

STRANGE SIGNAL PICK-UP

SIR,—I have been interested in the recent correspondence and would point out that I have met some similar instances, and think that many of these freak cases are due to reflections coupled with abnormal conditions. It is well known that conditions can be favourable or unfavourable to radiation (witness the reception of BBC in Australia and the cessation of telephone signals across the Atlantic, for

instance) and a signal from a certain direction may be reflected to a receiving aerial, but under poor or perhaps normal conditions there may be no signal present in that direction. On conditions when a signal is present it would be reflected and cause trouble, but its source would not be apparent due to the reflection. A case would be the police and similar services which could be heard in one house when conditions are right but not by a neighbour, so it would be no use asking neighbours if they had heard the interference.—G. DOUGLAS (Cardiff).

VALVE DESIGN

SIR,—I wonder if other readers have experienced a difficulty which I have met with, or whether I am unlucky. For some months now I have been keen on experimenting and to this end I have obtained a number of the novel based valves and the associated holders. I have found, however, that these have been a frequent source of trouble due to one or more of the pins failing to make good contact in the small

holders. These appear to be fitted with a thin edge type contact between the two faces of which the valve pins pass, but it appears that there is a tendency with some valves for the adjacent edges to turn and the springy nature of the material then makes them pass on each side of the pin, with the result that that particular pin has no contact. The trouble is sometimes aggravated by the spring contained screening cover made for the valve base which, when pushed down over the valve, holds it firmly perhaps in the "off" position. I discovered the trouble when an experimental hook-up failed to work as required, and although everything was checked and found in order no satisfaction could be obtained. The valve was going to be changed, and as the screening can was twisted to release it the circuit came to life and the trouble was traced as above. Since that date I have had dozens of cases where bad or no contact has resulted in a circuit not acting as required, and it depends, of course, upon which pin fails to make good contact. It would be interesting to hear whether other readers have had this experience, or whether I have just been unlucky.—G. GOODSON (N.W.).

INTERMITTENT FAULTS

SIR,—It is often stated that one of the serviceman's biggest bugbears is the intermittent fault. This is of a type which only occurs from time to time and accordingly one has to spend a long time waiting for it to turn up. Has anyone yet found a way of tracking such a fault? I am not over technical, but was thinking of this recently and had an idea which might help. If a device such as a relay, etc., is connected in place of the loudspeaker it could be so adjusted that it remained in a certain position whilst a steady note such as obtained from a signal generator was received. If the set suddenly went off, the relay could open (or close) and actuate some device such as a tester con-

ected in each anode circuit. If an alarm were also joined up, the service man would hear this and could immediately attend to the set and see by the anode indicators which stage was responsible and this would simplify matters. Is the idea practicable?—H. WELLS (Edgware).

THE RF.26 UNIT

SIR.—I have just finished testing out your Band III converter built round the ubiquitous RF.26 Unit and am more than pleased with the results. This is truly a wonderful ex-government unit, and I have used it to build at least 10 different sets. In not only your paper but in *Practical Wireless* and in other journals I have read of tuners, pre-amplifiers, etc., and I have used a single unit to make up most of these, pulling them down when a new design came out, but only now have I used it for TV. The same parts are used and I only found about three condensers which needed replacing, otherwise I have used most of the original parts. I wonder if any reader has had war-time experience of this unit and could let us know what it was used for, as I have been told that the Government incorporated it in several different designs also, as it was such a good piece of apparatus.—G. H. TREEBY (Harrow).

TESTMETER DESIGN PROBLEMS

SIR.—In the February issue you gave an article about Testmeter design, and I have for a long time been making up test sets built round ex-army meter units. There is one point, however, which appears a problem in connection with these meter movements, and it concerns the question of a fuse. I have burnt out more than one, and it seems to me that the makers could protect the instruments and

at the same time help the user by connecting the hair-spring to a small fitting which could carry a small plug-in fuse. This would make one connection, and the hair-spring could be so fixed that removal of the fuse would in no way affect the instrument, but in the event of an overload the fuse would blow and the meter remain undamaged. The fuse-holder could then be withdrawn and a new one (or suitable piece of fuse wire) replaced and the meter would be ready for further use. For those making up test sets I definitely recommend that a safe-guarding fuse be incorporated as a part of the design in such a lead that it is in circuit all the time.—R. B. REECE (Bradford).

STABLE CONDITIONS

SIR.—Some years ago we used to read your paper avidly to see what was new. This occurred also in radio, and one was continually hearing of new circuits and new applications. For years now there has been nothing new in radio (I exclude F.M., which is, of course, not new but merely the BBC development), and now for a long time television has been in the same position. Does this mean that the technicians have dried up or run out of ideas, or that the science has found its level. Surely it cannot be that, as both radio and television are far from "perfect." There must be lots of room for improvement, say, in timebase circuits to prevent drift and similar things, but I am surprised that all the experts seem to be doing now is simply putting transistors in place of valves and printed circuits in place of wires, but there is nothing really new in these. I am sure there must be hundreds like me longing for some new circuits to try out.—H. G. RYDER (Dover).

MAKING A KILO-VOLTMETER

(Concluded from page 525)

a decimal point followed by the number on the circular scale nearest its pointer—in the example, this is 65, making a reading of 4.65. (The decimal point may be omitted if desired.)

Calibrating the Instrument

To calibrate the spark-gap all that is necessary is to connect it to different known voltages and, for each voltage, to start with the gap wide open and gradually close it until it sparks over, reading the gap length from the two scales each time. Then the voltage is plotted against the gap length as can be seen in the chart on the instrument in the photograph. In connecting to the high voltage source, of course, the flying lead terminated in the crocodile clip should first be connected to the earth point and the probe then applied to the high voltage terminal.

If access can be obtained to a calibrated high voltage supply, the above process is simple. The average experimenter, however, is unlikely to be able to do so, but the EHT supply of a normal TV receiver, or a similar source, can be used instead. The voltage of this can be determined by connecting a suitable high resistance in series with a milliammeter across it and measuring the current; the meter, should, of course, be connected at the earthy end of the resistance. The resistance should have a value of up to about 50 megohms and may be composed of a number of smaller resistances in series, but it is

desirable to know the total value as accurately as possible, since it directly affects the accuracy of the calibration. The milliammeter should preferably read 0.1 mA or less. The required value of the voltage, in kilovolts, is then given by

$$\text{Kilovolts} = \text{megohms} \times \text{milliamps}$$

The addition of the resistance to a TV EHT supply will almost certainly reduce its voltage, but this does not matter so long as the spark gap voltmeter is applied whilst the resistance is in circuit. It does, in fact, enable different voltages to be obtained by using two or three different values of the resistor and thereby obtaining two or three calibration points for the chart. Since, for practical purposes, the calibration curve is a straight line above about 3 kV for this particular instrument, these points are sufficient to enable the whole curve to be drawn up to 20 kV or so by merely drawing a straight line through them.

It is convenient in use to stick a small-scale copy of the calibration chart to the body of the instrument, as seen in the photograph, but for greater accuracy the chart should be drawn to a larger scale.

"PRACTICAL TELEVISION CIRCUITS"

288 pages, 156 illustrations

15/- net or 15/6 by post from:

GEO. NEWNES LTD.

Tower House, Southampton Street, Strand, W.C.2

Presenting the new HOMELAB range of SIGNAL GENERATORS

TYPE 2

100 kc/s. to 100 Mc/s CW or 400~ modulation. Audio signal for amplifier tests PRICE : £4.10.0d., p. & p. 5/-

TYPE 12

100 kc/s. to 130 Mc/s. Sine and square wave modulation at 1,000~. Sine or square wave signal for amplifier tests PRICE £8.10.0d., p. & p. 5/-

TYPE 20

An AM/FM signal generator covering all modern radio and TV requirements up to 240 Mc/s PRICE £15.15.0d., p. & p. 5/-

Send stamp for full details of above, and also our Mullard FM Tuner complete with power supply PRICE : £12.0.0d.

HOMELAB INSTRUMENTS LIMITED

615-617, HIGH ROAD, LEYTON, LONDON, E.10

Telephone : LEYtonstone 6851

GUARANTEED VALVES

CV6	1/-	EL33	15/-	VR116	6/-	6R7	8/6
DET19	1/6	EL41	10/-	VR150/30	7/6	6SA7	8/-
DET25	5/-	EL42	10/-	VU111	2/-	6SH7	5/-
DF81	7/6	EL44	10/6	X85	10/-	6SK7	7/6
DF82	7/6	EL49	7/-	0Z4A	6/6	6SK7	7/6
DL92	7/6	EL91	8/6	1L4	7/6	6SL7	6/6
DL93	7/6	EM80	13/-	1T4	7/6	6SN7	7/6
DL95	7/6	EN91	7/6	1Q5	8/6	6SS7	5/-
EA50	1/-	EX11	11/6	1U5	7/6	6T8	9/6
EABC80	9/-	EZ35	8/-	2C34	3/6	6V6	7/6
EB34	2/6	EZ40	8/-	2D21	7/6	6X4	7/6
EB91	6/-	EZ80	8/6	2X2	4/-	8D2	4/6
EB93	9/-	FC13C	4/6	3A4	7/6	9D2	4/6
EBF80	9/-	HL13C	4/6	3Q4	7/6	12A6	7/6
ECC33	7/6	H63	7/6	4D1	4/-	12AH8	10/-
ECC35	7/6	KT33C	8/6	5U4	8/-	12AT7	7/6
ECC81	7/6	KT44	10/-	5Z4	8/6	12AU7	9/-
ECC82	9/-	KTW61	7/6	6AG5	6/6	12AX7	9/-
ECC83	9/-	RTW63	7/6	6AK5	6/6	12H6	2/6
ECC84	11/-	PL33	20/-	6AL5	6/6	12J5	5/-
ECH35	10/-	PL81	10/6	6AM6	7/6	12J7	7/6
ECH81	9/-	PL82	10/6	6AQ5	7/-	12K7	7/6
ECH42	10/-	PY80	9/-	6AT6	8/-	12K8	17/6
ECC82	11/-	PY81	8/6	6AU6	7/-	12Q7	7/6
ECL40	9/-	PY82	8/6	6BE6	8/-	12SC7	7/6
EC52	5/-	PCF80	9/6	6BA6	8/6	12SG7	5/-
EC54	5/-	PCF82	10/-	6BC5	6/6	12SH7	5/-
EC90	6/-	PC81	10/-	6BH6	7/6	12SJ7	5/-
EF36	7/6	PC84	11/6	6BR7	8/6	12SK7	5/-
EF37A	10/-	PCL82	10/-	6BS7	8/6	15D2	5/-
EF39	6/-	PEN46	8/6	6BW6	8/6	35L6	9/-
EF41	10/-	P61	5/-	6BX6	8/6	35Z4	8/6
EF42	10/-	PZ30	15/-	6B8	5/-	45	6/6
EF50	5/-	RK34	2/6	6C4	6/6	58	5/-
EF54	7/6	RL37	5/-	6F32	5/-	76	5/-
EF55	9/-	SP13C	4/6	6F33	7/6	85A2	9/-
EF80	8/6	SP41	5/-	6G6	5/-	90C1	8/-
EF85	10/6	SP61	5/-	6H6	2/6	807	7/6
EF91	7/6	U301	20/-	6J5	3/-	829	40/-
EF92	5/6	TT11	4/-	6J7	7/6	832	30/-
EF94	7/-	UBC41	10/-	6K7	5/6	954	5/-
EF95	6/6	UF41	10/-	6K8	8/6	955	5/-
EF96	6/6	U9	20/-	6L6	10/-	7153	3/-
EF98	8/6	UL46	10/-	6N7	7/6	8012	6/6
EK90	8/-	UY41	8/-	6P28	20/-	9001	5/-
EL32	6/6	VP13C	4/6	6Q7	8/6	9003	5/-

Post & Packing 6d. Free over £1. C.O.D. 2/6 extra.

LAWRENCE ELECTRONICS
158, CHIPSTEAD VALLEY ROAD, COULSDON, SURREY.
UPLANDS 9075. Personal callers preferably on Saturdays.

MULLARD TAPE AMPLIFIERS

We stock all the components for the Amplifiers as described in the Mullard Tape Recording Booklet.

RESISTOR KITS. LAB. All fixed and variable resistors as specified. Model A, 33/3. Model B, 31/9.

CONDENSER KITS. Model A, 33/3. Model B, 35/3. These kits are made up for the Brenell and Collaro Decks. If Lane or Truvox Decks are being used this must be stated when ordering.

OUTPUT TRANSFORMERS. Gilson OP767, 25/6. Elstone OT/3, 21/6. Partridge SVO/1, 60/6.

ELCOM PLUGS AND SOCKETS. PO4 Chassis Plug, 3/6. S04T Flex Socket, 5/3.

IGRANIC JACK SOCKETS. P71, 3/4. P72, 3/10. Bulgin Jack Plugs to fit, 3/6.

BELLING LEE PLUGS AND SOCKETS. Speaker Sockets. L316 Red and Black, 1/- each. L378 Plugs to fit, 10d. each. Co-Ax Socket L734S, 1/- L604S, 1/3. L734 Plugs to fit, 1/3 each.

MCMURDO VALVE HOLDERS. BM9/U, 10d. XM9/UC1, 1/7. XM9/UG1, 2/3.

SWITCHES. Set of three for Model A, 32/6. One Switch for Model B, 16/6.

BULGIN TAG BOARDS. C120, 1/3. C125, 2/3.

EQUALISER PLUG AND SOCKET. Plugs 2/3 each. Socket, 6d.

CERAMIC STAND OFF PILLAR. 1/- each.

OSCILLATOR COILS. Brenell, 8/6. Truvox TR98, 6/9.

CHASSIS. Denco. Fully drilled. Model A, 31/6. Model B, 31/6.

VALVES. EF86—Mullard, 24/4; Alternative, 15/6. ECC83—Mullard, 19/6; Alternative, 10/6. EM81—Mullard, 18/1. EL84—Mullard, 16/6; Alternative, 12/6. OA71 Diode, 6/6.

KNOBS.—Bulgin K370, 1/6 each. EM81 ESCUTCHEON, 2/6.

SUNDRIES KIT. Contains all nuts, bolts, tags, wire, flux solder, etc., 8/6.

FULLY DETAILED LIST is available free upon request. This gives prices for complete kits and details of Power Unit Components.

WATTS RADIO

8, Apple Market, Kingston-on-Thames, Surrey

Telephone : KINGston 4099

TECHNICAL TRADING CO.

ION TRAP MAGNETS, 4-. FOCUSING MAGNET ASSEMBLIES, wide angle, centring control, 9/6. **DITTO**, latest twin magnet, 12/6. **12 VOLT 4 AMP SELENIUM RECTS.** 9/6 each, 25 doz. **GOODMANS P.M. SPEAKERS**, 5in., 17- 6in., 18- 7 x 4, 17/6. 6in. (F.M. Quality), 22/6. 10 x 6, 26- 10in., 25-. **NEW CONDENSERS**, 10 pF-5 mfd., our assortment, 50 for 6/6. 100 for 12- **WIDE ANGLE TRANSFORMER KITS:** (a) Line Trans. 14 Kv., ceramic base. EY51 mountings, ferroxcide core, 17/6 with instructions. (b) Frame Trans. for ECL80, 9/6. (c) 250 ma 7H Smoothing Chokes, 7/6. **COMPLETE KIT AS ABOVE**, 30-. With Coils to match, 4- ea. **VISCON COND.**, .002 mfd., 18 Kv., 4/9. **DEFLECTION COILS**, Standard 35 mm., iron cored, 9/6. **BOWLER HATS**, 1- **PRE-SET POT.**, 500 Ω , 1 K, 2.5 K, 5 K, 10 K, 20 K, 25 K, 50 K, 2- ea. **AMPHIPHON HOLDERS**, Octal, Mazda, Novol, B7G, B9A, 6- doz. B9G W/Screen. 1/6 ea. Tube Holders, Octal, 6d. Duodecal, 1-.

13 CHANNEL CONVERTERS, famous make, complete PC84, PCF80, beaut. bakelite cabinet, adjustable all I.F. freqs., £3.15. **GERMANIUM CRYSTAL DIODES**, famous make, tested, general purpose, polarity marked, 10d., p. & p. 3d., 8/6 doz.


GUARANTEED BOXED RADIO VALVES, 24 HOUR SERVICE.

5Y3GT	6/6	6K7GT	5/6	12AX7	8/6	ECF80	12/6	HVR2A	8/6
5U4G	6/6	6K7M	6/6	12K7GT	7/6	ECH42	9/6	KT81	8/6
6A3	9/6	6H6M	2/6	12Q7GT	7/6	ECL80	8/6	P61	2/6
6AC7	6/6	6L6G	8/6	25L6GT	8/6	EF36	4/6	PC84	7/9
6AG5	4/9	6L6M	9/6	35Z4GT	7/6	EF37	7/6	PC85	11/6
6AG7	9/6	6SA7	7/6	80	2/6	EF37A	9/6	PCF80	8/6
4-6AK5	4/9	6SCTM	5/6	83	7/6	EF38	5/6	PEN25	5/6
6AM6	7/6	6SJ7	7/6	807(E)	3/9	EF50	2/6	PL82	8/6
6B7	8/6	6SK7GT	5/6	807(AM)	5/6	EF50 red	3/6	PY80	8/6
6BA5	6/6	6SL7GT	6/6	896A	11/6	EF80	8/6	PY81	8/6
6BE3	6/6	6SN7GT	5/6	CI(Barr)	12/6	EF85	9/6	PY82	7/6
6C4	4/9	6V6G	6/6	6- C1C	12/6	EF89	9/6	SP4B	2/6
6C5GT	6/6	6V6GT	6/6	6- C1C	12/6	EF91	7/6	SP41	2/6
6C6	5/6	6V6M	6/6	6- EB34	1/6	EF92	5/6	SP61	2/6
6D6	5/6	6X4	6/6	6- EBC33	7/6	EF95	8/6	SP210	3/6
6P6G	6/6	6X5GT	5/6	6- EC52	4/6	EL32	5/6	U22	7/6
6F33	9/6	6B7	7/6	6- ECC31	9/6	EL81	4/6	U32	6/6
6J5M	5/6	6C5	7/6	6- ECC81	8/6	EL91	4/6	U32	6/6
6J5GT	4/6	6D9	6/6	6- ECC82	7/6	EY51	10/6	UCH41	9/6
6J5G	3/6	6- 12A6M	6/6	6- ECC83	8/6	EZ40	7/6	UY41	9/6
6L6	5/6	6- 12AT7	7/6	6- ECC84	11/6	EZ83	8/6	VR150	30 3/9
5J7G	5/6	6- 12AU7	7/6	6- ECC85	9/6	CT1C			

Postage 1/- in £1 (19 in £1 Speakers Trans.) Min. 6d. No. C.O.D., 10,000 OTHER BARGAINS TO CALLERS AT :-

350/352 FRATTON ROAD, PORTSMOUTH
PORTSMOUTH'S RADIO, TV AND TOOL SHOP

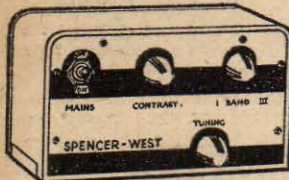A SPENCER-WEST BAND III CONVERTER FOR £6.5.0




The Type 80 with printed circuits, panel controls for Band switch and fine tuning and a performance which ensures enthusiastic satisfaction. Handsomely designed and finished to stand on your receiver with its self-contained power supply it just plugs straight in.

From your dealer or post free from the manufacturers:

SPENCER-WEST LTD.,
Quay Works, Great Yarmouth,
Norfolk.

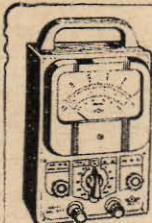*Phones: Works 4794; Sales 3009
Grams: Spencer-West, Great Yarmouth.
Leaflets gladly sent.



PULLIN SERIES 100 TEST METER

AC/DC 10,000 Ω /V
21 RANGES
100 μ A to 1000 V
COMPLETE IN DIE-CAST
CASE WITH TEST LEADS
CLIPS AND PRODS
FULLY GUARANTEED

SENT POST FREE FOR £2.10.0 AND
NINE FURTHER MONTHLY PAYMENTS
OF £1.4.6. CASH PRICE £12.7.6.

FRITH RADIOCRAFT LTD
69-71 CHURCH GATE LEICESTER
& 23 HIGH ST NEWPORT MAGNELL Bucks

TELEVISION COMPONENT SERVICE

Replacement components available for
the popular home constructor designs.
Catalogue available on request.

J. T. FILMER Maypole Estate,
Bexley, Kent.
Tel.: Bexleyheath 7267

TRANSFORMERS?

CONTACT **Forrest** FIRST!

Rewinding and manufacture of all types
for Television Radio and Electronic
Application.

FORREST (TRANSFORMERS) LTD.,
Shirley, Solihull, Warwickshire.
Phone: SH1. 2483. Est. 34 years.

EDDY'S (Nottm.) LTD.

172 ALFRETON ROAD, NOTTINGHAM

OUTSTANDING BARGAIN!

A FEW ONLY COLLARO RC54, 3-SPEED AUTOCHANGE
UNITS CRYSTAL TURNOVER CARTRIDGE. NEW &
GUARANTEED, 200-250 volts A.C. £7.19.6.

Postage and Packing 5/- each.
RECORDING TAPE—1,200ft. reels. THE AMAZING PRICE
OF 9/11 each.

Postage, etc., 1/- Limited Quantity.

Postage and
Packing
6d. per valve
over £2
FREE

VALVES

ALL NEW & GUARANTEED

Any parcel
insured against
damage in
transit
6d. EXTRA

IR5	7/3	6X5GT	7/6	954	1/6	EF85	11/6
IS5	7/3	787	7/11	955	3/11	EF89	9/6
IT4	7/3	7C5	7/11	956	2/11	EP91	7/11
354	7/3	7C6	7/11	958	3/11	EL32	5/11
3V4	8/3	7H7	7/11	9003	5/3	EL84	10/3
5U4G	7/11	757	8/11	DAF96	9/6	EX51	9/6
5Y3GT	7/6	7Y4	7/11	DP96	9/6	EY86	10/3
5Z4G	8/3	12AH8	10/6	DK96	9/6	EZ80	8/3
6AT6	7/11	12K7GT	9/6	DL96	9/6	PEN46	5/11
6BA6	7/3	12K7GT	8/11	DM70	7/11	PC84	10/11
6B6	7/11	12Q7GT	9/3	EAB80	7/6	PCF80	9/11
6B8G	3/6	1A57	10/6	EB91	6/11	PCL83	11/9
6F1	12/11	19A05	11/6	EBF80	9/6	PL81	11/6
6F15	12/11	25L6GT	8/6	ECC81	8/11	PL82	8/11
6J5M	3/11	25Z4G	8/11	ECC82	7/6	PL83	11/6
6K7G	2/11	35A5	10/6	ECC83	8/3	PY81	8/3
6K8GT	9/6	35L6GT	8/11	ECC84	10/11	PY82	8/3
6Q7GT	8/3	35W4	8/11	ECC85	9/6	UBC41	8/11
6SN7GT	7/11	35Z3	10/3	ECH35	9/6	UL41	9/11
6V6GT	5/11	35Z4GT	8/3	ECH81	8/11	UL84	9/6
6X4	6/11	60L6GT	8/6	ECL80	8/11	UY41	7/11
		807	3/11	EF80	8/3	VU111	1/6

TELEVISION RECEIVING EQUIPMENT

30/-. By W. T. Cocking. Postage 1/-

THE RADIO AMATEUR'S HANDBOOK. By A.R.R.L. 1957. 32/6.
Postage 1/6.

TELEVISION EXPLAINED. By
W. E. Miller, revised by E. A. W.
Spreadbury. 12/6. Postage 9d.

T.V. FAULT FINDING. A Data
Publication. 5/-. Postage 4d.

RAPID TV REPAIR. By G. W.
Heath. 23/-. Postage 1/6.

THE V.T.V.M. By R. Samuel.
How it works. How to use it. 20/.

**MAINTAINING HI-FI EQUIP-
MENT.** By J. Marshall. 23/.

RADIO VALVE DATA. Compiled
by "W.W.V." 5/-. Postage 6d.

The MODERN BOOK CO.

BRITAIN'S LARGEST STOCKISTS
of British and American Technical Books

19-23 PRAED STREET,
LONDON, W.2

Write or call for our catalogue.

Phone: PADddington 4185.

Open 6 days 9-6 p.m.

SETS & COMPONENTS

CONDENSERS, var. spindled ceramic, 15, 25 or 50 pfs., 1/3; 75 pfs., 1/6; butterfly, 25 pfs., 1/6. Suppressors, radio interference, ex-A.M., 5/6 (post 2/-). Brand new RF 26, 27, 27/6 (postage 2/6); RF25, 10/6. Dynamotors (post 3/-); 12v. to 250v. 65 mA. and 6.3v. 2.5 A., 10/6. Eddystone, 12v. to 190v. 75 mA., cased, 15/-. Metal Rectifiers: 600v. 30 mA., 6/-; 500v. 500 mA., 10/6; 240v. 30 mA., 3/6; 1,000v. 30 mA., 7/6; 700v. 80 mA., 7/6. R1155 S.M. Tuning Drives, "N" type, brand new, 10/6. Chokes, L.F. Ferranti, 10H, 120 mA., 8/6. Screened, 7/6; 10H, 200 mA., 8/6; 5H, 200 mA., 4/6; "C" core, 10H, 130 mA., 12/6. Bond Testers (Record), 0-0.10, 30/. Power Packs, input A.C. 230v., outputs 150v. 16 mA., D.C., and 4v. 1.1 A., A.C., 17/6 (p.p. 3/-). Bel/Lea spigotted Plugs, 5 pin, Fem., 6d; mated 7 pin, 1/6 pr.; 10 way, 2/6. Switches, wafer, 1 pole 6 way, 1 bank, 1p 11w 1b, 1p 8w 1b, 1p 3w 3b, 2p 3w 2b, 4p 2w 1b, 1p 6w 5b, 1p 6w 2b, 2/6; 1p 11w 2b, 6p 2w 4b, 3/6. Ceramic: 3p 4w 2b, 4/6; 2p 5w 1b, 3/6. Stud type, 1p 10w 2b, 4/6; 1p 24w 2b, 7/6. Condensers: Bakelite tub. 0.1mfd, 1.2kV, 1/-; 0.03, 2.5kV, 1/3; 0.05, 3.5kV, 0.25, 1.5kV, 1/6. List and enquiries, S.A.E. please! Terms: c.w.o. Postage extra. Immediate despatch. W. A. BENSON (PT), 136, Rathbone Road, Liverpool, 15.

TELEVISION, 12in., 5 channel, tunable anywhere, models for £25 each, carriage paid; guaranteed perfect. RYAN ELECTRICS, 134, Acre Lane, Brixton, London, S.W.2. (BRI 4533.)

I.T.V. CONVERTERS from £19/6, self-contained, guaranteed. H.P. without fuss. Aerials from 14/6. Trade enquiries invited! G. A. STRANGE, Dept. P, North Wrexham, Chippendale, Wilt.

SEVERAL EARLY MODELS, 9in. Television, complete and mostly working, £5/5 each, carriage paid. TOMLINS, 127, Brockley Rise, Forest Hill, S.E.23. (FOR 5497.)

TELEVISION, 9in. models, £7/10/-; 12in. models, £15; all makes; working; carriage paid. TOMLINS, 127, Brockley Rise, Forest Hill, S.E.23.

AERIALITE CONVERTABLES (McMichael) Band 3 Converters, Channels 6 to 13, including beautiful walnut table, list price £18/18/-, £10/15/-; carriage paid (makers' guarantee), money back guarantee. TOMLINS, 127, Brockley Rise, S.E.23.

TELEVISION, 12in. Televisions, £13/10/- each, carr. paid. TOMLINS, 127, Brockley Rise, Forest Hill, S.E.23. (FOR 5497.)

TELEVISIONS, 12in., 5 Channel, £19/10/-; guaranteed; carriage paid. TOMLINS, 127, Brockley Rise, Forest Hill, S.E.23.

5-CHANNEL TELEVISIONS: 12in. screen Ferguson 988, Ekco 161, etc., £25 each. A good selection of 12in. T.V.s (London), 100% condition, from £15; 9in. from £7. Also 12in. T.V.s, slight faults, from £7, 9in. from £4. TYLER TELEVISION, 63, Lee High Rd., Lewisham, S.E.13. (LEE 5979.)

ELECTRADIO, Dual Wave Coil 2/6 with circuit, ditto, plus Reaction 4/- Tuning Condenser 3/10, Crystal Diode 1/6, tested 4 Transistor Set Circuit 1/3. All Transistor Components stocked. Post free. 18, Broadlands Av., Keynsham, Somerset.

TELEVISION, 10in., London models, good working order, £7 each, carriage paid. RYAN ELECTRICS, 134, Acre Lane, Brixton, London, S.W.2. (BRI 4533.)

LOUDSPEAKERS repaired promptly. MODEL LOUDSPEAKER SERVICE, Bullington Rd., Oxford.

RATES: 4/- per line or part thereof, average five words to line, minimum 2 lines. Box No. 1, extra. Advertisements must be prepaid and addressed to Advertisement Manager, "Practical Television," Tower House, Southampton St., Strand, London, W.C.2.

IDENTIFICATION UNITS REF No. 1, ZC.13312, each 27/6, plus carr. (7/6), all as new and complete with free data for conversion to T.V. Each unit contains many useful components and the following valves: one 524G, one VR54, five VR65, two VR66, three VR92, one CV63 and one VR137, in totally enclosed case. From J. A. B. JACOBSEN LTD., 22, Ritherdon Rd., Balham, London, S.W.17.

F.M. AERIALS direct from manufacturers, examples. Indoor Telescopic Dipole with mast and base, 15/-, Indoor "H" with mast and base, 22/6. T.V. Indoor Combined 1 and 3 Bands, 5 elements, 20-mile range, 35/-, T.V. Indoor Band, 3 only, 27/6. All post free. Low loss Cable, very cheap if ordered with above. Aerial parts, lists and data 1/-. Special terms to aerial erectors. Write for details. SKYLINE WORKS, Burnall Rd., Coventry. (Tel. 60418.)

GUARANTEED TELEVISION, 12in. models, first-class picture, 5-channel, £26 each, carriage paid. THE GRAMOPHONE SHOP, 19-21, Brockley Rise, Forest Hill, S.E.23.

T.V. TUBES, High emission reclaimed. As supplied to trade throughout the British Isles, 14in. £5; 15/16in. £5/10/-; 12in. £6. Guaranteed 6 months, 12in. (short supply) £5, guaranteed 3 months. The finest value ever offered in T.V. Tubes. TELETTUBES, 34 & 18, Market Parade, Rye Lane, Peckham, London, S.E.15.

TELEVISIONS, Large range 9in.-10in. models, needing repair, £4/10/-, carriage paid, 12in. Televisions needing repair, £6/6/-, carriage paid, immediate despatch. 13in. Televisions and Philips projection models needing repair, £11/10/-; immediate despatch. BARKERS, 325, Brockley Road, Brockley, S.E.4. (TID 6752.)

SITUATIONS VACANT

AEROPLANE AND ARMAMENT EXPERIMENTAL ESTABLISHMENT, Boscombe Down, requires skilled men to serve as: Instrument and Electrical Craftsmen, Radio/Radar and Electronic Craftsmen for laboratory and aircraft installations work; Airframe and Engine Fitters for aircraft servicing and fitting of special equipment; Fitters and Turners for research workshops. Rate of pay on entry for 44 hour 5 day week 17/4 plus 10/- merit lead or 17/4 plus 38/- merit lead according to experience. Prospects of re-assessment of rate within three months, any increase backdated to date of entry, merit lead can rise to 70/-. Two weeks (88 hours) paid annual leave. Paid sick leave scheme. Apply giving details of apprenticeship and experience to AIR COMMODORE, Commanding (Civilian Administration Office) (P.T.), A. & A.E.E., Boscombe Down, Amesbury, Wiltshire.

COILS T.R.F. M & L 4/6 pair
COILS T.R.F. IRON CORE
M & L 5/6 pair
LOUD SPEAKERS

5" 17/6 — 8" 19/6

Send S.A.E. for lists of Components, Kits, etc.

BERNARDS ELECTRICAL INDUSTRIES Ltd.

99, Kingsley Road, Hounslow, Middlesex.

TELEVISION AND TUBE BARGAINS.

—12in., 5-channel T.V., tunable anywhere, from £18/10/-; good emission S/H Tubes (12in., 14in., 15in., 16in., 17in.), £5 each; 12in. T.V., faulty, £7/10/- each; most makes. (Phone: Labrooke 1734.) Call 1070, Harrow Road, London, N.W.10; 300 yds. from Scrubs Lane.

FOR SALE

MAKING YOUR OWN? Telescopes, Enlargers, Binoculars, Microscopes, Projectors, or, in fact, anything that needs lenses. Then get our booklets "How to Use Ex-Gov. Lenses & Prisms," Nos. 1 & 2, price 2/6 ea. Also our stereo book, "3-D Without Viewers," price 7/6. Comprehensive list of lenses, optical, radio and scientific gear free for s.a.e. H. W. ENGLISH, Rayleigh Road, Hutton, Brentwood, Essex.

SUPERSONIC SUNLAMPS, listed £7/10/-; 80/-, S.A.E. SCIENTIFIC PRODUCTS CO., Croyley, Lancs.

VIEWMASTER Line Transformer W.B.107; Auto Mains Heater Transformer W.B.103A; both unused. Offers? Box 193, c/o PRACTICAL TELEVISION.

VIEWMASTER 12in. Console Channel 1, little used, any reasonable offer considered. Write Box 192, c/o PRACTICAL TELEVISION.

PAM CONVERTER (universal) with makers' guarantee, shop sold, £6/15/- (originally £9/9/-), 107, St. Paul's Road, N.I.

SALE, Closing down. New Playtime and recorders, £21. A/D/C record player £14/10/-; Baffleite 43/-; Ovenette 70/-; Soil Heater 20/-; M.R. Heat Meter £3. H.P. terms, s.a.e. for list, WILLIAMS, 13, Woodchurch Lane, Birkenhead.

SERVICE MANUALS/SHEETS, Tel./Radio for hire, sale and wanted. S.A.E. enquiries, W. J. GILBERT (PT), 24, Frithville Gardens, London, W.12.

WANTED

ALL TYPES OF VALVES REQUIRED for cash. State quantity and condition. RADIO FACILITIES LTD., 33, Chalcot Road, N.W.1. (PRImrose 9090.)

WANTED, Valves E.V.1, 6CH6, 10F1, PL81, KT61, 6F1, FW4/500, 20W2, 20F2, 10P14. Prompt cash. W.M. CARVIS, LTD., 103, North St., Leeds 7.

EDUCATIONAL

INCORPORATED Practical Radio Engineers' home study courses of Radio and TV Engineering are recognised by the trade as outstanding and authoritative. Moderate fees to a limited number of students only. Syllabus of Instructional Text is free. "The Practical Radio Engineer" journal, sample copy 2/-, 6,000 Alignment Peas for Superhets, 5/9. Membership and Entry Conditions booklet 1/-. All post free from the SECRETARY, I.P.R.E., 20, Fairfield Road, London, N.8.

FREE! Brochure giving details of Home Study Training in Radio, Television and all branches of Electronics. Courses for the Hobby Enthusiast or for those aiming at the A.M.Brit. I.R.E. City and Guilds, R.T.E.B., and other professional examinations. Train with college operated by Britain's largest Electronics organisation. Moderate Fees. Write to E.M.I. INSTITUTES, Dept. PT28, London, W.4.

LEARN IT AS YOU DO IT—we provide practical equipment combined with instruction in Radio, Television, Electricity, Mechanics, Chemistry, Photography, etc. Write for full details to E.M.I. INSTITUTES, Dept. PT47, London, W.4.


Practical, up-to-date books for daily reference—

TELEVISION PRINCIPLES AND PRACTICE

F. J. Camm

(Editor of this Journal)

2nd Edition

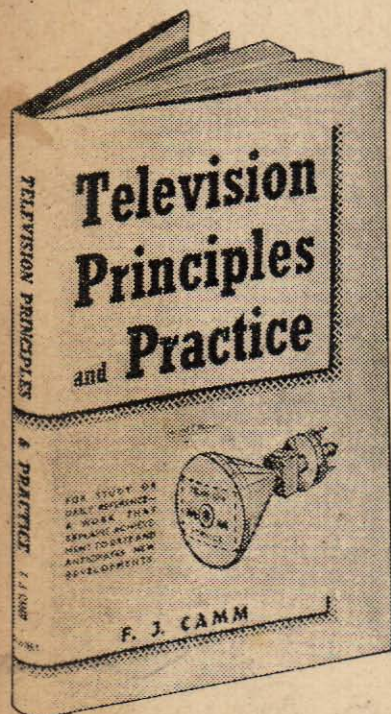

WRITTEN by one of the leading technical authorities of the day this handbook is a necessity for everyone interested in television—technician, student and amateur.

Some of the Contents include : The B.B.C. Television System—The Television Camera—From Transmitter to Receiver—Projection Receivers—Stereoscopic and colour Television—Time Bases—D.C. Receivers—Aerials—London-Birmingham Converter—Servicing—Interference—A Pattern Generator—Choosing a Receiver—Dictionary of Television Terms.

"The technician and the student will find this book invaluable."
Manchester Daily Dispatch.

25s. net.

(26s. post free)

T.V. CONVERSION FOR I.T.A.

C. E. Lotcho

THIS book gives details of converter units and full information for fitting them to a wide range of receivers, produced by nearly 30 television manufacturers. Over 100 illustrations and circuit diagrams are used to make all stages of the work quite clear and there are valuable chapters on conversion methods ; aerials and interference and suppression. Demy 8vo.

25s. net.

(26s. post free)

TELEVISION ENGINEERS' POCKET BOOK

Edited by E. Molloy and J. P. Hawker

Contains—240 pages of valuable Servicing information :—70 pages of tabular matter ; 201 illustrations ; data on more than 300 post-war T.V. receivers ; Panel of Specialist contributors.

10s. 6d. net.

(11s. 3d. post free)

From all booksellers or in case of difficulty at post free rates direct from the publishers.

**GEORGE NEWNES LIMITED,
TOWER HOUSE,
SOUTHAMPTON STREET,
LONDON, W.C.2.**



NEWNES

BAND III AERIALS OR FITTINGS

Whether you are contemplating the construction of a Band III aerial or purchasing one complete it will be well worth your while to write to us who, as manufacturers, can offer you real

VALUE FOR MONEY

THE FOLLOWING IS A CROSS SECTION OF ITEMS TAKEN FROM OUR NEW COMPREHENSIVE CATALOGUE.

- * 10 Element Band III Aerial, 77/6.
- * 8 Element Band III Aerial, 62/6.
- * 6 Element Band III Aerial, 47/6.

FITTINGS

- * Universal Band III Clamp-on Fitting.
- * Band III Insulator, complete with folded dipole.
- * Director and Reflector Rod Holders for Bands I, II, and III.
- * Straight and Cranked Masts (all sizes).
- * Chimney and Wall Brackets. Alloy Tubing, etc. etc.

Send 1/- P.O. for the NEW MULTI-PAGE illustrated Catalogue (together with element and boom measurements (all Bands) to help the constructor) to :

FRINGEVISION LTD. MARLBOROUGH, WILTS.

Phone 657/8

ARTHURS HAVE IT!

LARGE STOCKS OF VALVES and C.R.T.s. METERS, Avo, Advance, Taylor and Cossor Oscilloscopes in stock. AMPLIFIERS, Leak, Trix & Quad. GRAM UNITS, Garrard & Collaro. Collaro TRANSCRIPTION UNIT 2010PX.

LOUDSPEAKERS, Goodmans, Wharfedale, WB, Tannoy and leading makes. PICK-UPS and STYLII of most makes. TAPE RECORDERS, Grundig, Philips, Truvox, Playtime & Ferrograph.

LATEST VALVE MANUALS

Mullard, 10/6; Osram & Brimar No. 6, 5/- each; Osram Part 2, 10/-.

Postage 9d. each extra.

PARTICULARS ON REQUEST.

Terms C.O.D. OR CASH with order.

Arthur's

PROPS: ARTHUR GRAY, LTD.

OUR ONLY ADDRESS: Gray House

150-152 Charing Cross Road, London, W.C.2


TELEPHONE: 5833/4 and 4765

TELEGRAMS—"TELEGRAY, WESTCENT, LONDON."

CABLES—"TELEGRAY," LONDON.


SIGNAL GENERATOR

Coverage 120 Kcs-230 Kcs, 300 Kcs-900 Kcs, 900 Kcs-2.75 Mcs, 2.75 Mcs-8.5 Mcs, 8 Mcs-28 Mcs, 16 Mcs-56 Mcs, 24 Mcs-84 Mcs. Metal case 10in. x 6in. x 4in. Size of scale, 61 x 3in. 2 valves and rectifier. A.C. mains 230-250 v. Internal modulation of 400 c.p.s. to a depth of 30 per cent., modulated by slow-motion R.F. output continuously variable 100 milli-volts. C.W. and mod. switch, variable A.F. output and moving coil output meter. Grey hammer finished case and white panel. Accuracy plus or minus 2%. £4.19.6 or 34/- deposit and 3 monthly payments 25/- P. & P. 4/6 extra.

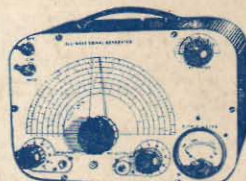

SIGNAL & PATTERN GENERATOR

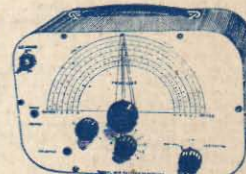Coverage 7 Mcs-210 Mcs in five bands, all on fundamentals, all on modulation tuning, audio output, 8 vertical and horizontal bars, logging scale. In grey hammer finished case with carrying handle. Accuracy = 1%. A.C. mains 200-250 v.




£6.19.6. Or £3 deposit and 3 payments of 30/- P. & P. 5/6

COMMERCIAL TELEVISION CONVERTER SUITABLE ANY T.V. EXCEPT PHILIPS ALL CHANNELS NO ALTERATIONS TO SET

Complete with built-in power supply, 230-250 v. A.C. mains. Or crackle finish case 5in. long, 3in. wide, 4in. high. Incorporating gain control and band switch. Illustrated with cover removed.

£3.19.6 Plus P. & P. 2/6.

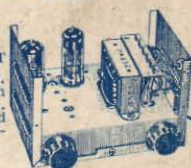SPECIAL OFFER FOR ONE MONTH ONLY.—3 element folded dipole loft aerial, 12 yds. co-ax. cable and 2 co-ax. plugs, if purchased together with Converter 12/6 plus P. & P. 2/6.



FAMOUS MAKE

TURRET "TELETUNER"

Covers all Channels, Bands 1 and 3. Valves used: PCC84, R.F. double triode, cascade R.F. amplifier, PCF80, triode pentode i.c. and mixer. I.F. output 33-38 Mcs. Easily modified to other I.F. outputs. Full instructions and circuit diagram supplied. Complete with 12 Coil Sets 99/6 post 2/6 Knobs, 3/6.

BATTERY CHARGER 6 or 12 v. 4 amp.

A.C. Mains 200-250 v. Fitted ammeter, selector switch, fuses, battery clips, indicator lamp. Incorporating G.E.C. Metal Rectifier. Ready for use. In grey hammer finish case. Wall fixing. 59/6 P. & P. 3/6


T.R.F. KIT IN PLASTIC CABINET

3 valve plus metal rectifier. A.C. mains 200-250 v. Medium and long waves. In pastel blue or brown. Valve line-up: 2 VR65S and VT52. Size 15in. long by 9in. high by 7in. deep.

£3.19.6. P. & P. 4/6.

A point-to-point wiring diagram, 1/6. Free with complete kit.

All parts supplied separately.

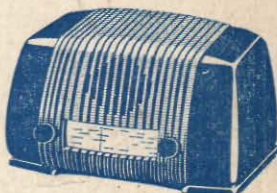

1,200 ft. RECORDING TAPE on plastic spool, 12/6. P. & P. 1/- MAINS TRANSFORMER. Primary 110-250, Secondary 0-120-180-230 v. 63 mA. 6.3 v. 3 amp., 10/8. P. & P. 2/- S.M.F.D. 450 WKG. CAN. size 2in. x 1in. 1.3 each, 12/- doz. T.V. COILS, moulded former, 2iron cores, all can. 2in. x 1in., 1/- As above single coil, 1in. x 1in., 9d. Semi air spaced co-ax. cable 6ft. yard, 12 yards 6/- P. & P. 1/6. 50 yards 25/- post free.

RADIO & T.V. COMPONENTS (Acton) LTD.

23, HIGH STREET, ACTON, LONDON, W.3

GOODS NOT DESPATCHED OUTSIDE U.K.

C.R.T. ISOLATION TRANSFORMER

Type A. Low leakage windings. Ratio 1:1.25 giving a 25% boost on secondary.

2 v., 10.6; 4 v., 10.6; 6 v., 10.6; 10.6 v., 10.6; 13 v., 10.6.

With main primaries, 12/6 each.

Type B. Main Input 220/240 volts. Multi Output 2, 4, 6.3, 7.5, 10 and 13 volts. Input has two taps which increase output volts by 25% and 50% respectively. Low capacity, suitable for most Cathode Ray Tubes. With Tag Panel, 21" each.

Type C. Low capacity wound transformer for use with 2 volt Tubes with falling emission. Input 220/240 volts. Output 2-21-21-23 volts at 2 amps. With Tag Panel, 17/6 each.

NOTE.—It is essential to use mains primary types with T.V. receivers having series-connected heaters.

TRIMMERS Ceramic. 30, 50, 70 pf., 9d. 100 pf., 150 pf., 1.3; 250 pf., 1/8; 500 pf., 750 pf., 1/8.

RESISTORS. All values. 10 ohms to 10 meg., 1 w., 4d.; 1 w., 8d.; 1 w., 8d.; 2 w., 1/8.

HIGH STABILITY. 1 w., 1/2. Preferred values 100 ohms to 10 meg.

WIRE-WOUND RESISTORS (1/3 10 watt; 25 ohms—10,000 ohms) 1/6

15 watt 15,000 ohms—50,000 ohms, 5 w., 1/9; 10 w., 2/3

12/6 PURETONE RECORDING TAPE

1,200 ft. on standard fitting, 7" Plastic

rolls. Brand new, boxed, 12/6.

Spools 5" metal, 1/6; 7" plastic, 4/3.

FERROVOICE 1,200ft. Plastic Tape 25/-.

OP TRANSFORMERS. Heavy Duty 50 m.A., 4/6

Multitap, push-pull, 8/6. Small pentode 3/9.

F.L. CHOKES 15-10 H. 10/65 m.A. 5/-; 10 H.

80 m.A. 6/5; 30 H. 150 m.A. 12/6.

MAINS TRANS. 250-0-250, 50 m.A., 6.3 v., tapped

4 v., 4 s., 5 v., tapped 4 v., 2 a., ditto 250-0-250, 21/-

Bargain, 250-0-250 50 m.A., 6 v., 4 a., 4 v., 2 a., 15/-

HEATER TRANS. Tapped primary, 200/250 v., 6.3 v.

1 amp., 7/6; tapped sec. 2, 4, 6.3 v., 1 amp., 8/6;

prim. 250 v. sec. 6.3 v., 3 amp., 10/6.

ALADDIN FORMERS and core, 1/6; 21/2, 1/6; 10, 1/6

0.3 in. FORMERS 5037 8 and Cans TV1.2, 1/6; sq. 3

in. and 1/2 in. sq. x 1 1/2 in., 2/- ea., with cores.

TYANA—Midget 3A5 12.5, 200/240 v. or

250-250 v., 16.9. Solon Instrument 10, 24/-

MAINS DROPPERS, 3 in. x 1 1/2 in., Adl. Sliders, 3

amp., 750 ohms, 4/3. 2 amp., 1,000 ohms, 4/3.

LINE COORD. 3 amp., 60 ohms per foot, 2 amp., 100

ohms per foot, 3-way, 6d. per foot, 3-way, 7d. per foot.

LOUDSPEAKERS 2 M. 3 O.E.M. 2 1/2 in., 17/6

5 in. Goodman, 17/6. 7 in. H. Goodman, 21/-

3 1/2 in. Goodman, Elac, 21/-

5 in. Goodman, 18/6. 10 in. R. A. & Co., 30/-

TSL Tweeter, L573, 8/6. 12 in. Pleasure, 24/6

SIN. M.E. 2.5d. each, tapped O.P. trans., 24/6

CRYSTAL DIODE G.E.C. 2/- GEX34 4/-

HIGH RESISTANCE PHONES, 4,000 ohms, 16/6 p.

MIKE TRANSF. Ratio 50:1, 3.9 ea.; 100:1, 10/6

CRYSTAL MIKE INSERT by Acco, precision

engineered. Size only 1 1/2 x 3 1/2 in. Bargain

Price 6/6. No transformer required.

SWITCH CLEANER Fluid, squirt sprout, 4/3 tin.

TWIN GANG TUNING CONDENSERS. 365 pf.

miniature 1 in. x 1 1/2 in., 10 s., .0005 Standard

size with trimmers, 9/-; less trimmers, 8/-; midget,

7/6; standard .0005 mid, 3/6; 7/6.

SPEAKER PRET. Expanded Metal Silver, 15 1/2 in.

x 9 1/2 in., 2 each; 14 1/2 in. x 12 1/2 in., 3 ea.

GOLD CLOTH. 18 in. x 25 in., 5/-; 25 in. x 36 in., 10/-

TRANSISTORS (Red Spot) similar to OC71 10/- ea.

VALVES

All Boxed 1/6 New & Guaranteed

3/6 5/6 EA50 6/6 10/6

1R5 6B8 954 6AL5 524

1T4 D92 2/6 6J7 12A77

185 EP50 6K6 12AU7

884 6X4 6BE6 12BC6

3V4 EP81 EB34 EP80 EP85

5U4 SP41 3/6 HVR2 ECL80

6AM6 EP92 3/6 (near) EP41

6AT6 PEN 4d 6H6M 8K7 EP40

6K8 7/6 7/6 7/6 EL41

6SL7 6BE6 6BE6 12BE6 EL84

6SN7 6BW6 6X4 EL32 EZ40

6V6GT 6D6 6X5 HVR2A KT33C

EB3C3 6P6 6X5 PEN25 MT14

EP50 6K7GT EP20 VP25 PY81

Navy Red EP91 12K7

EP91 3524

EZ40 EY31 U25 PL51 6Q7



1957 RADIOGRAM CHASSIS

THREE WAVEBANDS FIVE VALVES

S.W. 16 m.—50 m. LATEST MULLARD

M.V. 200 m.—550 m. ECH42, EF41, ECH40,

L.W. 800 m.—2,000 m. EL41, EZ40,

12 month guarantee.

A.C. 200/250 v. 4-way switch; Short-Medium-

Long-Gran. A.V.C. and Negative feedback

42 watts. Chassis 10 1/2 x 2 1/2 in. Glass Dial

10 x 4 in. horizontal or vertical available.

2 Pilot Lamps, Four Knobs, Walnut or Ivory.

Aligned and calibrated. Chassis isolated from

mains. T.S.L. Tweeter Supplied Free!

10 gns. Carr. & ins., 4/6.

TERMS: Deposit £5.50 and six monthly

payments of £1.

AM/FM RADIOGRAM CHASSIS

Measurements 13 in. x 6 in. x 7 in. high. Dial

cut-out required only 10 1/2 in. x 2 1/2 in. 5 valve

plus metal rect., gram. socket, piano key

wavechange, tone control, med. long and

V.H.F. wavebands. Valve line-up: ECC85,

80H1, EP80, RABCO8, EL41. For A.C.

mains 100-250 v.

PRICE £16.19.6 Carriage 10/6.

MATCHED SPEAKERS FOR BOTH CHASSIS

Sin., 19.6; 10 in., 25/-; 12 in., 30/-.

B.S.R. MONARCH 4-SPEED RECORD

CHANGERS 1957 MODELS

Brand new and fully guaranteed 12 months.

NOT JOB LINE REJECT STOCK

Designed to play 10, 33, 45, 78 r.p.m. Records,

7 in., 10 in., 12 in. Lightweight Xtal pick-up,

turnover head, two separate sapphire styl,

for Standard and L.P., each plays 2,000 records.

Voltage 200-250 A.C.

OUR PRICE £8.15.0 each, Post Free.

Terms: Deposit £5 and 5 monthly payments

of £1. Space required 14 in. x 12 in. 5 in.

above and 3 in. below.

GARRARD R 80m 3 speed Autochange Universal

AC-DC 100-250 volts. List price £27.10/-

OUR PRICE £15.15.0 carr. & ins. 5/6

COLLARO AUTO-CHANGER RC631 for 78

r.p.m., 10 in. and 12 in. records. Brand new

in maker's boxes! High impedance lightweight

Pick-up with sapphire needle, will match any

Amplifier or Radio. Less than half price.

5 gns. Post free. Sorry—No C.O.D.

SUPERHET COIL PACK 27/6. Miniature

size 2 1/2 in. x 2 1/2 in. x 1 1/2 in. "Q" Dist

cored Coils. Short, Medium, Long, Gran.

Switching. Single hole fixing with connection

diagram, and circuit. 455 Kc/s L.F.

B.S.R. MONARCH. 3-speed Motor and Turntable

with selecting switch for 33, 45 and 78

r.p.m. records. 100-120 v. and 200-250 v. A.C.

50 cps. Also B.S.R. MONARCH Lightweight

Pick-up with Acco Xtal turnover head, separate

Sapphire styl for L.P. and Standard records.

SPECIAL OFFER, THE TWO! £4.12.6 post 2/6.

T.V. PRE-AMP (MEMICHAEL). Tunable

Channels 1 to 5. (With Amplify Output of your

Band 3 Converter.) Midget size. High Gain.

Ready for use. (H.T. 200 v., L.T. 6.3 v., 3

amp. required.) BRAND NEW, £25.00. ea.

MAINS POWER PACK for above, 25/- extra.

TELETRON BAND III CONVERTER

For London, Midland and Northern I.T.A.

MARK I

Suitable all T.V. makes. T.R.F. or Superhet.

Ready wound coils, two EF80 valves, all

components, punched chassis, circuit diagram,

wiring plans. COMPLETE KIT for mains

operation 200-250 v. A.C. £3.10.0.

As ABOVE less POWER PACK. Requires

200 v. 50 m.A. H.T. 6.3 v. 10 s., L.T. £2.5.0.

Mark II cascade £1 extra each Kit

Mains Transformers to above Spec. ... 10/6

Mln. Contact Rect. 250 v. 50 m.A. ... 8/6

D.B.C./I.T.A. aerial crossover unit ... 7/6

Punched and drilled chassis 1/- 50 ohms only

Larger chassis for Main Model ... 8/-

Teletron Collect Mk. I, 15/-; Mk. II, 17/6.

Full plans and circuit details ... 6d.

VOLUME CONTROLS 80 ohm CABLE COAX

Long spindles. Guaranteed 1 year. Midget,

10,000 ohms to 2 Meg.

No Sw. S.P.S. D.P.S. 3/-

4/- 4/9

Ltn or Log Tracks. 1 in. Coax 8d. yd

COAX PLUGS — 1/- DOUBLE SOCKET — 1/3

SOCKETS 1/- OUTLET BOXES — 4/6

BALANCED TWIN FEEDER, yd. 6d. 80 or 300 ohms

DITTO SCREENED per yd. 1/- 80 ohms only

WIRE-WOUND POTS. 3 WATT. Pre-Set Min.

T.V. Type. All values 25 ohms to 30 K. 3/- ea.

50 K. 4/- (Carbon 50 K. to 2 m., 3/-)

WIRE-WOUND 4 WATT. Pots 2 1/2 in. Spindle.

Values, 100 ohms to 50 K. 5/6; 100 K. 6/6

CONDENSERS. New stock. .001 mid. 7 kV.

T.C.C.S. 5/6; DITTO 20 kV. 9/6; 100 pf. to 500 pf.

MMS. 6d.; Tubular 500 v. .001 to .01 mid., 9d.

.05, .1, .15, 1.6, 3.3, 6.3, 10, 15, 20, 25, 50, 100

.1/600 v. 1/3; 1 mfd., 2,000 volts, 4/-

CERAMIC CONDS., 500 v., .3 pf. to .01 mid., 10d.

SILVER MICA CONDENSERS. 10v., 5 pf. to 300

pf. 1/-; 400 pf. to 1,000 pf., 1/3. DITTO 1/2

1.5 pf. to 500 pf. 1/3; 515 pf. to 5,000 pf., 2/-

I.F. TRANSFORMERS 7/6 pair

465 Kc. Slug type Miniature Can. 2 1/2 in. x

1 in. x 1 in. High Q and good bandwidth.

By Pte Radio. Data sheet supplied.

Wearite M800 IF 455 Kc/s 12/6 per pair.

NEW ELECTROLYTICS. FAMOUS MAKES

TUBULAR TUBULAR CAN TYPES

1/350 v. 2/- 100/250 v. 2/- 8+10/500 v. 5/6

2/450 v. 2/8 8+5/500 v. 4/6 16+16/500 v. 6/-

4/450 v. 2/- 16+16/500 v. 25+25/450 v. 5/6

8/500 v. 2/- 32+32/500 v. 32+32/500 v. 4/6

16/450 v. 3/6 Clips 3/6 50+50/350 v. 6/6

16/500 v. 4/- 16/450 v. 3/6 60+100/350 v. 11/6

32/450 v. 5/6 32/350 v. 4/- 100+200/275 v. 12/6

25 v. 1/2 150/450 v. 3/6 1,000+1,000/6 v. 12/6

50/50 v. 2/- 8+16/450 v. 5/6

Screw Base Type 512, 8/500 v. 3/-; 16/500 v. 4/6

SEVENGEAR RECTIFIERS. E.H.T. TYPE FLY-

BACK VOLTAGE. K3/20 v. 2 kV. 5/-; K3/40 v. 4 kV. 7/-

K3/100 v. 8 kV. 14/6. MAINS TYPE CONTACT

COOLED 250 v. 50 m.A., 8/6; 250 v. 35 m.A., 9/6

COILS Wearite. "P" type, 8/- each. Osborn Midget

"Q" type mid. dist. core, 4/- each. All ranges.

TELETRON. L & Med. T.R.F. with reaction 3/6

FERRITE ROD AERIALS. M.W. 3/9; M & L. 12/6

T.R.F. COILS A/H.P. 7/- pair. H.F. CHOKES, 2/6

ALUMINIUM CHASSIS. 18 s.w.g. undrilled.

With 4 sides, riveted corners and lattice fixing

</